 


Logic design (2016 fall)


Quiz # 11

Name: _____ ID: _____

1. (100%) The X flip-flop with three S-R latches is as follows.



 
(a) (64%) Complete the following timing diagram, if initially $S = Q = 0$ and $T = U = V = Q' = 1$. Note that each NAND gate has the same propagation delay 5ns.



- (a) (6%) Which active edge can trigger the X flip-flop: rising edge or falling edge?
- (b) (20%) Is the X flip-flop edge-triggered? Explain your reasoning.
- (c) (10%) Derive and minimize the next-state equation for the X flip-flop.

Ans:

(a)

 

(b)

Rising Edge

(c)

Yes.

The value of X at the time of the rising clock edge determines the value of Q and any extra changes in X that occur between rising clock edges have no effect on Q.

(d)

$$Q(t+\epsilon) = X$$