

Logic design (2016 fall)

Quiz # 15

Name: _____ ID: _____

1. (60%) Given below is incompletely specified state table.

<i>Present State</i>	<i>Next State</i>		<i>Present Output</i>
	<i>X = 0</i>	<i>1</i>	
S_0	S_1	S_0	0
S_1	S_0	S_2	0
S_2	S_3	S_4	1
S_3	S_0	S_3	0
S_4	S_0	—	0

- (a) (20%) Reduce the state table to four states in two different ways by specifying proper states for the don't-care term in the state table and show the two different reduced tables.
- (b) (40%) Use an implication table to determine whether your two state tables in part (a) are equivalent; if they are, prove your answer by showing equivalent states.

Ans:

(a)

Reduced table 1 (T_1)

Present State	Next State		Present Output
	X = 0	1	
S_0	S_1	S_0	0
S_1	S_0	S_2	0
S_2	S_3	S_1	1
S_3	S_0	S_3	0


Reduced table 2 (T_2)

Present State	Next State		Present Output
	X = 0	1	
S_0	S_1	S_0	0
S_1	S_0	S_2	0
S_2	S_3	S_3	1
S_3	S_0	S_3	0

(b)

S_0	S_1-S_1' S_0-S_0'	S_1-S_0' S_0-S_2'	S_1-S_0' S_0-S_3'	
S_1	S_0-S_1' S_2-S_0'	S_0-S_0' S_2-S_2'	S_0-S_0' S_2-S_3'	
S_2	S_3-S_3' S_1-S_3'	S_3-S_3' S_1-S_3'	S_3-S_3' S_1-S_3'	
S_3	S_0-S_1' S_3-S_0'	S_0-S_0' S_3-S_2'	S_0-S_0' S_3-S_3'	
	S_0'	S_1'	S_2'	S_3'

No equivalent states

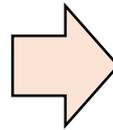

$$T_1 \neq T_2$$

2. (40%) Following shows the state table of a Moore sequential circuit, which has two inputs X, Y and two outputs Z_1, Z_2 .

<i>Present State</i>	<i>Next State</i>				<i>Present Output</i> Z_1Z_2
	$XY = 00$	01	11	10	
S_0	S_0	S_3	S_0	S_3	10
S_1	S_0	S_1	S_2	S_3	01
S_2	S_1	S_1	S_2	S_2	01
S_3	S_0	S_2	S_1	S_3	11

If the sequential circuit is implemented by using primitive gates and D flip-flops based on one-hot encoding, write down and minimize output functions for Z_1, Z_2 and next-state equations for $Q_0^+, Q_1^+, Q_2^+, Q_3^+$, which correspond to states S_0, S_1, S_2, S_3 respectively.

Ans:

$$Q_0^+ = X'Y'Q_0 + XYQ_0 + X'Y'Q_1 + X'Y'Q_3$$

$$Q_1^+ = X'YQ_1 + X'Y'Q_2 + X'YQ_2 + XYQ_3 = X'YQ_1 + X'Q_2 + XYQ_3$$

$$Q_2^+ = XYQ_1 + XYQ_2 + XY'Q_2 + X'YQ_3 = XYQ_1 + XQ_2 + X'YQ_3$$

$$Q_3^+ = X'YQ_0 + XY'Q_0 + XY'Q_1 + XY'Q_3$$

$$Z_1 = Q_0 + Q_3$$

$$Z_2 = Q_1 + Q_2 + Q_3$$