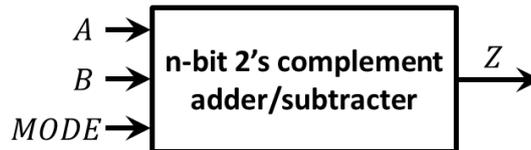


Logic design (2016 fall)
Quiz # 16

Name: _____ ID: _____

1. (30%) Design an n-bit 2's complement adder/subtractor using **one** 1-bit full adder, **one** D flip-flop, and **one** exclusive-OR gate. When *MODE* is 1, the circuit should output $A - B$, otherwise, it should output $A + B$. The definitions for inputs and outputs are shown as below.



Input signals :

A, B : n-bit serial-in 2's complement number ($A = A_n \dots A_1 A_0$ and $B = B_n \dots B_1 B_0$) with the LSB (least significant bit) first.

MODE :

0 (adder) : $Z = A + B$





1 (subtractor) : $Z = A - B$

Clock : clock

Output signals :

Z : n-bit serial-out 2's complement number ($Z = Z_n \dots Z_1 Z_0$) with the LSB first.

    Please draw your circuit by using the following blocks.



2. Given the transition table of a sequential circuit,

- (a) (30%) Draw a block diagram that shows how a ROM and two D flip-flops could be connected to realize the sequential circuit. Note that you must specify the size of the ROM.
- (b) (40%) Specify the contents of the PLA in the following tabular form if a PLA and two D flip-flops are used to realize the sequential circuit.

Transition table

Present State Q_1Q_2	Next State $Q_1^+Q_2^+$		Z
	X = 0	X = 1	
00	01	10	1
01	01	01	0
11	01	10	0
10	00	10	0

Product term	Inputs XQ_1Q_2	Outputs ZD_1D_2
XQ_2'	1-0	010
XQ_1	11-	010
$X'Q_1'$	00-	001
$X'Q_2$	0-1	001
$Q_1'Q_2$	-01	001
$Q_1'Q_2'$	-00	100

AND plane OR plane

