 


Logic design (2016 FALL)

Quiz # 8

Name: _____ ID: _____

1. (100%) Assuming that only one input signal can change each time, the given circuit may generate a static-1 hazard at the output F when some specific pairs of input values are supplied.
 - (a)(20%) Finish the Karnaugh map for F .
 - (b)(50%) Write down the terms which should be added.
 - (c)(30%) Write down all possible pairs of input values which can cause a static-1 hazard at output F .




(a)

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

(b) $F = A'B'C' + BC + AB'D$

Ans:

(a)

 

(b) $F = A'B'C' + BC + AB'D + ACD + B'C'D$

(c) $(A, B, C, D) = (1, 0, 0, 1) \rightarrow (0, 0, 0, 1)$

$(A, B, C, D) = (1, 1, 1, 1) \rightarrow (1, 0, 1, 1)$