


Logic design (2016 fall)

Quiz # 9

Name: _____ ID: _____

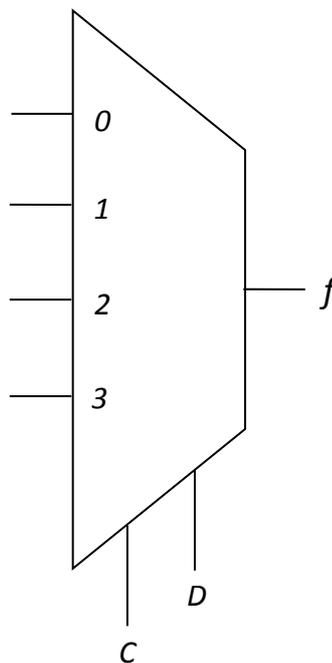
1. (50%) Given $f(A,B,C,D) = C'D + AB'C' + A'BD + BC'D + ABC'D' + ABCD$.

Implement the function f using a given 4-to-1 multiplexer with C and D as the select inputs where C is the most significant bit and D is the least significant bit. Note that complement inputs are not allowed.



Ans:
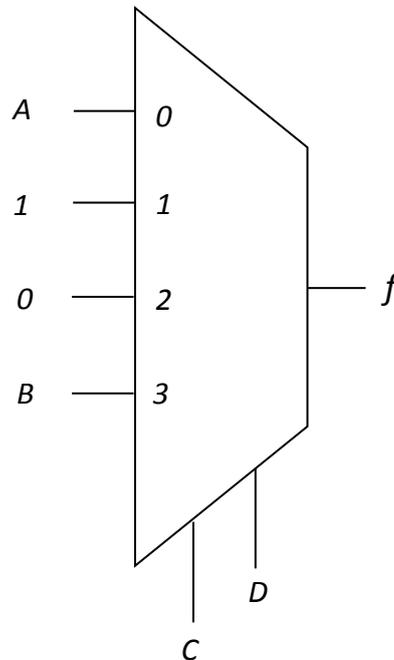
$$\begin{aligned} f(A,B,C,D) &= C'D + AB'C' + A'BD + BC'D + ABC'D' + ABCD. \\ &= C'D' \cdot (AB' + AB) + C'D \cdot (1 + AB' + A'B + B) + CD' \cdot (0) + CD \cdot (A'B + BC' + AB) \\ &= C'D' \cdot (A) + C'D \cdot (1) + CD' \cdot (0) + CD \cdot (B) \end{aligned}$$



2. (50%) Excess-3 and 2-out-of-5 codes for decimal digits are shown in the following table.

Decimal digit	Excess-3 code	2-out-of-5 code
0	0011	00011
1	0100	00101
2	0101	00110
3	0110	01001
4	0111	01010
5	1000	01100
6	1001	10001
7	1010	10010
8	1011	10100
9	1100	11000

Specify the data stored in the following 16-word \times 5-bit ROM that can realize an Excess-3 code to 2-out-of-5 code converter with four addresses inputs (W, X, Y, Z), representing Excess-3 code, and five data outputs (A, B, C, D, E), representing 2-out-of-5 code. Note that the signal W is the most significant bit of the address inputs and A is the most significant bit of data outputs.

Address Inputs				Data Outputs				
W	X	Y	Z	A	B	C	D	E
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

Ans:

<i>W X Y Z</i>	<i>A B C D E</i>
0 0 0 0	X X X X X
0 0 0 1	X X X X X
0 0 1 0	X X X X X
0 0 1 1	0 0 0 1 1
0 1 0 0	0 0 1 0 1
0 1 0 1	0 0 1 1 0
0 1 1 0	0 1 0 0 1
0 1 1 1	0 1 0 1 0
1 0 0 0	0 1 1 0 0
1 0 0 1	1 0 0 0 1
1 0 1 0	1 0 0 1 0
1 0 1 1	1 0 1 0 0
1 1 0 0	1 1 0 0 0
1 1 0 1	X X X X X
1 1 1 0	X X X X X
1 1 1 1	X X X X X