

Logic design (2016 spring)

Quiz # 12

Name: _____ ID: _____

Design a counter with 4 flip-flops (denoted as A, B, C and D) that can generate the following Boolean sequence. (ABCD) = 0000,1001,1000,0111,0110,0101,0100,0011,0010,0001,0000,..... (repeat). Note that you don't need to draw the circuit. You just need to derive the Boolean equations for the inputs of the four flip-flops.

(a) (40%) Design the counter with 4 D flip-flops. Just derive the minimum SOP for D_A , D_B , D_C and D_D

ABCD	$A^+B^+C^+D^+$
0000	1001
0001	0000
0010	0001
0011	0010
0100	0011
0101	0100
0110	0101
0111	0110
1000	0111
1001	1000
1010	XXXX
1011	XXXX
1100	XXXX
1101	XXXX
1110	XXXX
1111	XXXX

