

Logic design (2016 spring)


Quiz # 5

Name: _____ ID: _____

1. (40%) Given $f(A,B,C,D) = C'D + A'CD + A'BD' + AB'C'D'$

Using a Karnaugh map to find the minimum sum of products and the minimum product of sums.

Ans:

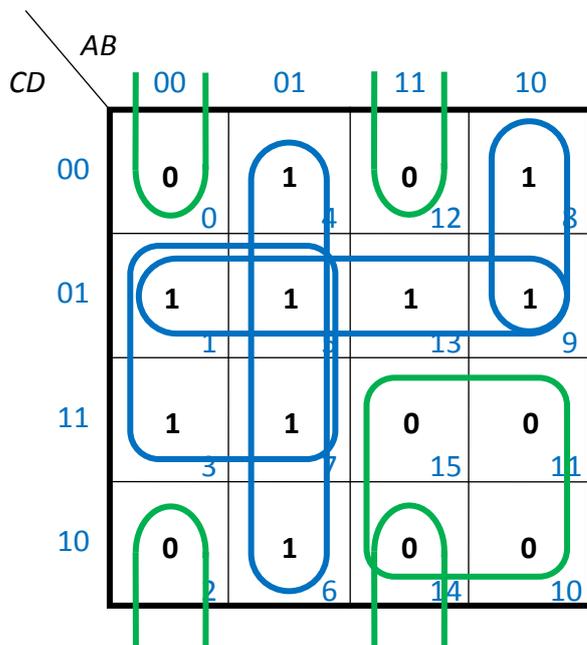


$$f = A'B + A'D + C'D + AB'C'$$

$$= (A' + C')(A' + B' + D)(A + B + D)$$

2. (60%) Given $f(A,B,C,D,E) = \sum m(4, 7, 9, 10, 12, 15, 19, 21, 25, 26, 27, 28, 29, 30) + \sum d(1, 2, 16, 17, 23, 31)$.
Using a Karnaugh map to find the minimum sum of products expression and underline essential prime implicants in your answer.

Ans:

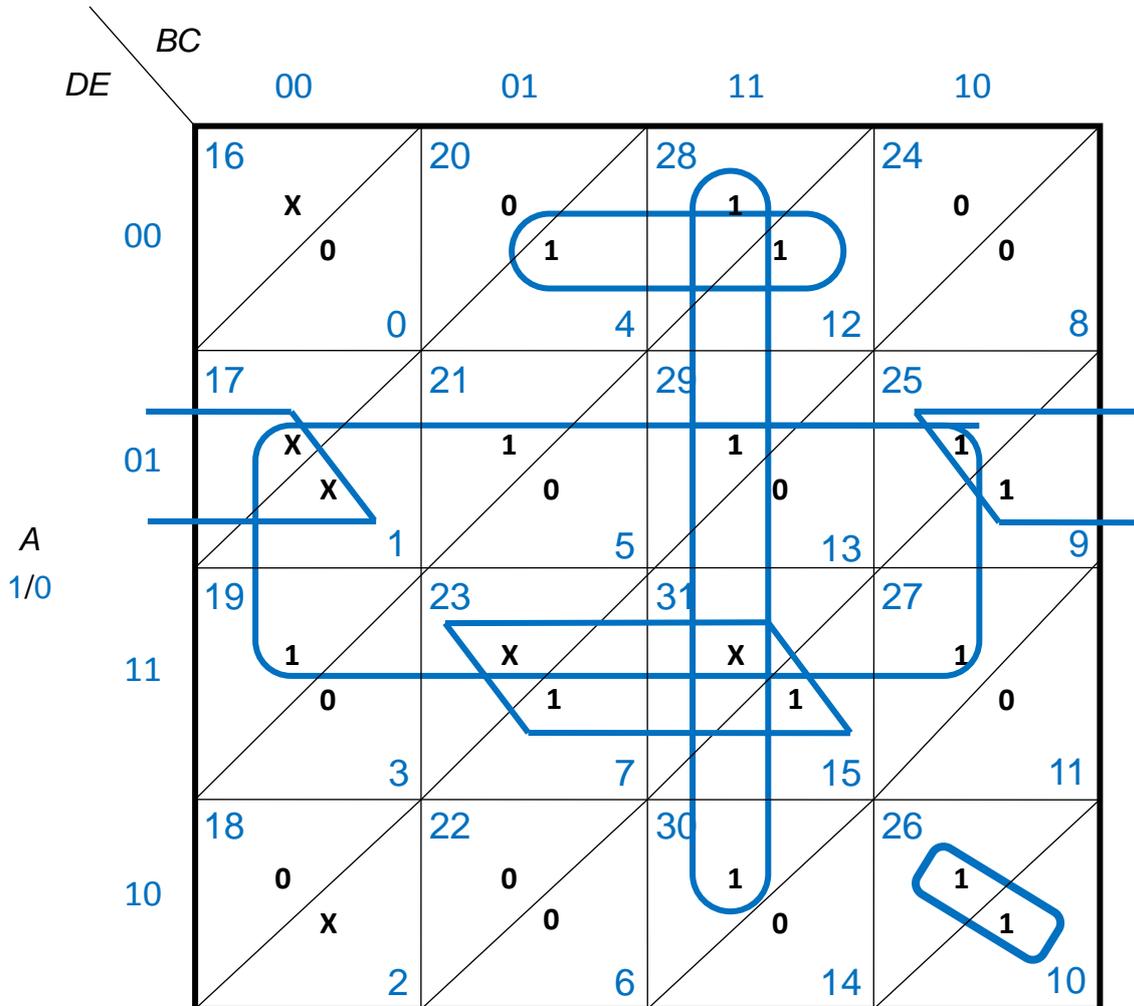

$$f = \underline{AE} + \underline{ABC} + \underline{CDE} + \underline{C'D'E} + \underline{A'CD'E'} + \underline{BC'DE'}$$