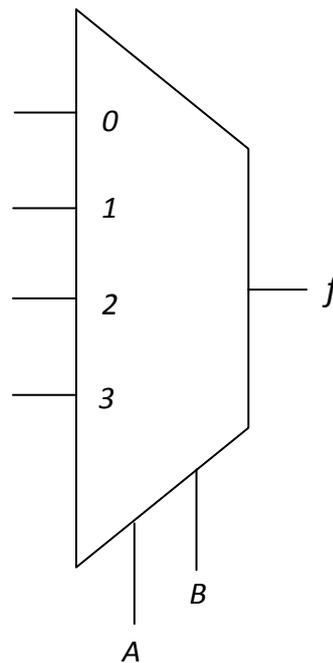


Logic design (2016 spring)

Quiz # 9


Name: _____ ID: _____

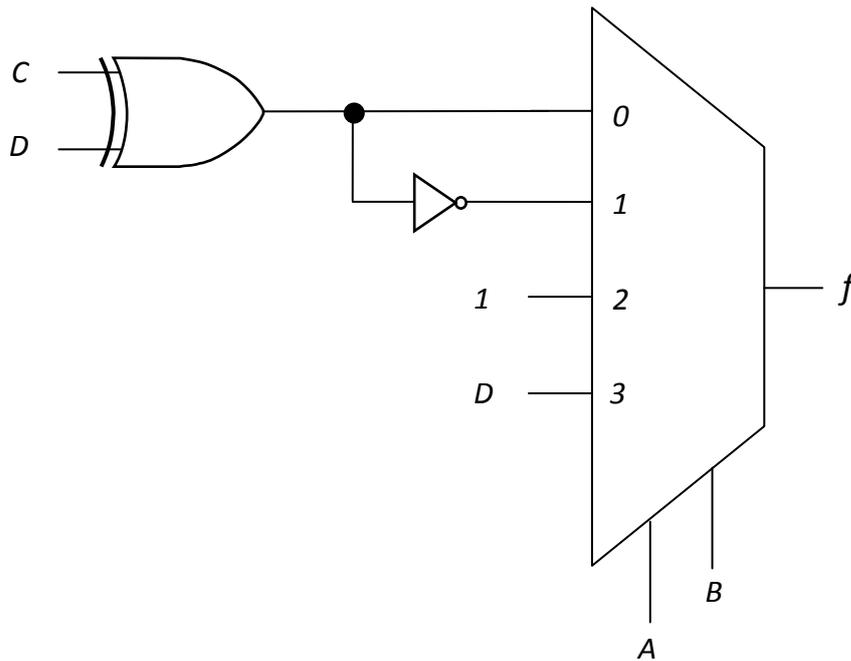1. (40%) Realize the function $f(A,B,C,D) = AD + AB'C' + BCD + B'CD' + A'BC'D' + A'B'C'D$ using only a XOR gate, a NOT gate and a 4-to-1 multiplexer with A and B as the select inputs where A is the most significant bit and B is the least significant bit. Note that complement inputs are not allowed.



Ans:

$$\begin{aligned} f(A,B,C,D) &= AD + AB'C' + BCD + B'CD' + A'BC'D' + A'B'C'D \\ &= A'B' \cdot (C'D + CD') + A'B \cdot (C'D' + CD) + AB' \cdot (C' + CD' + D) + AB \cdot (CD + D) \\ &= A'B' \cdot (C'D + CD') + A'B \cdot (C'D' + CD) + AB' \cdot (1) + AB \cdot (D) \end{aligned}$$




2. (60%) Implement the following equations using the PLA with four product terms only.

$$f_1(A,B,C,D) = \prod M(0, 1, 3, 4, 6, 8, 9, 11)$$

$$f_2(A,B,C,D) = \prod M(1, 3, 6, 9, 11, 13, 14, 15)$$


(a) (40%) List the four product terms used in the PLA

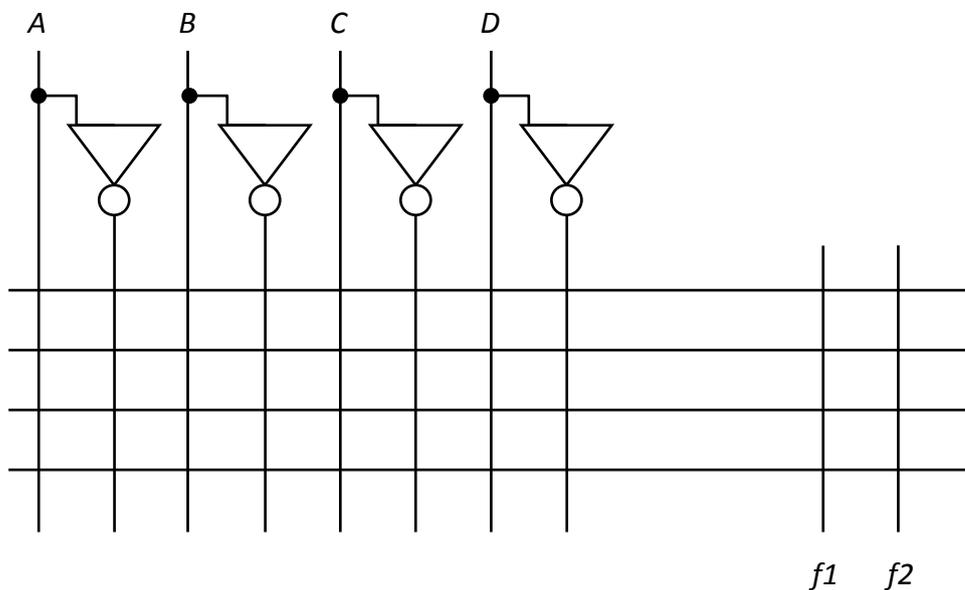(b) (20%) Following shows the PLA structure, of which left and right side are AND array and OR array respectively. The intersection of a row and input or output lines indicates the presence of a switching element in the array. Indicate the connections which will be made to program the PLA



Ans:

(a)

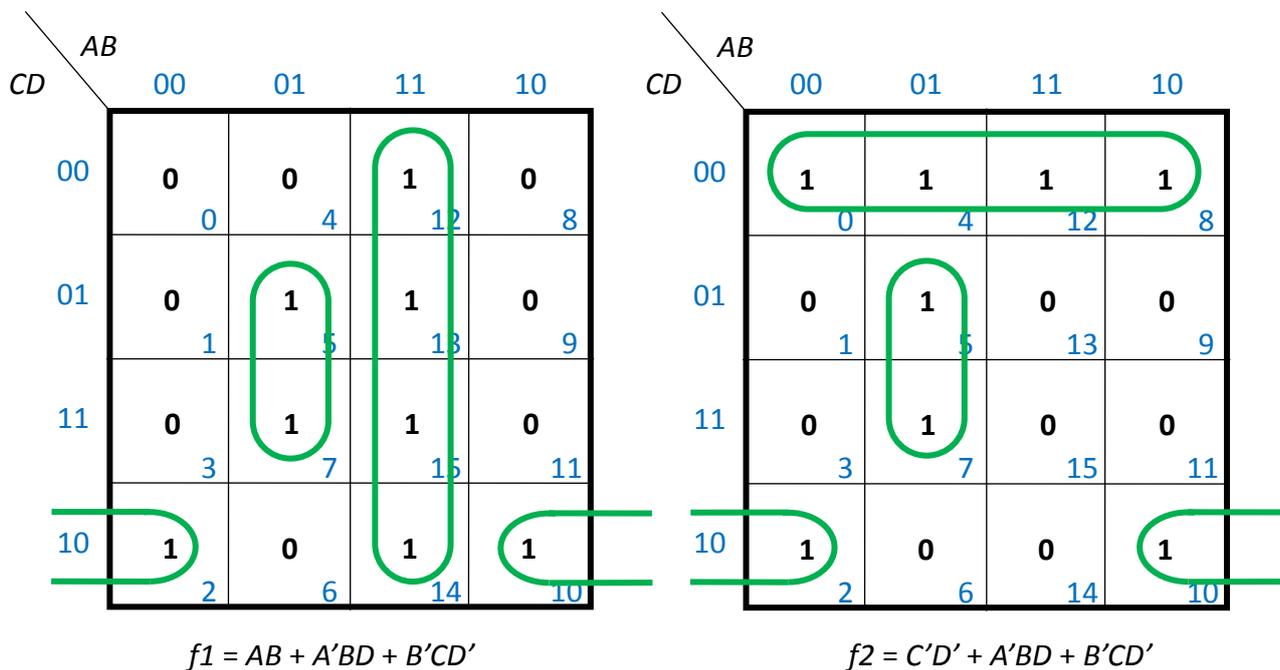

<i>A B C D</i>	<i>f₁ f₂</i>
11--	10
--00	01
01-1	11
-010	11

(b)

