

UNIT 11

LATCHES AND FLIP-FLOPS



Spring 2011


Latches and Flip-Flops

- **Contents**
 - Set-Reset latch
 - Gated D latch
 - Edge-triggered D flip-flop
 - S-R flip-flop
 - J-K flip-flop
 - T flip-flop
 - Flip-flops with additional inputs
- **Reading**
 - Unit 11

Recap: Two Types of Switching Circuits


□ Combinational circuits (**memoryless**)

 - Outputs depend only on **present** inputs



□ Sequential circuits (**with memory**)

 - Outputs depend on both **present** & **past** inputs
- In general, **sequential ckts = combinational ckts + memory**




How to Remember the Past?

- **Feedback:** the output of one of the gates is connected back into the input of another gate in the ckt so as to form a closed loop

- e.g., inverter with feedback

- Q: How fast does the circuit oscillate?

 
- A: Determined by the propagation delay of the inverter



- e.g., a feedback loop with two inverters

- Two stable states

 - **Latch:** basic memory unit (**store 1 bit**)







5

Set-Reset Latch

S-R latch


Set-Reset (S-R) Latch (1/2)

    


$$P = Q'$$

S-R Latch (2/2)

□ Cross-coupled form


 


 □ $S = R = 1 \Rightarrow$ Unstable! Not allowed!!



Next-State Equation



Timing diagram

  

Operation

$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

  } Unchanged
 } Reset to 0
 } Set to 1
 } Inputs not allowed





Next-state equation:
(Characteristic equation)

$Q^+ = S + R'Q$
 under $SR=0$
 ($S=1, R=1$ not allowed)

$$Q(t+\epsilon) = S(t) + R'(t)Q(t)$$


Application: Switch Debouncing

  - **When a mechanical switch is opened or closed, switch contacts tend to vibrate before settling down \Rightarrow Debounce with S-R latch**
 - ▣ e.g, when the switch is flipped from *a* to *b*...
 - ▣ Work only with a “**double throw**” switch
 - Double throw: switch between two contacts
 - Single throw: switch between one contact and open



Alternative Form with NAND-Gates

 
- \bar{S} - \bar{R} latch: **active-low** inputs for S & R






\bar{S}	\bar{R}	Q	Q^+	
1	1	0	0	} Unchanged
1	1	1	1	
1	0	0	0	} Reset to 0
1	0	1	0	
0	1	0	1	} Set to 1
0	1	1	1	
0	0	0	—	} Inputs not allowed
0	0	1	—	

11

Gated D Latch

 

Gated D Latch

   

G	D	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Unchanged
 $Q^+ = Q$


Update
 $Q^+ = D$

		GD			
		00	01	11	10
Q	0	0	0	1	0
	1	1	1	1	0

$$Q^+ = G'Q + GD$$

13


Edge-Triggered D Flip-Flop

 


Edge-Triggered D Flip-Flops

□ **Output changes are aligned with clock edges**

 - Positive (rising-edge) trigger 
- Negative (falling-edge) trigger 
- Symbol



Rising-edge trigger

 


Falling-edge trigger

□ Truth table

<i>D</i>	<i>Q</i>	<i>Q</i> ⁺
0	0	0
0	1	0
1	0	1
1	1	1


$Q^+ = D$

 □ Timing diagram for **falling-edge triggered** D FF




D FF – Rising Edge Trigger

- Construct from 2 gated D latches

 

- Timing diagram (setup/hold time)

 


Q: What's the difference between a latch and a FF?

The value of a flip-flop' output won't change during a clock cycle.

Timing of a D FF (Setup Time/Hold Time)

- Because a flip-flop changes state only on the active edge of the clock, the *propagation delay* (t_p) of a flip-flop is the time between the active edge of the clock and the resulting change in the output.
- To function properly, the D input to an edge-triggered flip-flop must be held at a constant value for a period of time before and after the active edge of the clock.
- The amount of time that D must be stable before the active edge is called the *setup time* (t_{su}), and the amount of time that D must hold the same value after the active edge is the *hold time* (t_h).

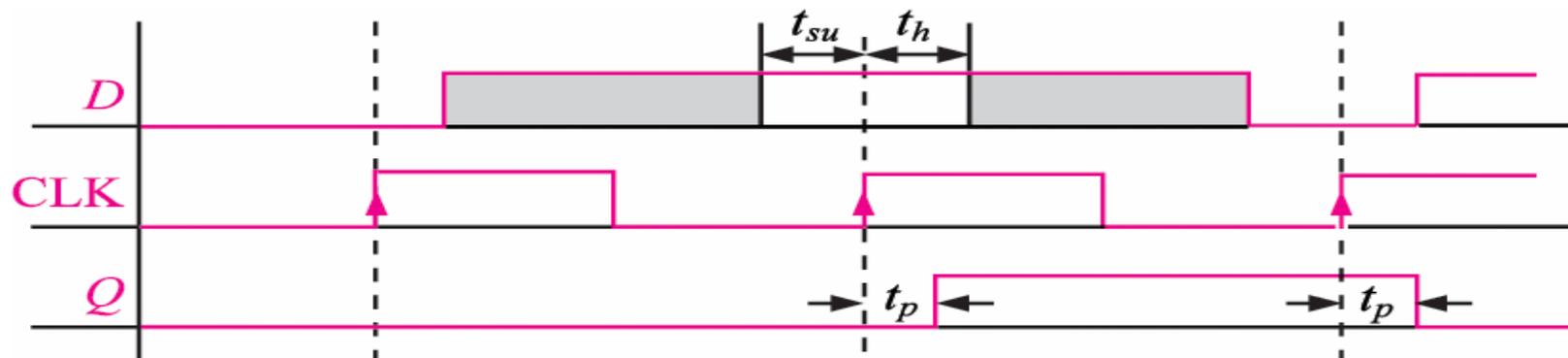


Minimum Clock Period

- **Determine the Minimum Clock Period**
 - Minimum clock period
=(total delay of gates) + (delay of flip-flop + setup time)
- **Example: Suppose that**
 - Propagation delay of the inverter = $2ns$,
 - Propagation delay of the D flip-flop = $5ns$,
 - Setup time of the D Flip-flop = $3ns$.


Determine the minimum clock period of the circuit.

Edge-Triggered D Flip-Flop


□ Example (cont.):

 


(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

 


(c) Setup time satisfied

 

(d) Minimum clock period



19

S-R Flip-Flop

 


S-R Flip Flop

  - Output changes at clock edges
- Construct from 2 latches



Operation

S	R	operation
0	0	No state change
0	1	Reset Q to 0 (after active Ck edge)
1	0	Set Q to 1 (after active Ck edge)
1	1	Not allowed

 


Not an edge-triggered FF


⇒ Do not allow SR change while CLK is low

21

J-K Flip-Flop

 


J-K Flip-Flop

 


Extension of S-R FF

- ▣ J : jump to 1
- ▣ K : clear to 0

 


J	K	Q	Q^+	$Q^+ = JQ' + K'Q$
0	0	0	0	Unchanged
0	0	1	1	
0	1	0	0	Clear to 0
0	1	1	0	
1	0	0	1	Jump to 1
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

 

23

T Flip-Flop

 


T Flip-Flop

T: Toggle


T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

$Q^+ = T'Q + TQ' = T \oplus Q$


Unchanged (for T=0)
Toggle (for T=1)

 

Implementation

 

 J-K FF based:
 $J = K = 0$ Unchanged
 $J = K = 1$ Toggle
 $Q^+ = JQ' + K'Q$
 $= TQ' + T'Q$




D FF based:
 D input: $T \oplus Q$
 $Q^+ = T \oplus Q$
 $= TQ' + T'Q$

25


FFs with Additional Inputs

D FF with Clear and Preset

 - Use additional inputs to set FF to an initial state independent of the clock
 - ▣ e.g., asynchronous Clear and Preset



Ck	D	PreN	ClrN	Q ⁺
x	x	0	0	- (not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)

 


Normal FF

Keep whole cycle

D FF with Clock Enable

 - We want some Flip-flops to **hold existing data** even though the data input may be changing
 - ▣ **Gated clock**: gate the clock by clock enable (CE)



28

Summary

Characteristic Equations for Latches & FFs

Type	Q^+
S-R latch or FF	$Q^+ = S + R'Q$ ($SR = 0$)
Gated D latch	$Q^+ = G'Q + GD$
D FF	$Q^+ = D$
D-CE FF	$Q^+ = D \bullet CE + Q \bullet CE'$
J-K FF	$Q^+ = JQ' + K'Q$
T FF	$Q^+ = T \oplus Q$