

# UNIT 9

## MULTIPLEXERS, DECODERS & PROGRAMMABLE DEVICES



Spring 2011


# Multiplexers, Decoders & PLDs

- **Contents**
  - Multiplexers
  - Three-state buffers
  - Decoders and encoders
  - Read-only memories
  - Programmable logic devices
  - Complex programmable logic devices
  - Field programmable gate arrays
- **Reading**
  - Unit 9

# 3

# Multiplexers


## MUX

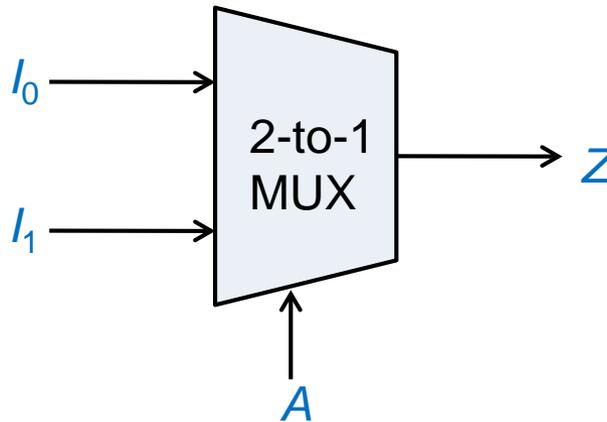

# Multiplexers (1/3)
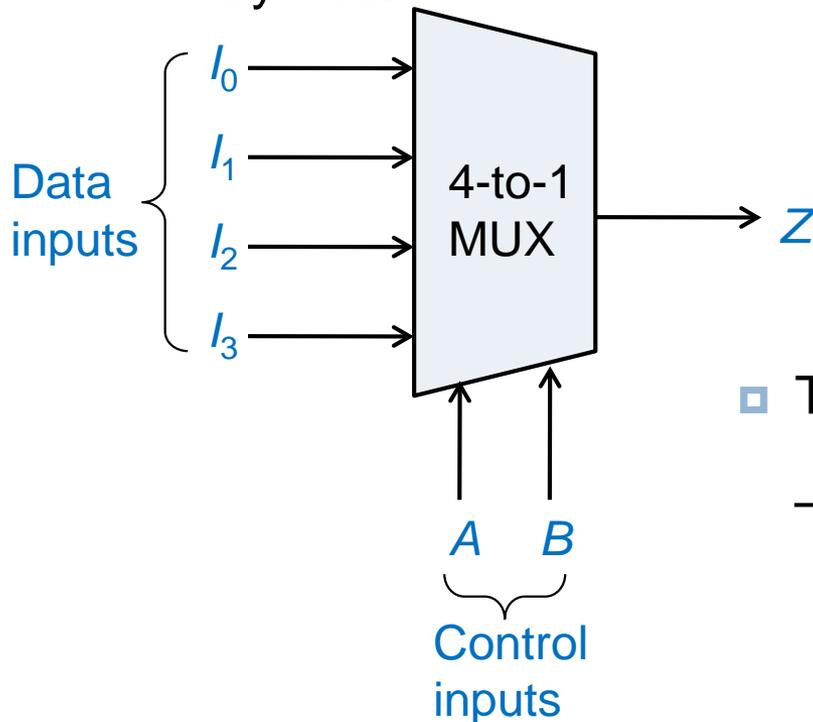
## □ A multiplexer (data selector, MUX)


- Uses the control inputs to select one of the data inputs and connects it to the output terminal
- One combination of control inputs corresponds to one data input
- Symbol



## □ Truth table

$A$	$B$	$Z$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

## □ Switch

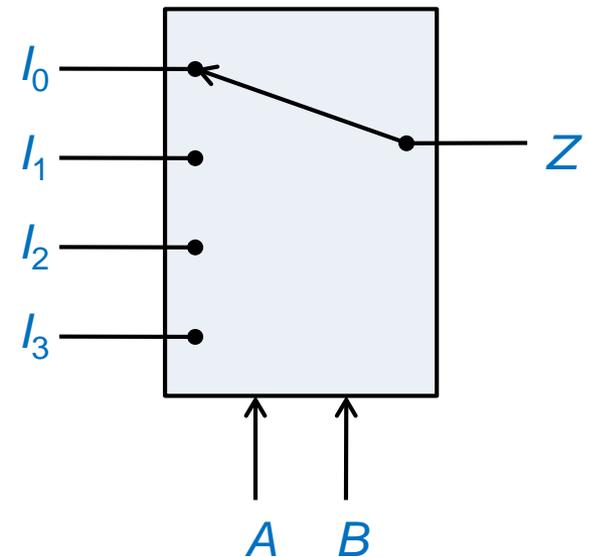


# Multiplexers (2/3)

## Logic equation of 4-to-1 MUX

$$\begin{aligned} Z &= A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3 \\ &= m_0I_0 + m_1I_1 + m_2I_2 + m_3I_3 \end{aligned}$$


A	B	Z
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

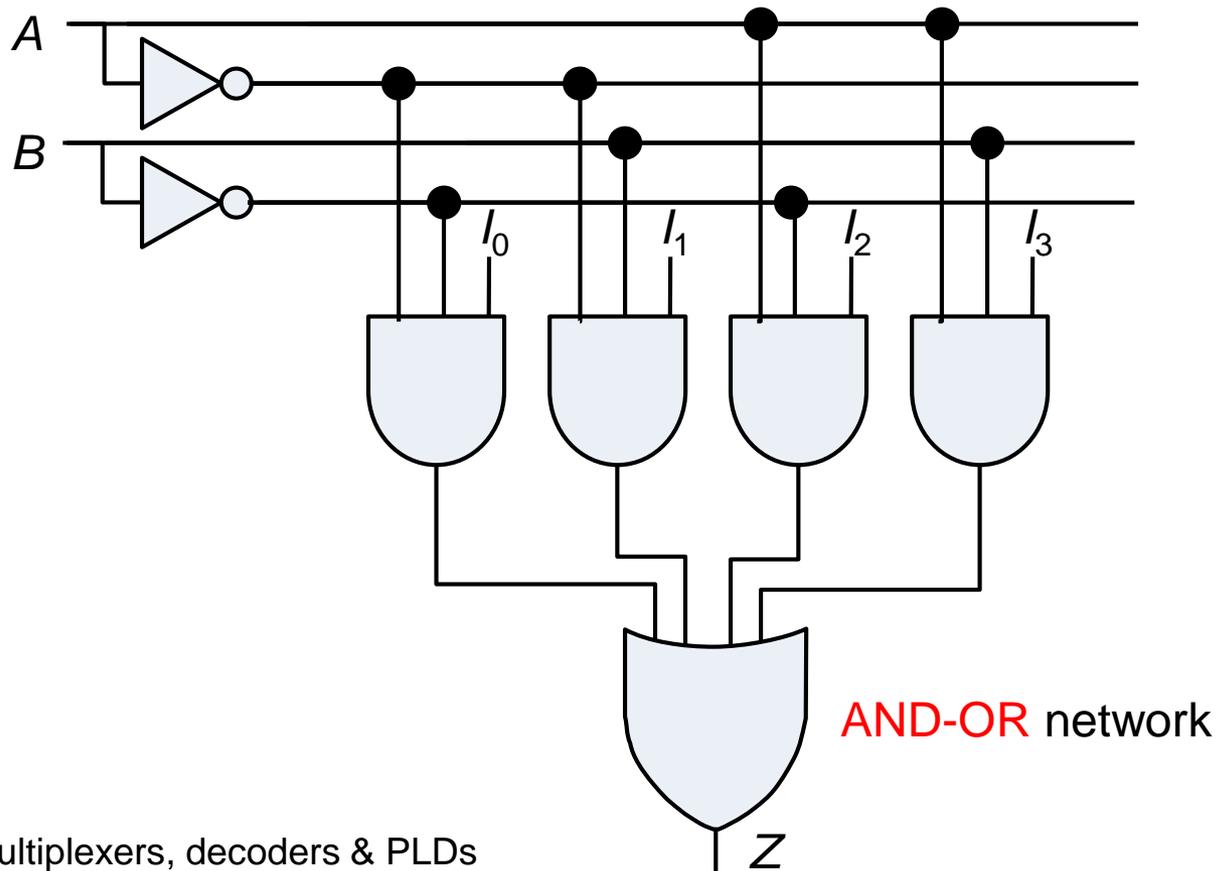

# Multiplexers (3/3)

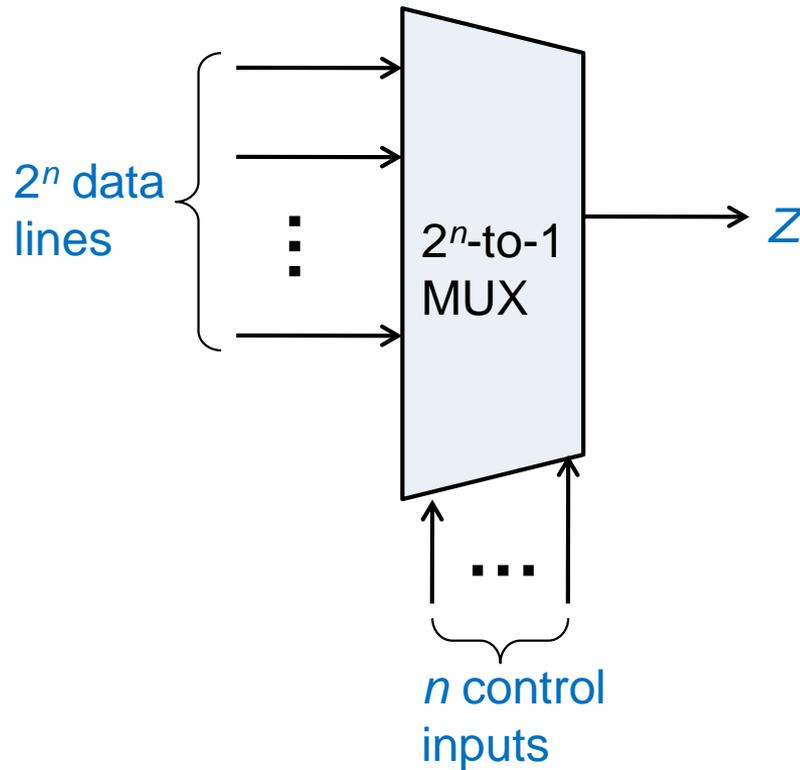
## □ The general equation for $n$ control inputs

$$\square Z = m_0 I_0 + m_1 I_1 + \dots + m_i I_i + \dots + m_{2^n-1} I_{2^n-1} = \sum_{k=0..2^n-1} m_k I_k$$



# Application: Quad Multiplexer

- Select one of two 4-bit data words

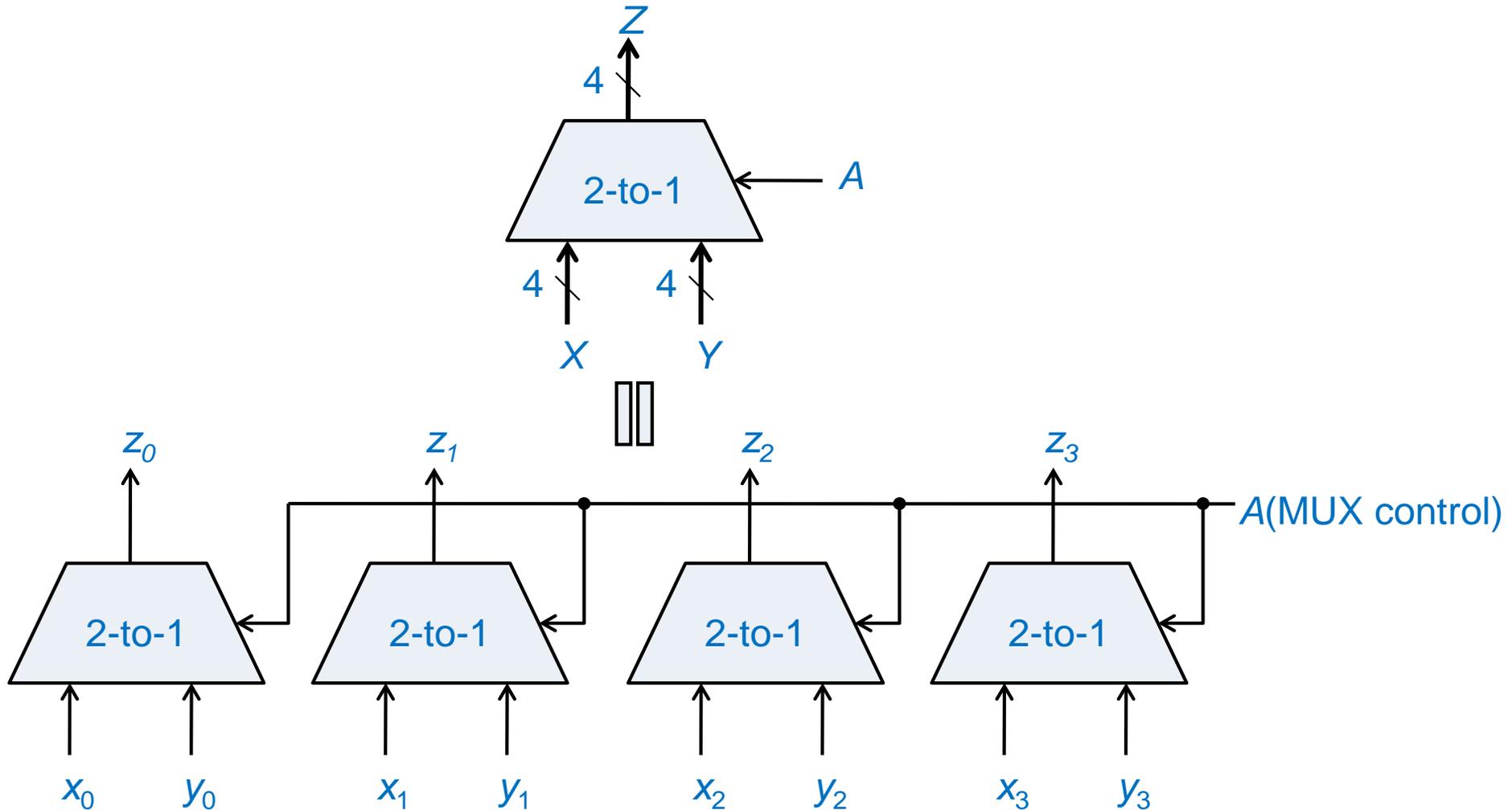


# Application: Realizing Combinational Logic

- e.g., realize a 3-variable function by a 4-to-1 MUX

$$F(A, B, C) = A'B' + AC$$


$$= A'B' + AC(B + B')$$
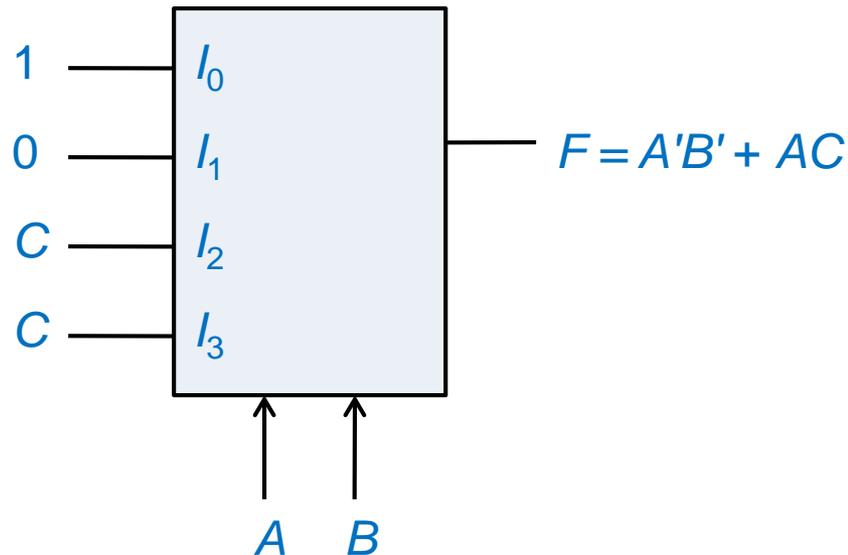
$$= 1 \bullet A'B' + 0 \bullet A'B + C \bullet AB' + C \bullet AB$$



A	B	F
0	0	1
0	1	0
1	0	C
1	1	C



## Tri-state buffers

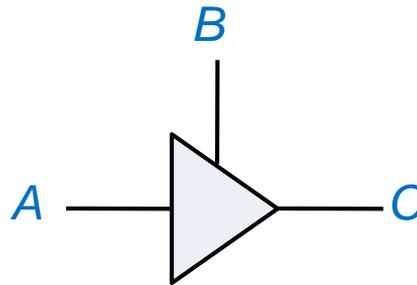

# Buffers

- **Buffers:** increase the **driving capability** of a gate output


- Symbol

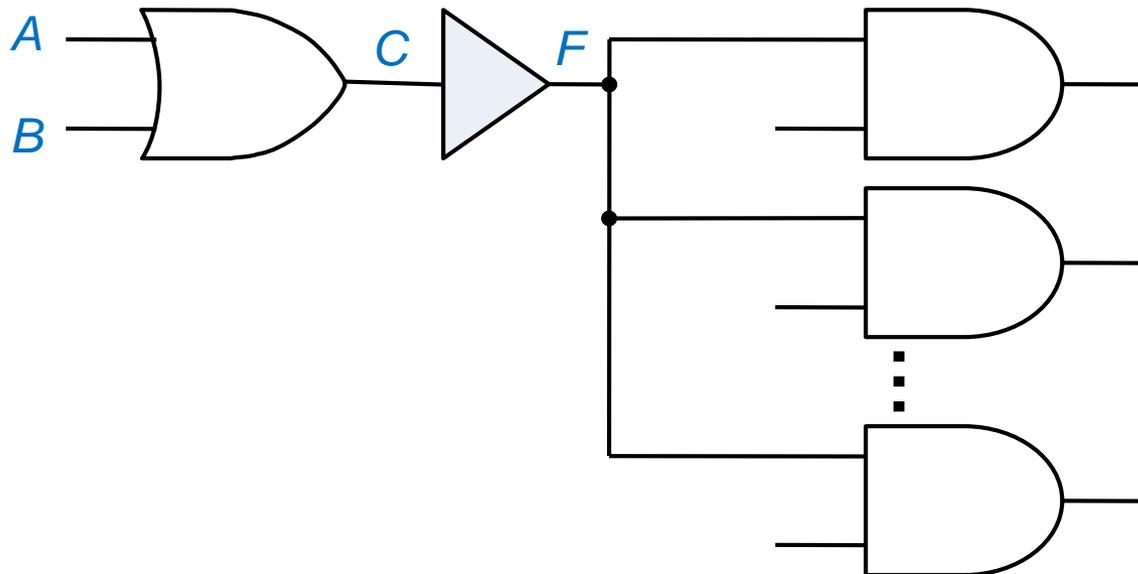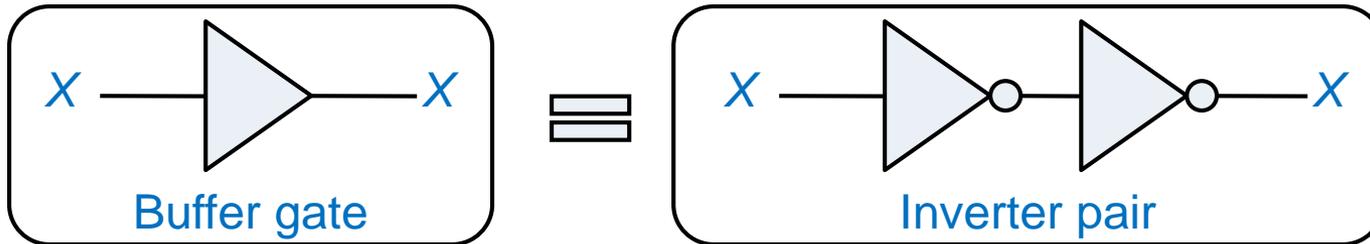


# Three-State Buffers

- Three-state (tri-state) buffers: permits gate outputs to be connected together

- Symbol

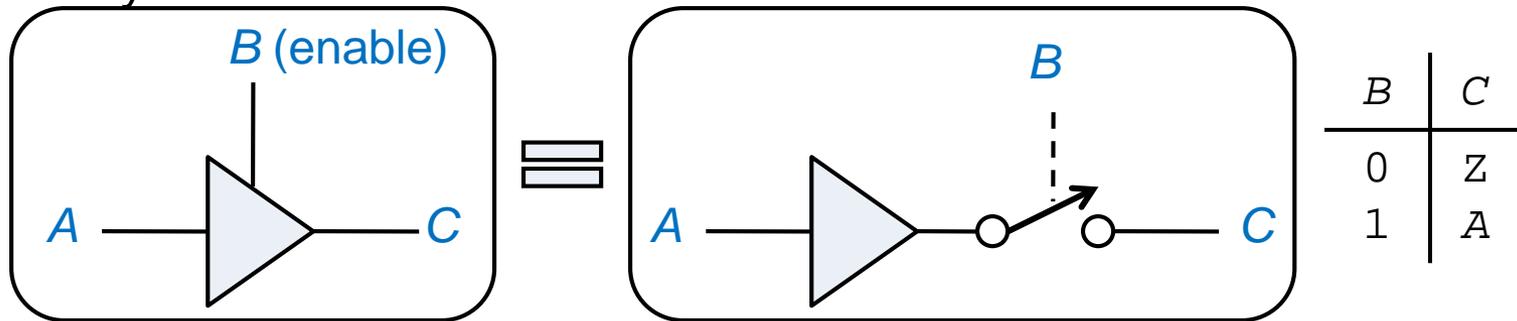


- 4 variants

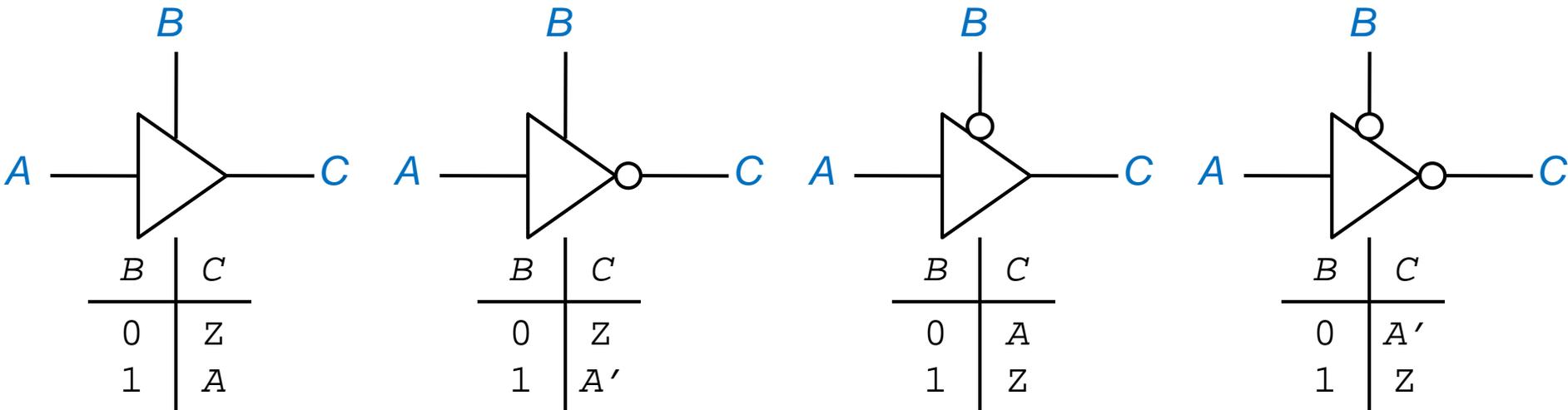


# Application (1/2)

## □ Data selection

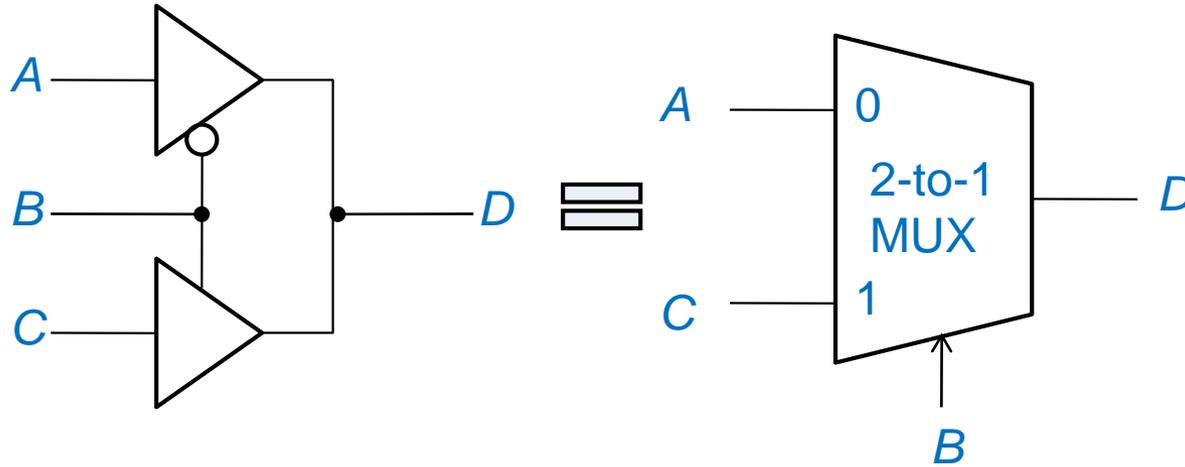

## □ Circuit with 2 tri-state buffers

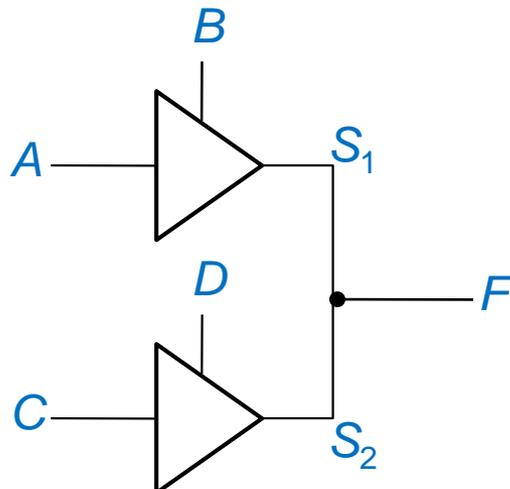


outputs of buffers


	X	0	1	Z
X	X	X	X	X
0	X	0	X	0
1	X	X	1	1
Z	X	0	1	Z

# Application (2/2)

## Tri-state bus

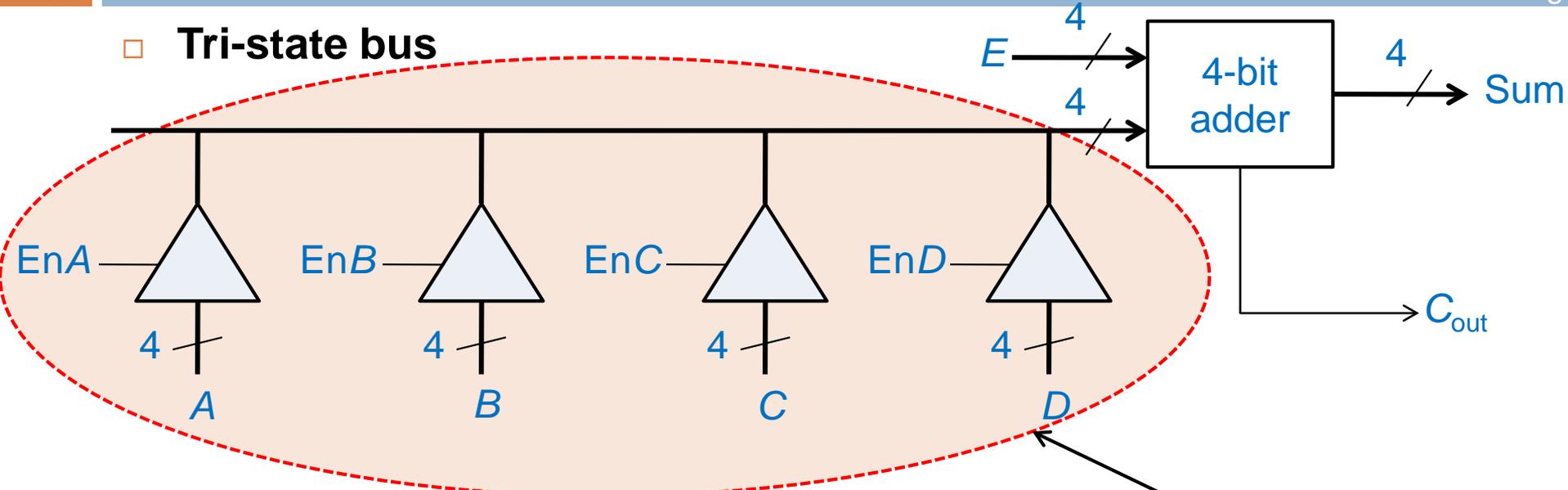

## Bi-directional I/O pin

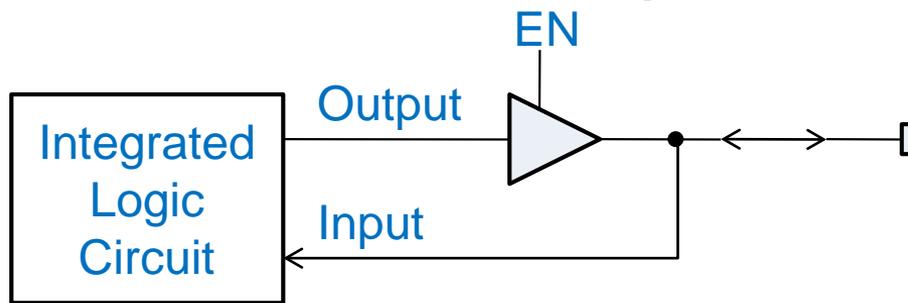

**Key:**  
{EnA, EnB, EnC, EnD} must be **exclusive**  
(Only 1 active at a time)


**Bi-directional input-output pin:**  
The same pin can be used as an **input** pin and as an **output** pin, but not both at the same time

14

# Decoders and Encoders
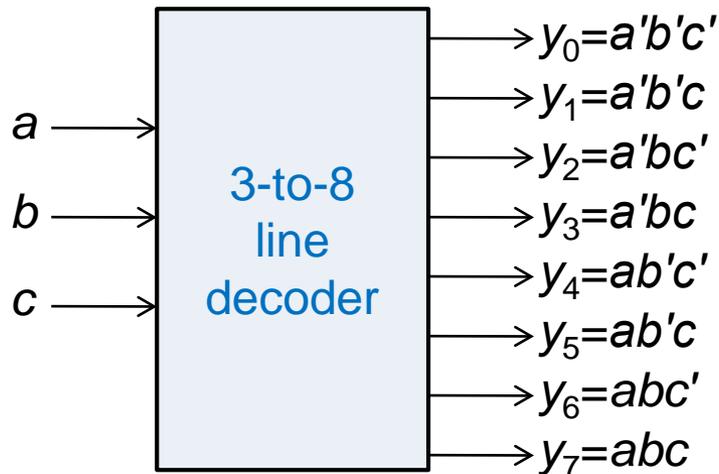
# Decoders

- **Decoder:** generates all of the minterms of input variables
  - Exactly one output line corresponds to one input combination
  - Symbol
  - Truth table




	$a$	$b$	$c$	$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
$m_0$	0	0	0	1	0	0	0	0	0	0	0
$m_1$	0	0	1	0	1	0	0	0	0	0	0
$m_2$	0	1	0	0	0	1	0	0	0	0	0
$m_3$	0	1	1	0	0	0	1	0	0	0	0
$m_4$	1	0	0	0	0	0	0	1	0	0	0
$m_5$	1	0	1	0	0	0	0	0	1	0	0
$m_6$	1	1	0	0	0	0	0	0	0	1	0
$m_7$	1	1	1	0	0	0	0	0	0	0	1

- General  $n$ -to- $2^n$  decoder
  - Noninverted outputs:  $y_i = m_i$ ,  $i = 0$  to  $2^n - 1$
  - Inverted outputs:  $y_i = m_i' = M_i$ ,  $i = 0$  to  $2^n - 1$

# Example: 4-to-10 Line Decoder


Block diagram

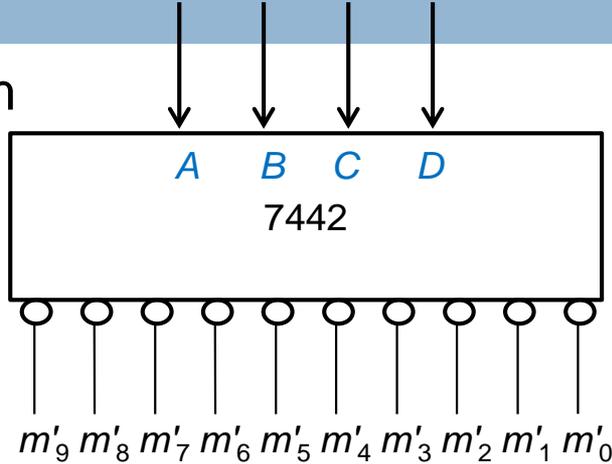

Truth table

BCD input	Decimal output
ABCD	0123456789
0000	0111111111
0001	1011111111
0010	1101111111
0011	1110111111
0100	1111011111
0101	1111101111
0110	1111110111
0111	1111111011
1000	1111111101
1001	1111111110
1010	1111111111
1011	1111111111
1100	1111111111
1101	1111111111
1110	1111111111
1111	1111111111

Logic diagram

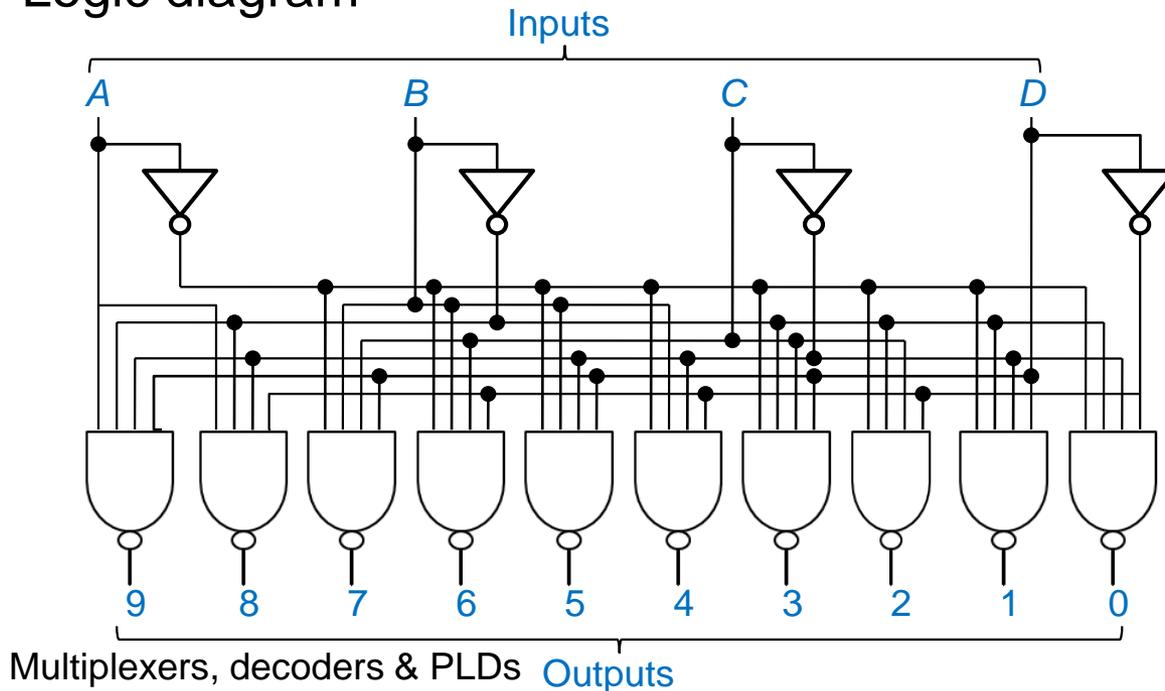


# Application: Realizing $n$ -Variable Functions

17


© Iris H.-R. Jiang

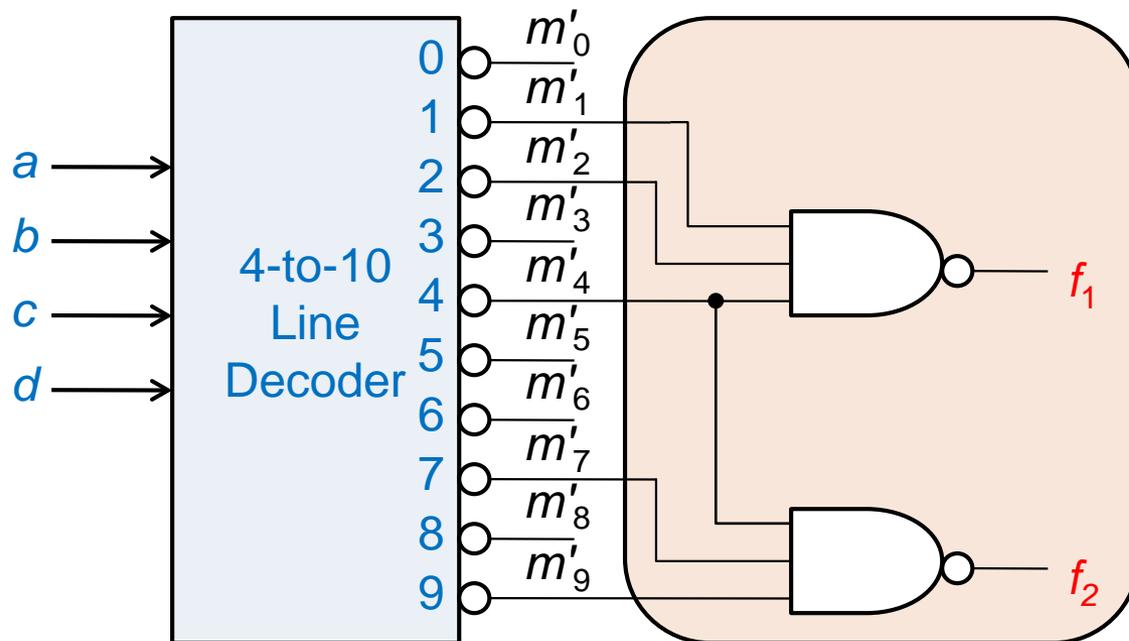- **Exactly one output line corresponds to one minterm**
  - $\Rightarrow$  Realize  $n$ -variable functions by **OR**ing selected minterm outputs from a decoder
  - e.g.,  $f_1 = \Sigma m(1, 2, 4)$ ,  $f_2 = \Sigma m(4, 7, 9)$


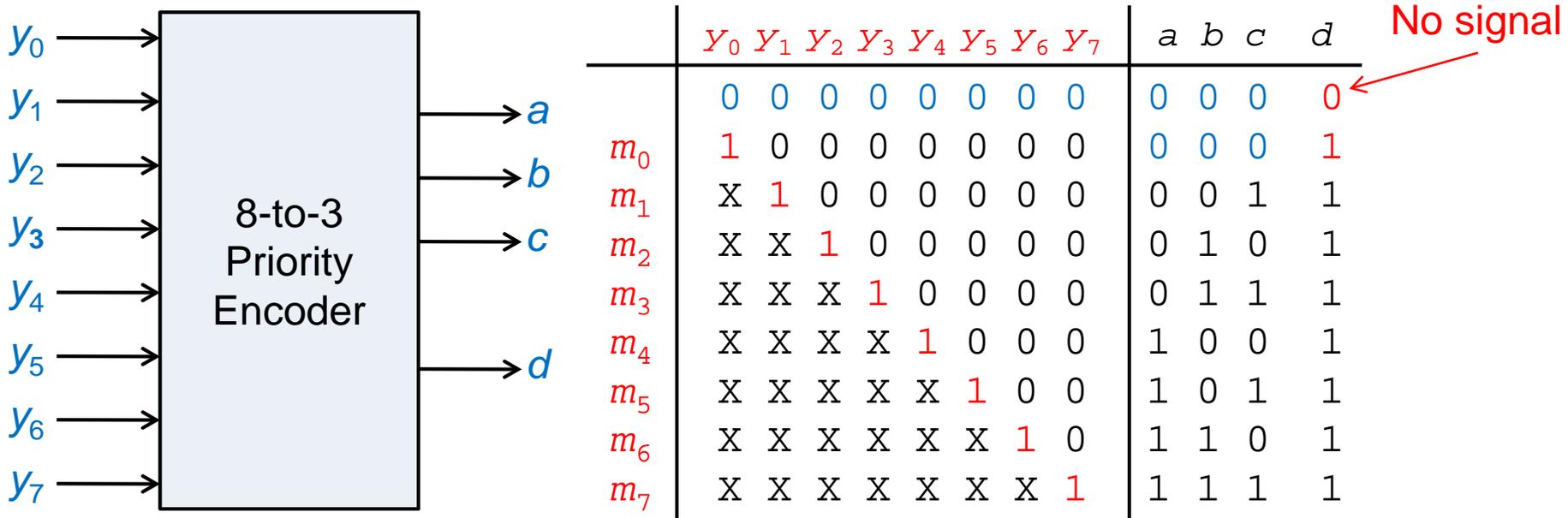
# Encoders

- **Encoder:** performs the inverse function of a decoder
  - ▣ If  $y_i = 1$ ,  $abc$  outputs represent a binary number equal to  $i$
  - ▣ If **more than one** input can be 1 at a time, use a priority scheme




19

# Read-Only Memories

## ROM
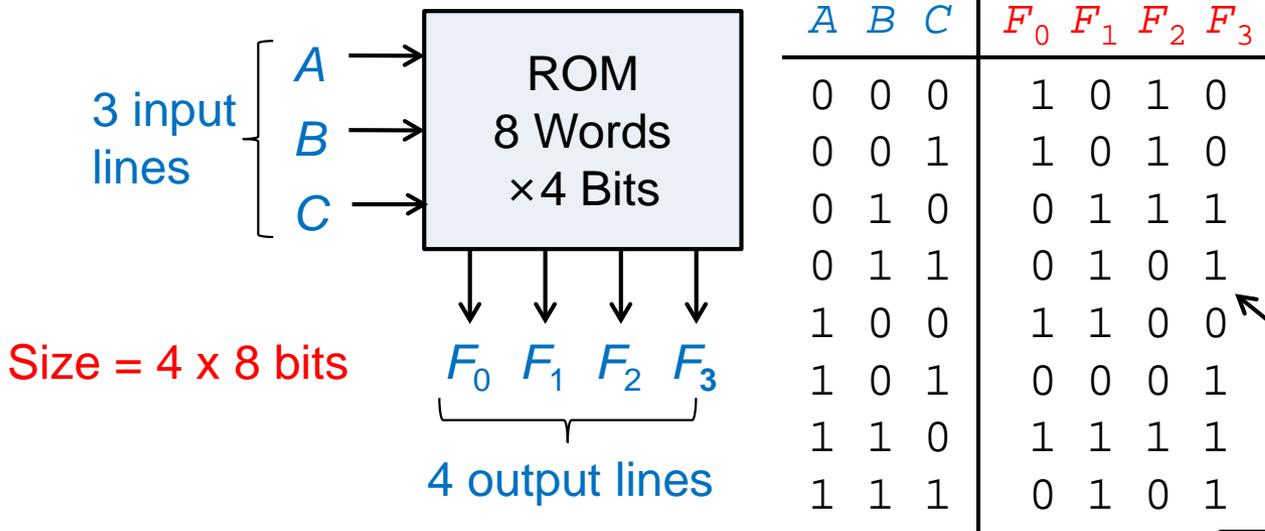
# Read-Only Memories (1/3)


- A **read-only memory (ROM)**: stores an array of binary data
  - ▣ Stored data cannot be changed
  - ▣ e.g., 8-word × 4-bit ROM: each word is 4-bit, total 8 words
    - Input:  $ABC$ : 3-bit lines can index  $2^3$  values (0~7 address)
    - Output:  $F_0F_1F_2F_3$ : each output pattern is called a word



typical data stored in ROM  
( $2^3$  words of 4 bits each)

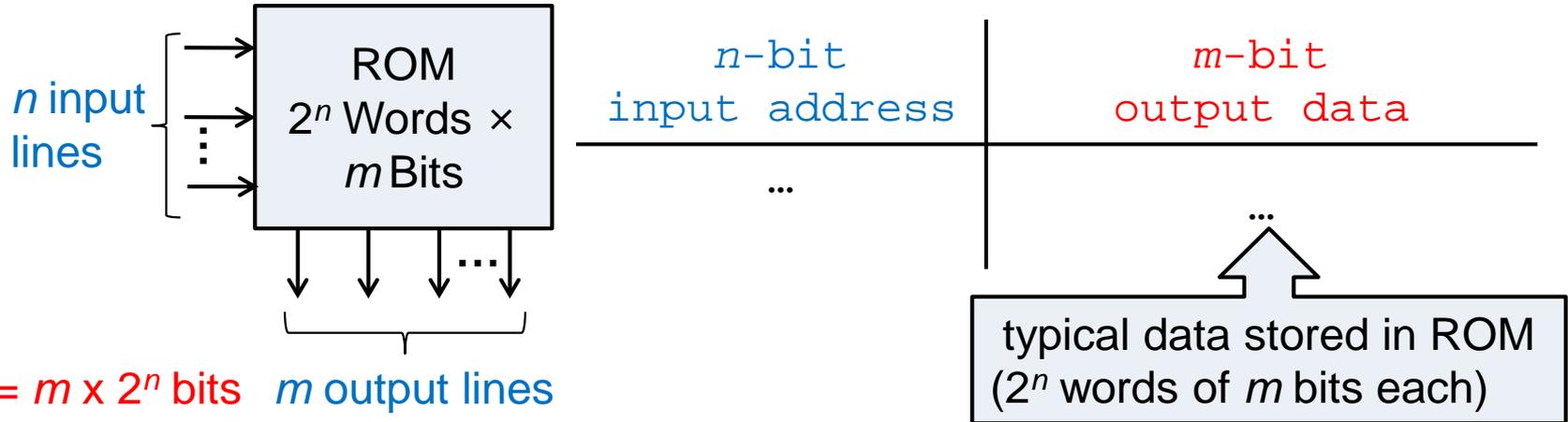
# ROM (2/3)

- Generalized form:  $2^n$  Words  $\times$   $m$  Bits ROM ( $n$ -inputs  $m$ -outputs)



Size =  $m \times 2^n$  bits  $m$  output lines


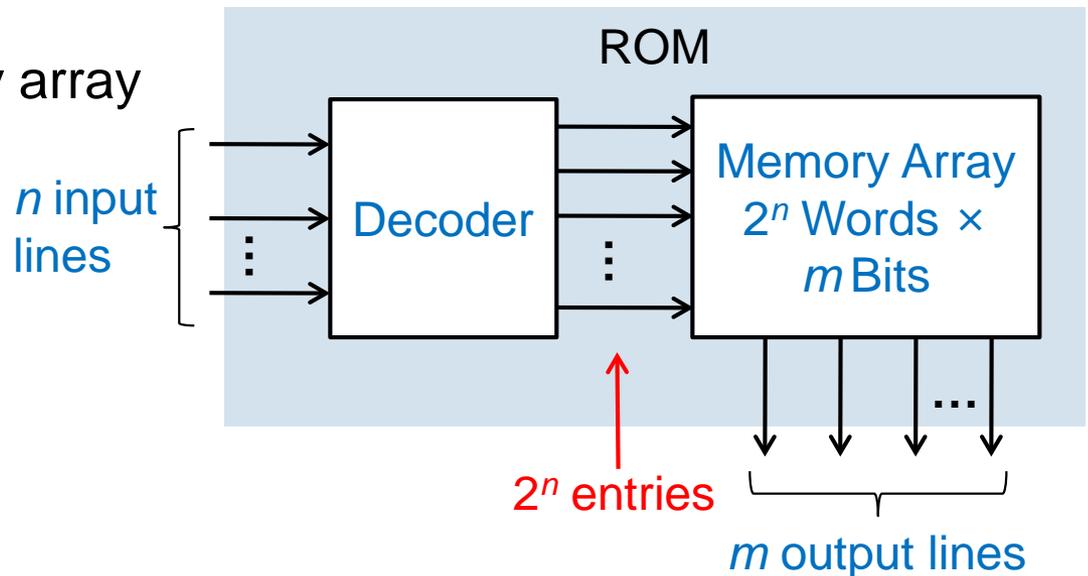
- Basic ROM structure
  - A decoder + memory array



# ROM (3/3)

The contents of a ROM are usually specified by a truth table


<i>ABC</i>	<i>F<sub>0</sub></i>	<i>F<sub>1</sub></i>	<i>F<sub>2</sub></i>	<i>F<sub>3</sub></i>
000	1	0	1	0
001	1	0	1	0
010	0	1	1	1
011	0	1	0	1
100	1	1	0	0
101	0	0	0	1
110	1	1	1	1
111	0	1	0	1

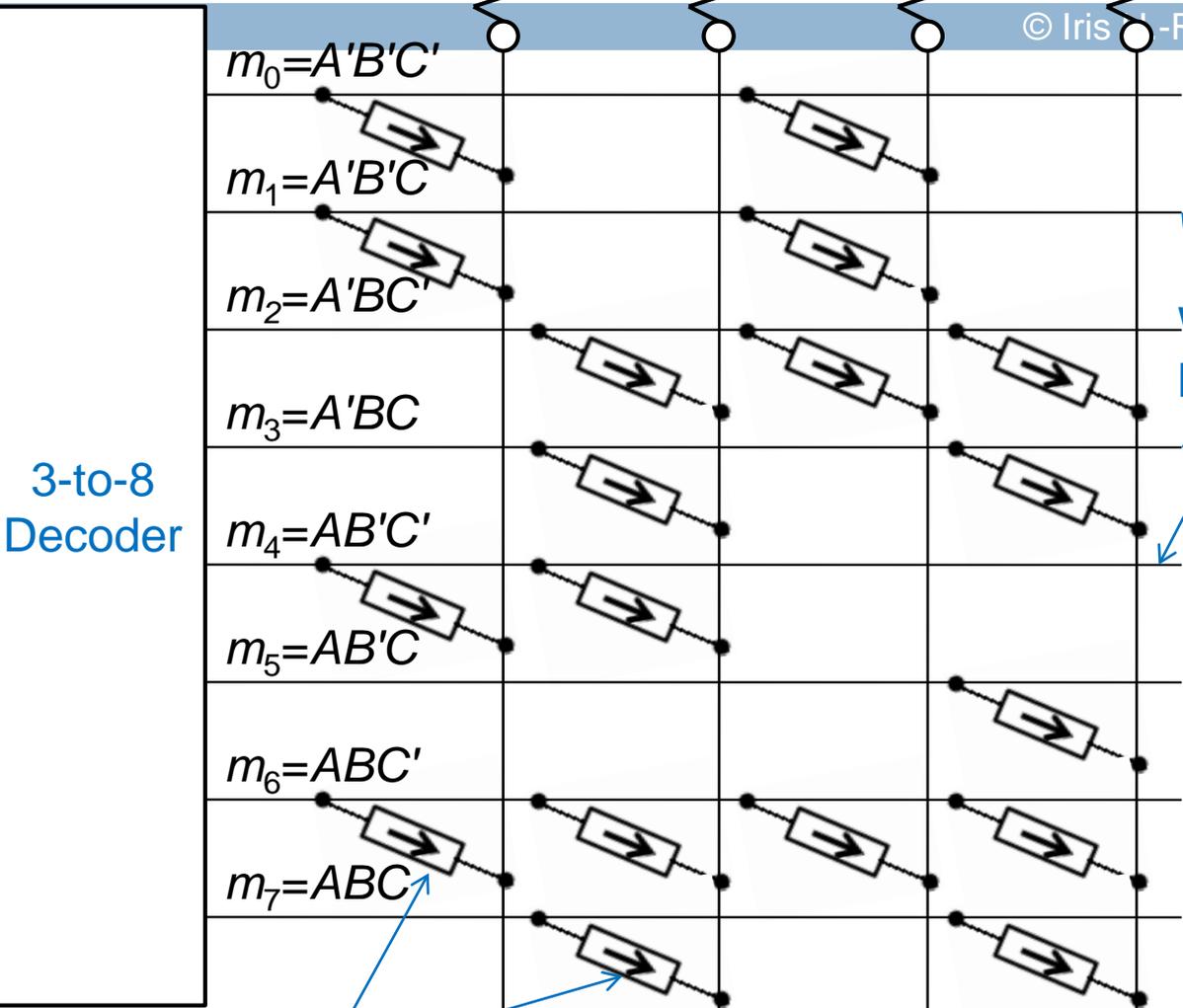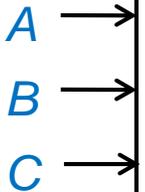

Word lines

Switching element

Output lines

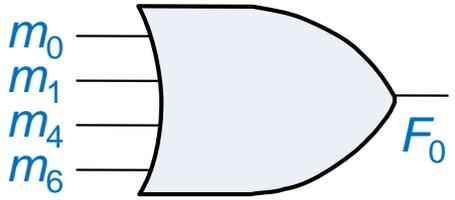


# Application: Multi-Output Combinational Ckts

□ e.g., hex to ASCII code converter

Hex	$A_6A_5A_4A_3A_2A_1A_0$
0	011 0000
1	011 0001
2	011 0010
3	011 0011
4	011 0100
5	011 0101
6	011 0110
7	011 0111
8	011 1000
9	011 1001
A	100 0001
B	100 0010
C	100 0011
D	100 0100
E	100 0101
F	100 0110

$A_5 = A_4$   
 $A_6 = A_4'$

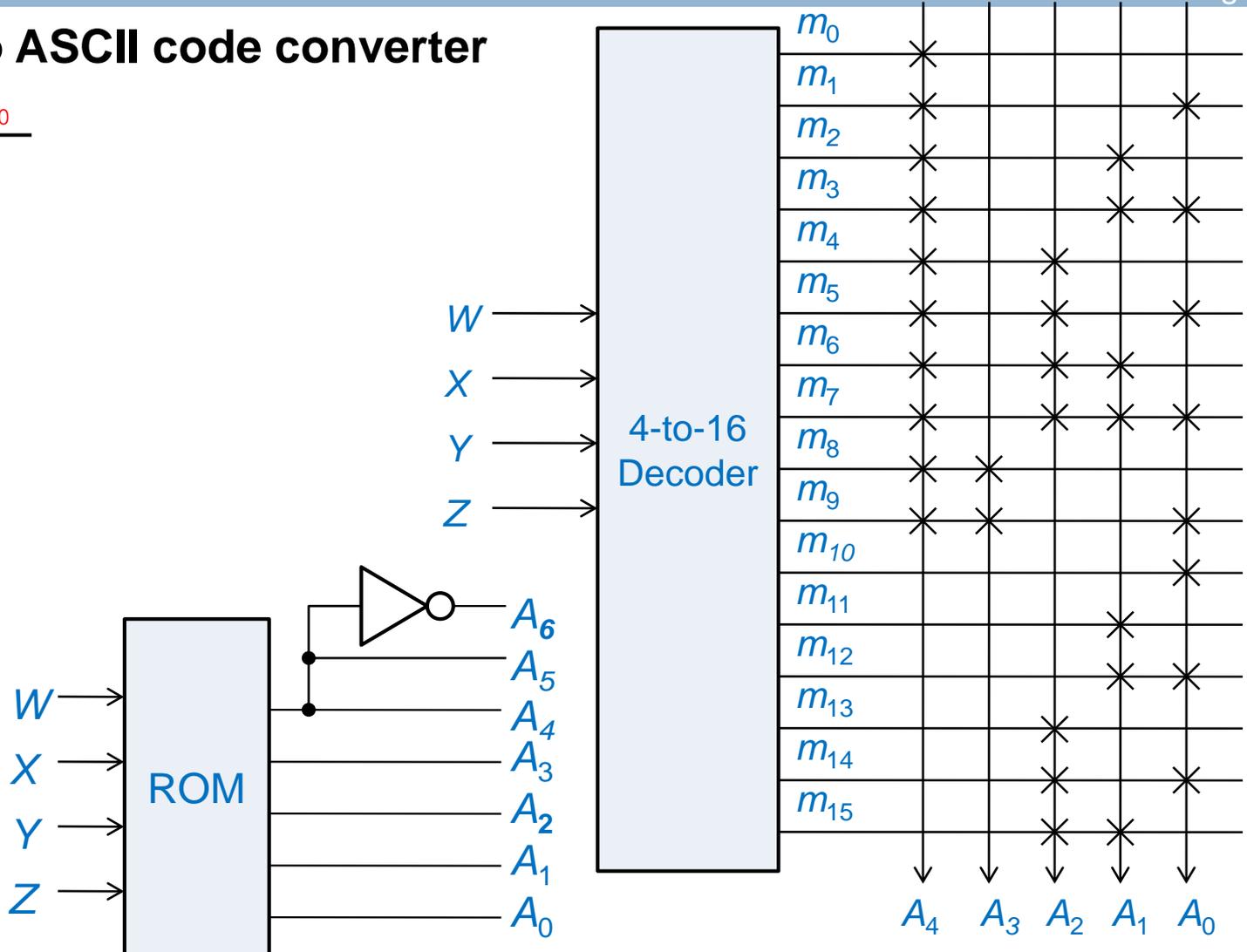

# Three Common Types of ROMs

- **Mask-programmable ROMs**
  - ▣ Use mask to program
    - Include/omit switching elements
- **Programmable ROMs (PROMs)**
  - ▣ Program once
- **Electrically erasable programmable ROMs (EEPROMs)**
  - ▣ Can reprogram 100—1000 times

25



# Programmable Logic Devices

**PLD**

**PLA / PAL**
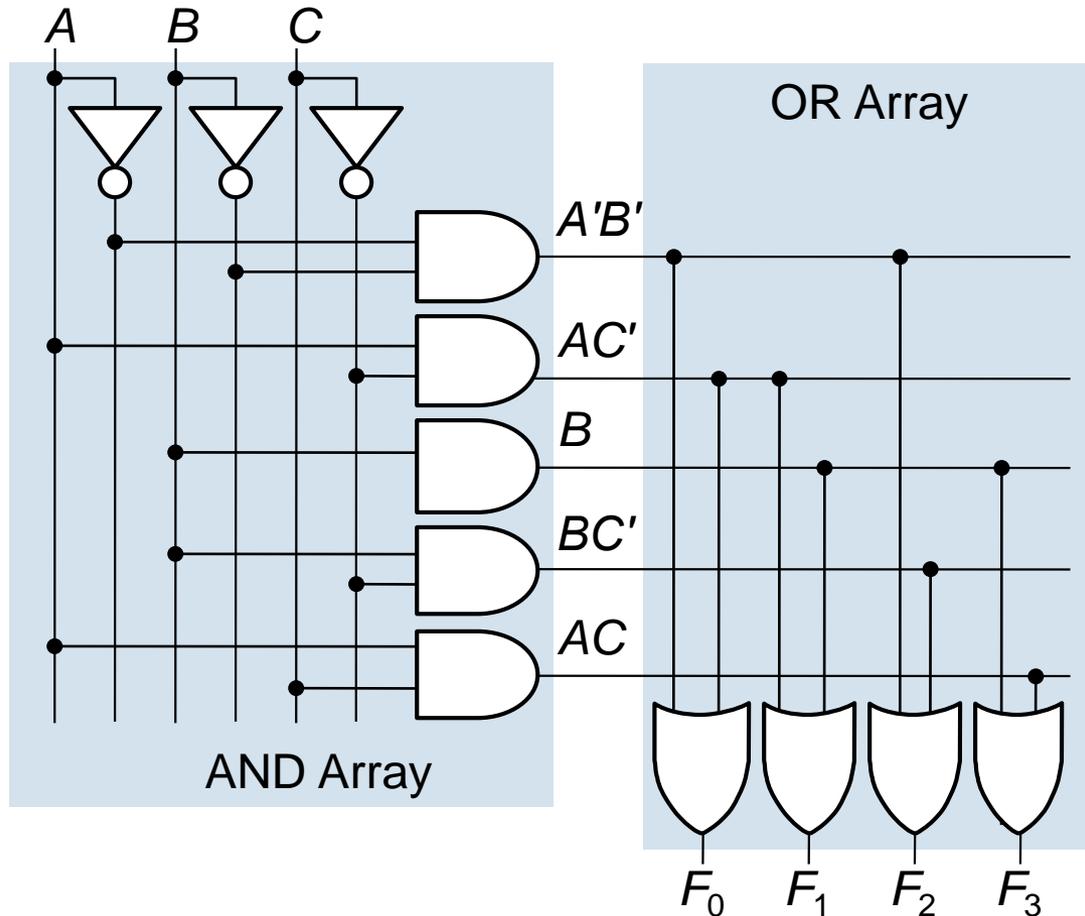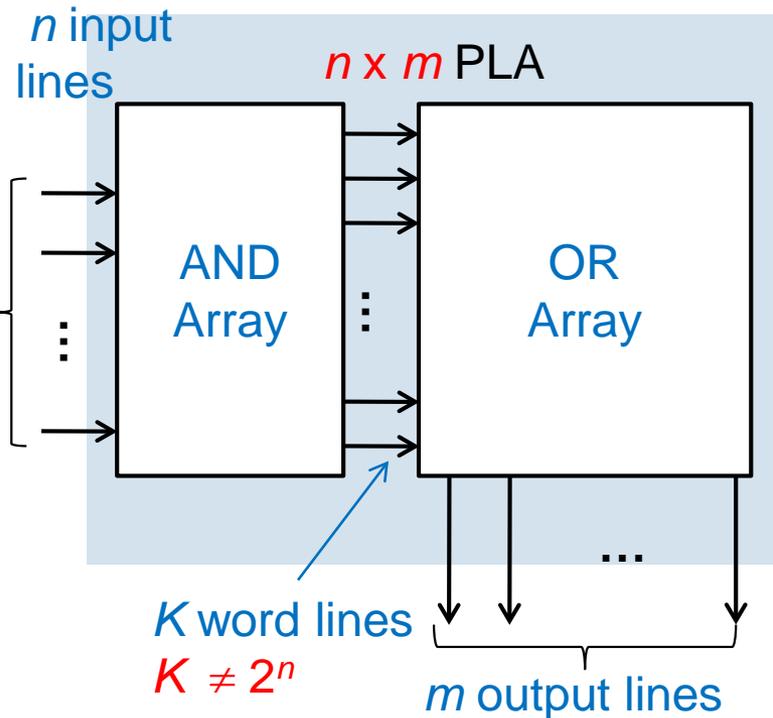
# Programmable Logic Arrays (1/3)



- Programmable logic arrays (PLAs): 2-level SOP implementation
  - AND plane generates product terms
  - OR plane sums the product terms



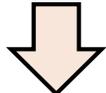
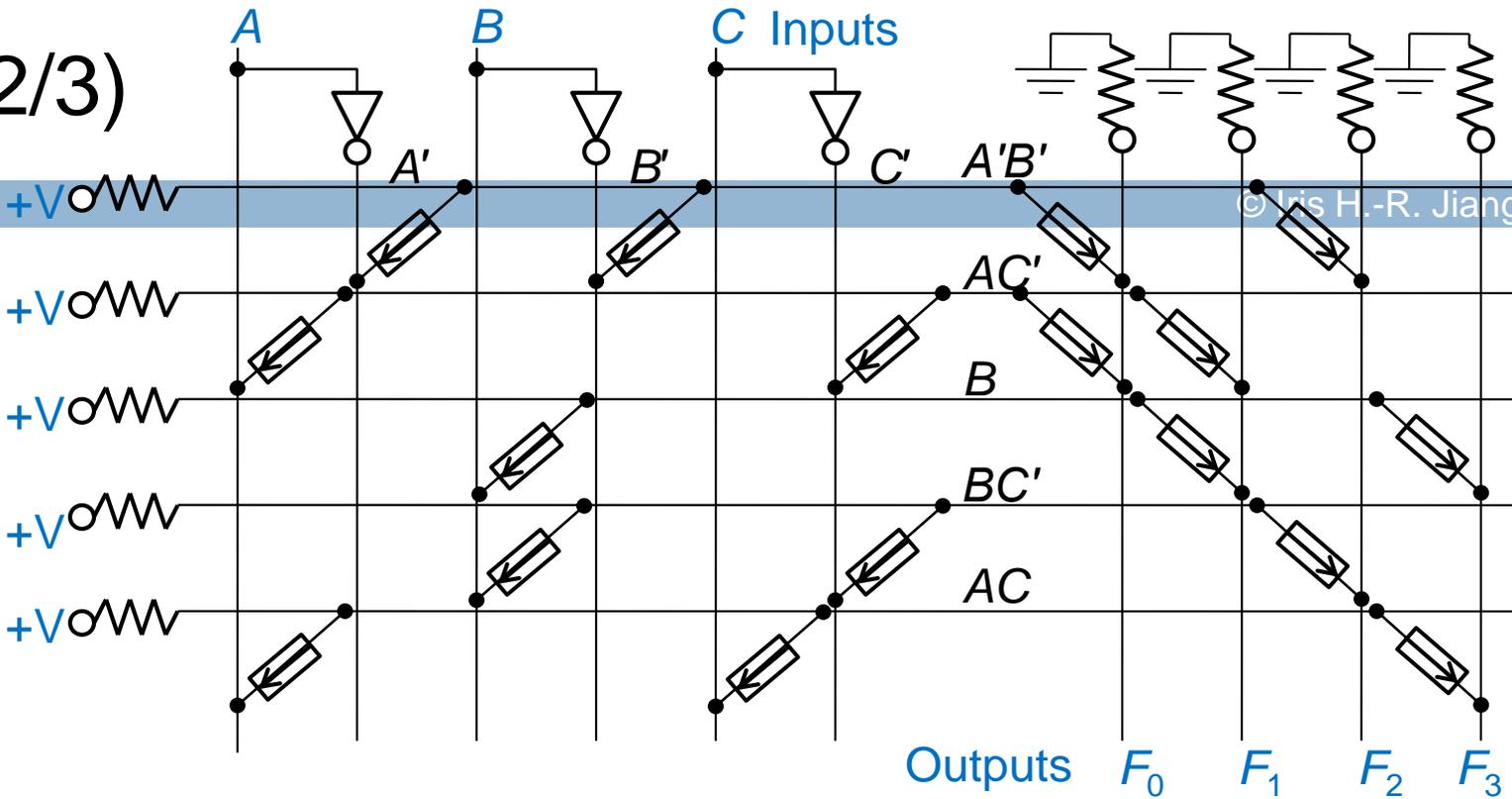
# PLA (2/3)

□ e.g.,

$$\begin{aligned}
 F_0 &= A'B' + AC' \\
 F_1 &= AC' + B \\
 F_2 &= A'B' + BC' \\
 F_3 &= B + AC
 \end{aligned}$$



Product term	Inputs			Outputs			
	A	B	C	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
A'B'	0	0	-	1	0	1	0
AC'	1	-	0	1	1	0	0
B	-	1	-	0	1	0	1
BC'	-	1	0	0	0	1	0
AC	1	-	1	0	0	0	1

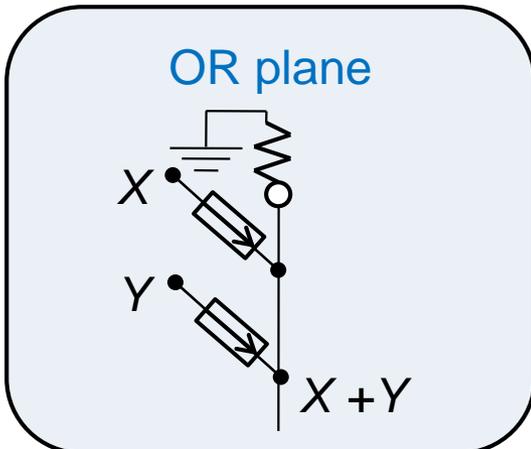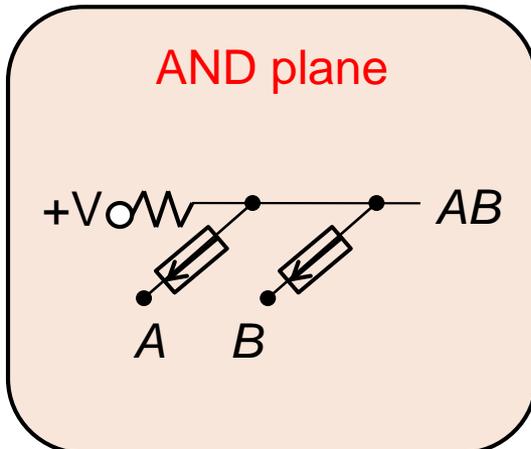

# PLA (3/3)


□ e.g.,

- $f_1(a, b, c, d) = \Sigma m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$
- $f_2(a, b, c, d) = \Sigma m(2, 3, 5, 6, 7, 10, 11, 14, 15)$
- $f_3(a, b, c, d) = \Sigma m(6, 7, 8, 9, 13, 14, 15)$

□ Minimize using K-map


- $f_1 = abd + a'bd + b'c + ab'c'$
- $f_2 = c + a'bd$
- $f_3 = bc + ab'c' + abd$

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	$f_1$	$f_2$	$f_3$
0	1	-	1	1	1	0
1	1	-	1	1	0	1
1	0	0	-	1	0	1
-	0	1	-	1	0	0
-	-	1	-	0	1	0
-	1	1	-	0	0	1

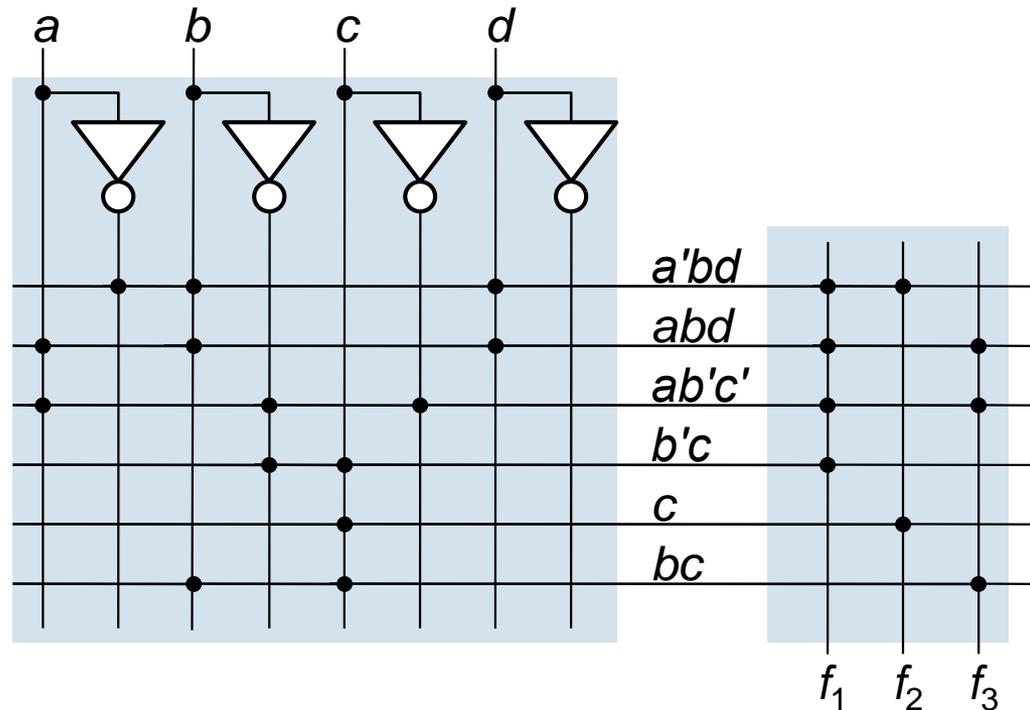
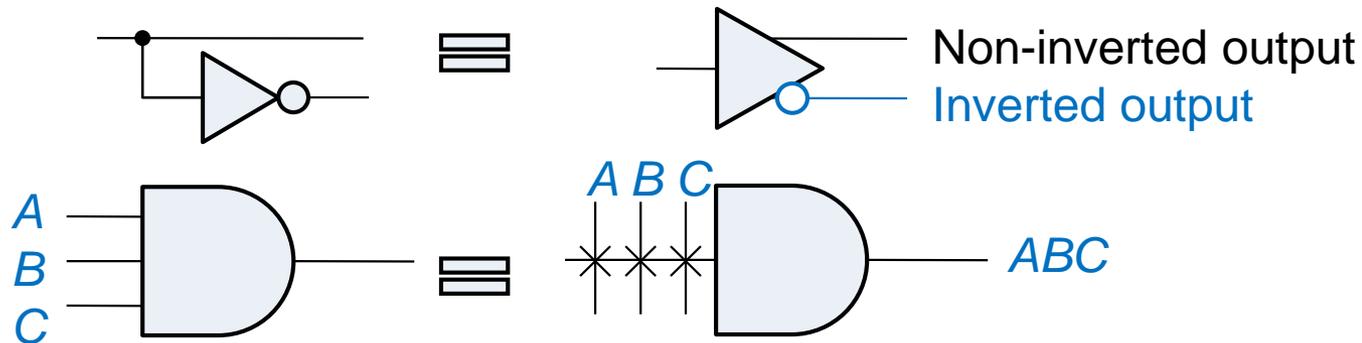
# Programmable Array Logic (1/2)



- **Programmable array logic (PAL):** A special case of PLA
  - AND array: programmable
  - OR array: **fixed**
  - Symbol



# PAL (2/2)

30


- Fixed OR array

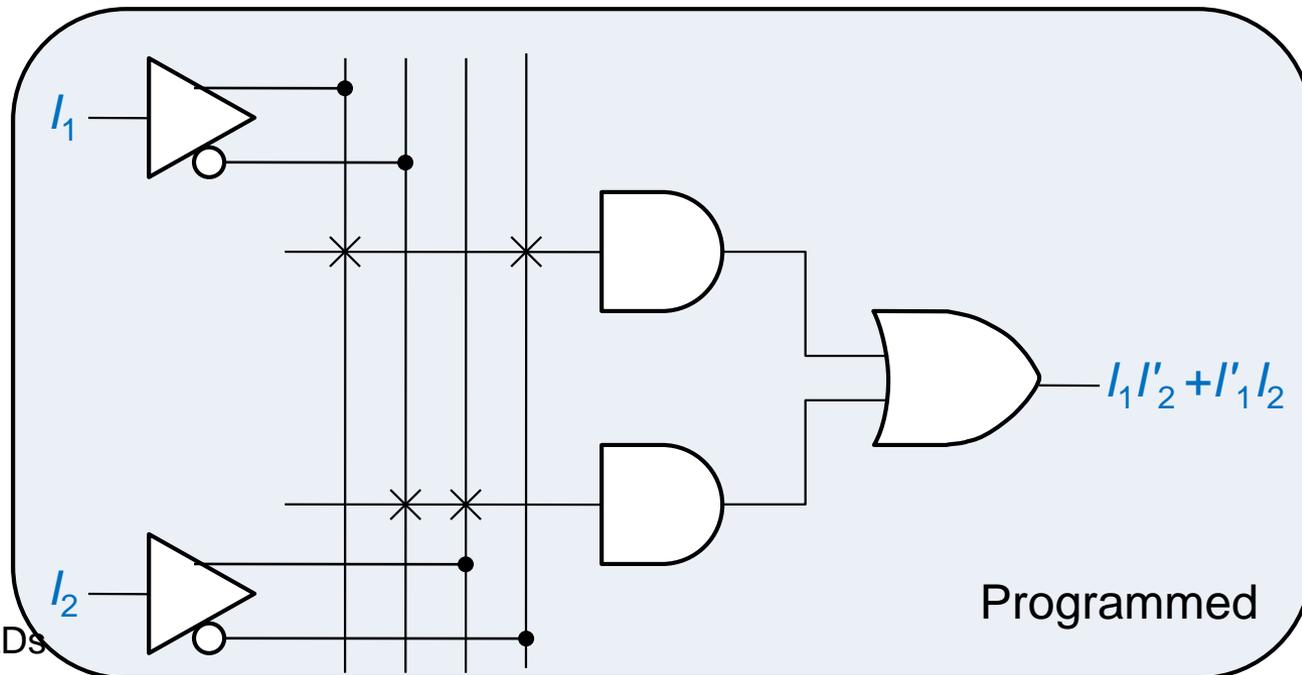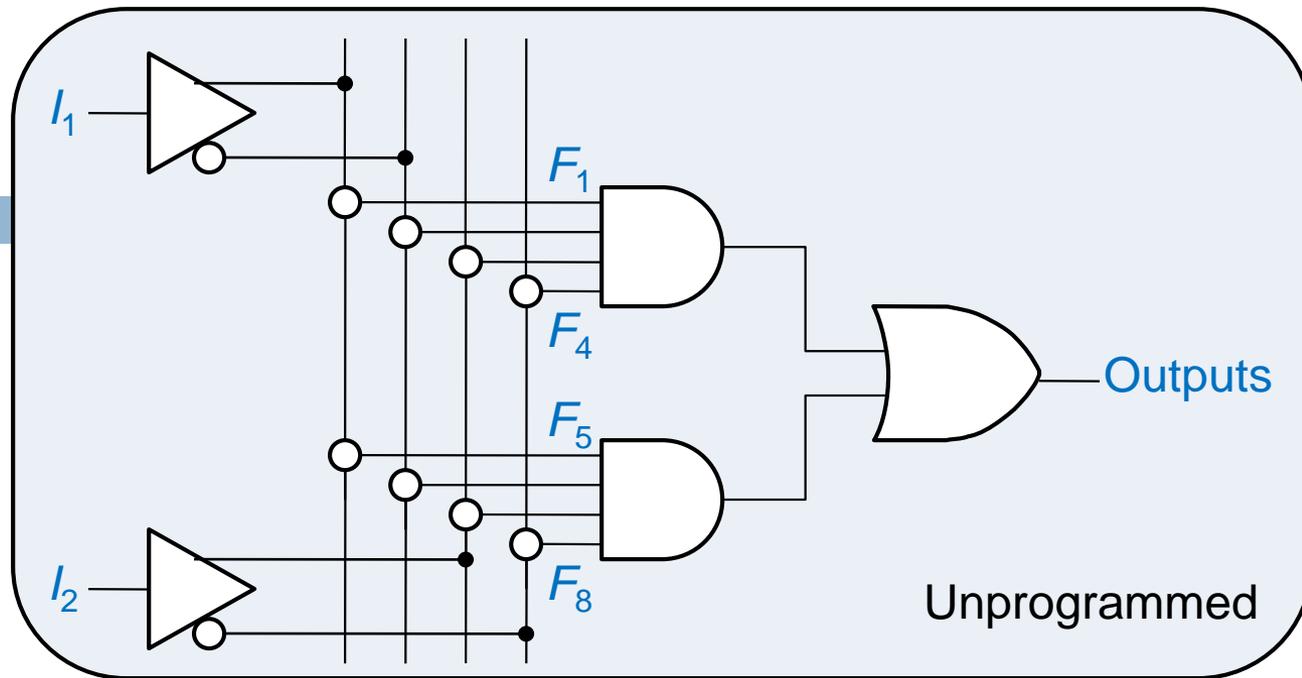

# Application: Full Adder

31

H.-R. Jiang

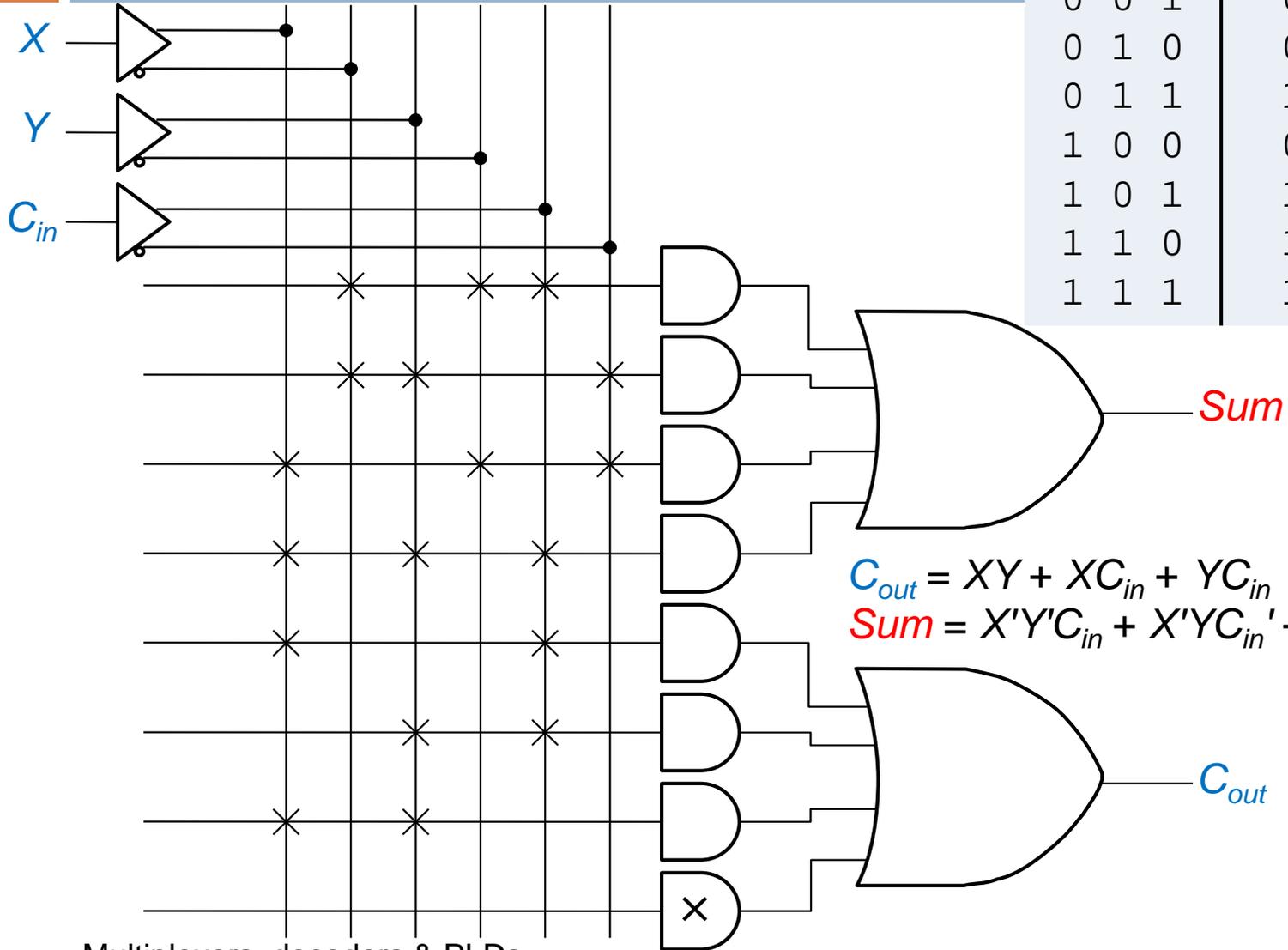

$X$	$Y$	$C_{in}$	$C_{out}$	$Sum$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$Sum = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$$


32

# Complex Programmable Logic Devices

## CPLD
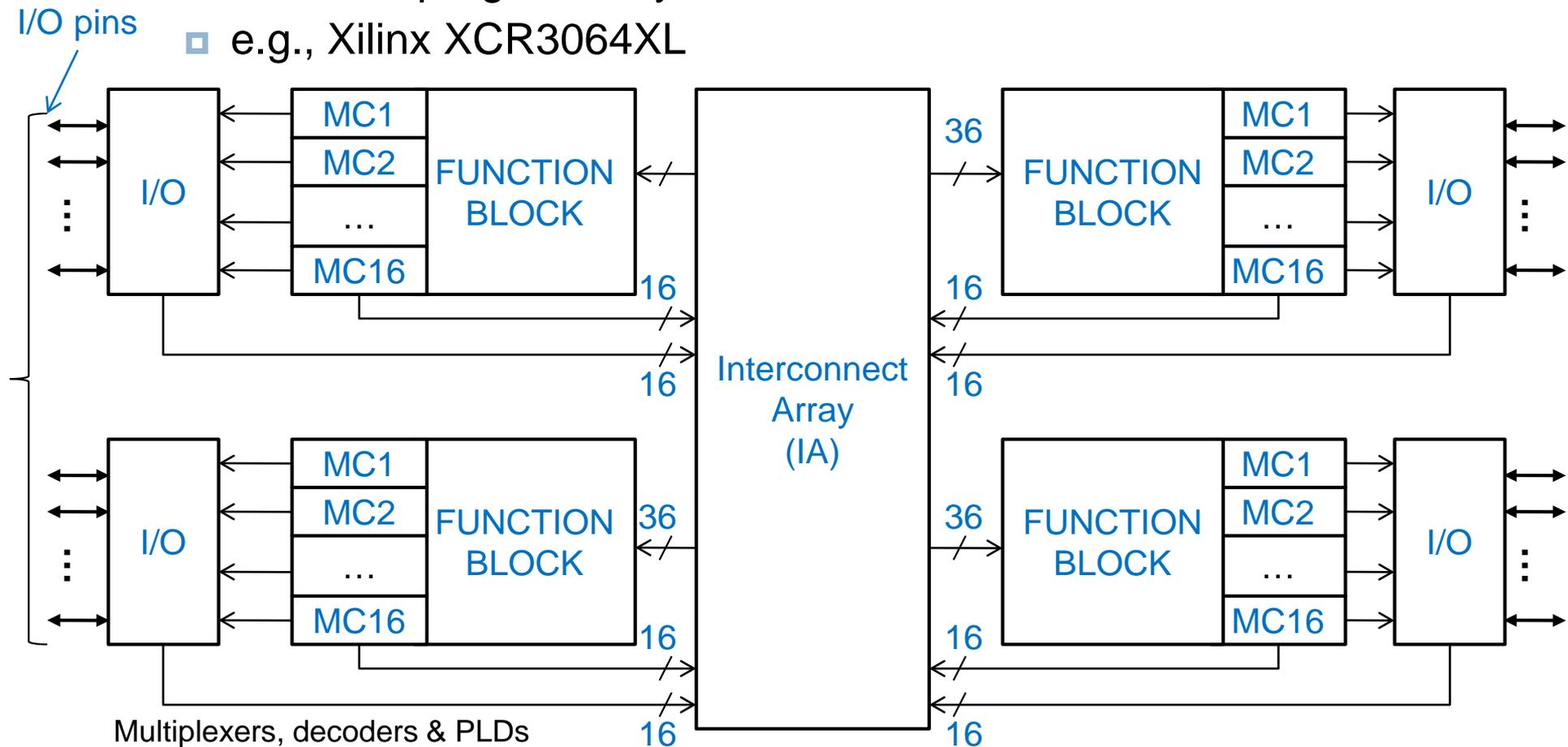
# Complex Programmable Logic Devices (1/2)

- Complex programmable logic device (**CPLD**): integrate and interconnect many PALs and PLAs on a single chip
  - Tools will program for you
  - e.g., Xilinx XCR3064XL




# CPLD (2/2)

## □ CPLD function block and macrocell

- ▣ A simplified version of XCR3064XL

36 Inputs from IA

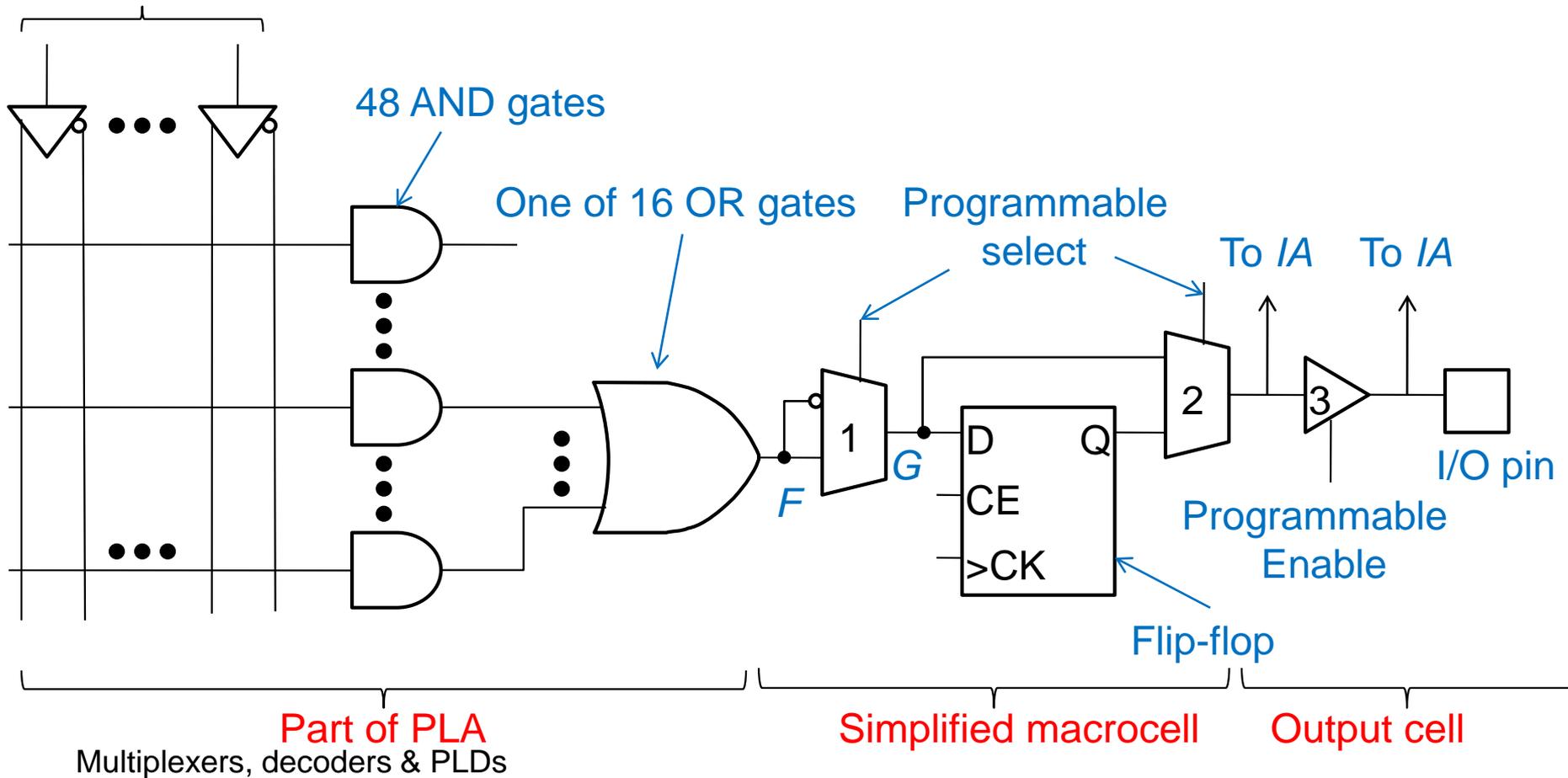


35

# Field Programmable Gate Arrays

## FPGA

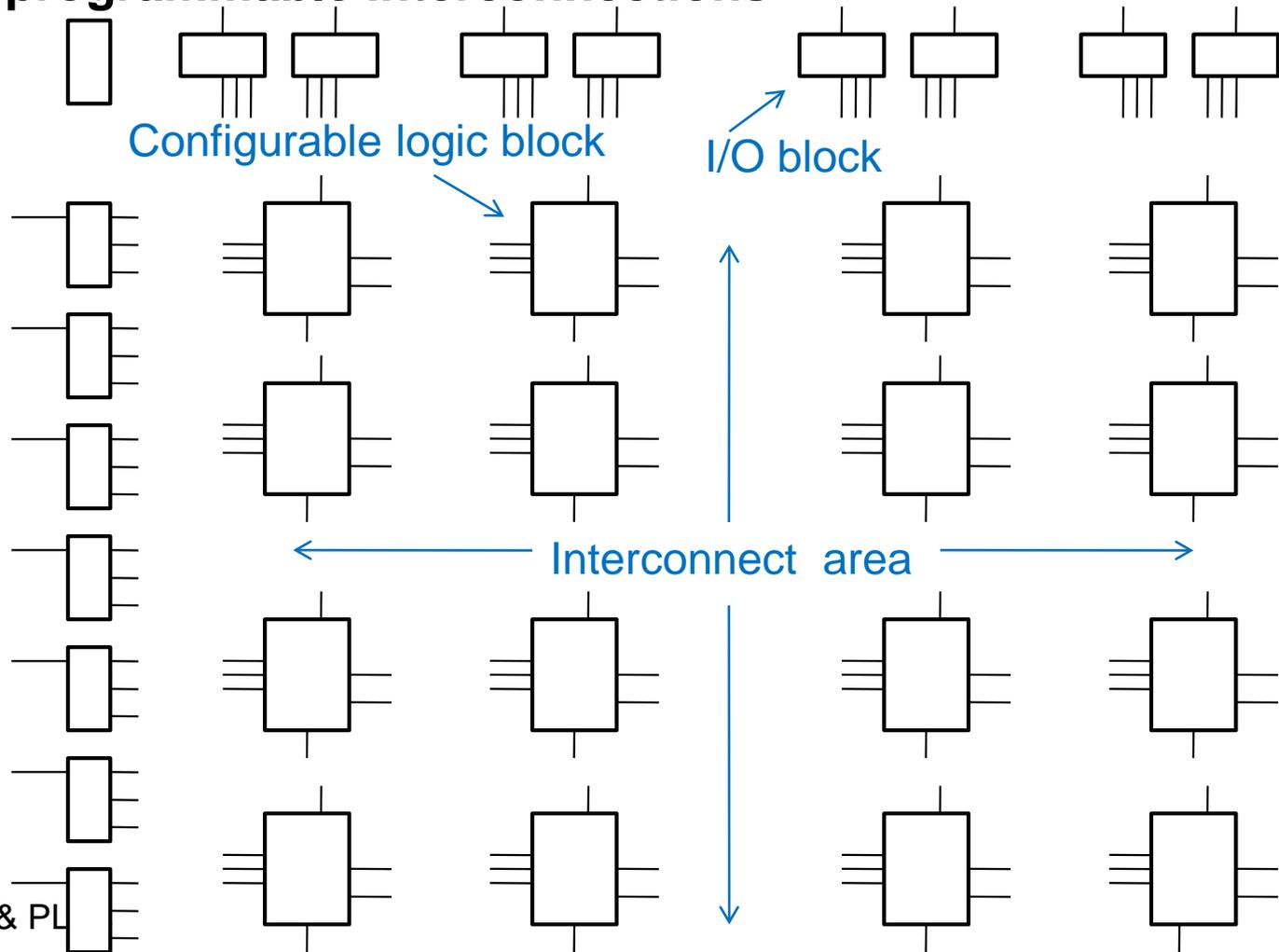
# Field Programmable Gate Arrays

- Field programmable gate arrays (**FPGA**): an array of identical logic cells + programmable interconnections




Multiplexers, decoders & PL
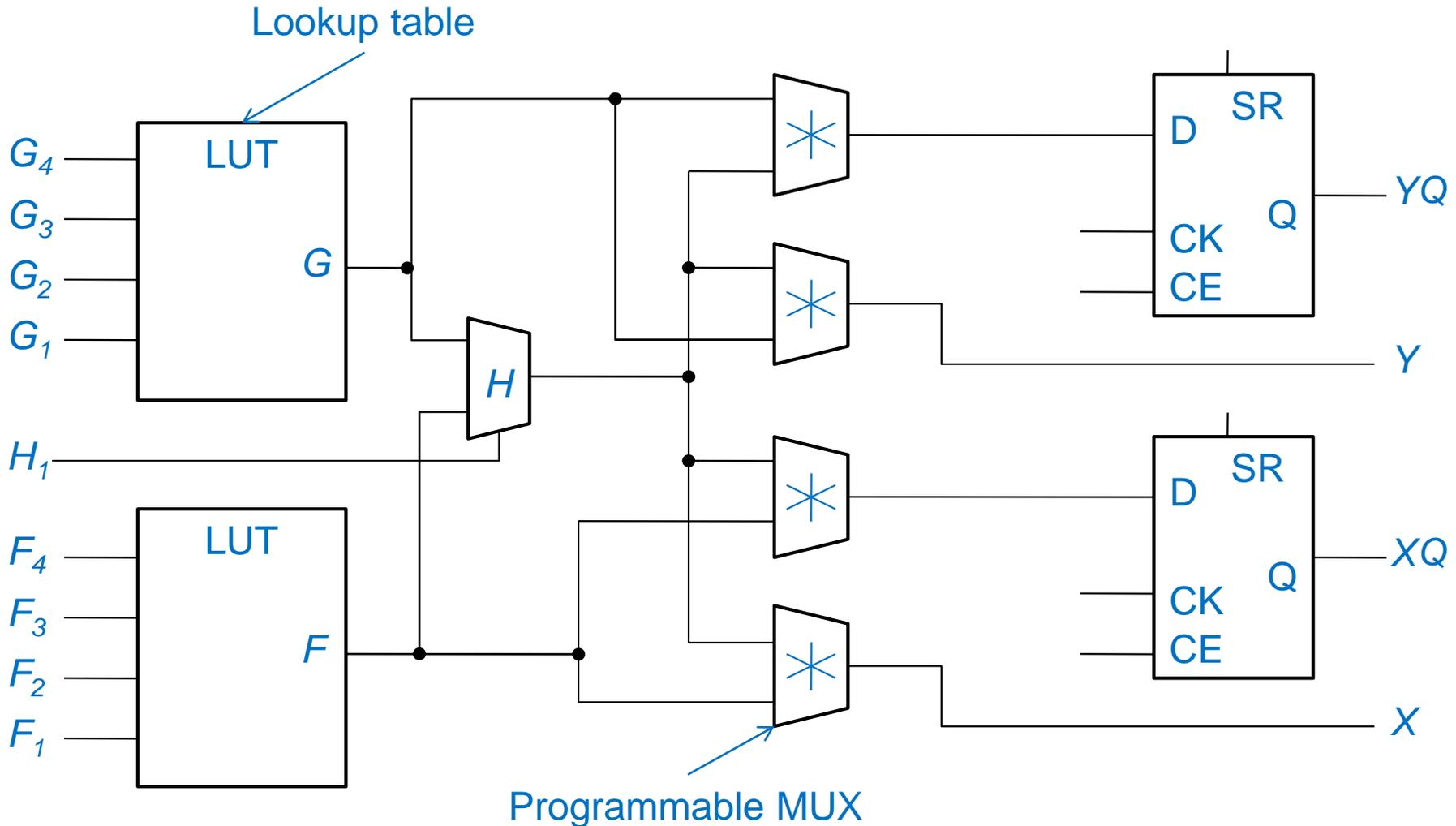
# Simplified Configurable Logic Block (CLB)



# Implementation of a Lookup Table (LUT)

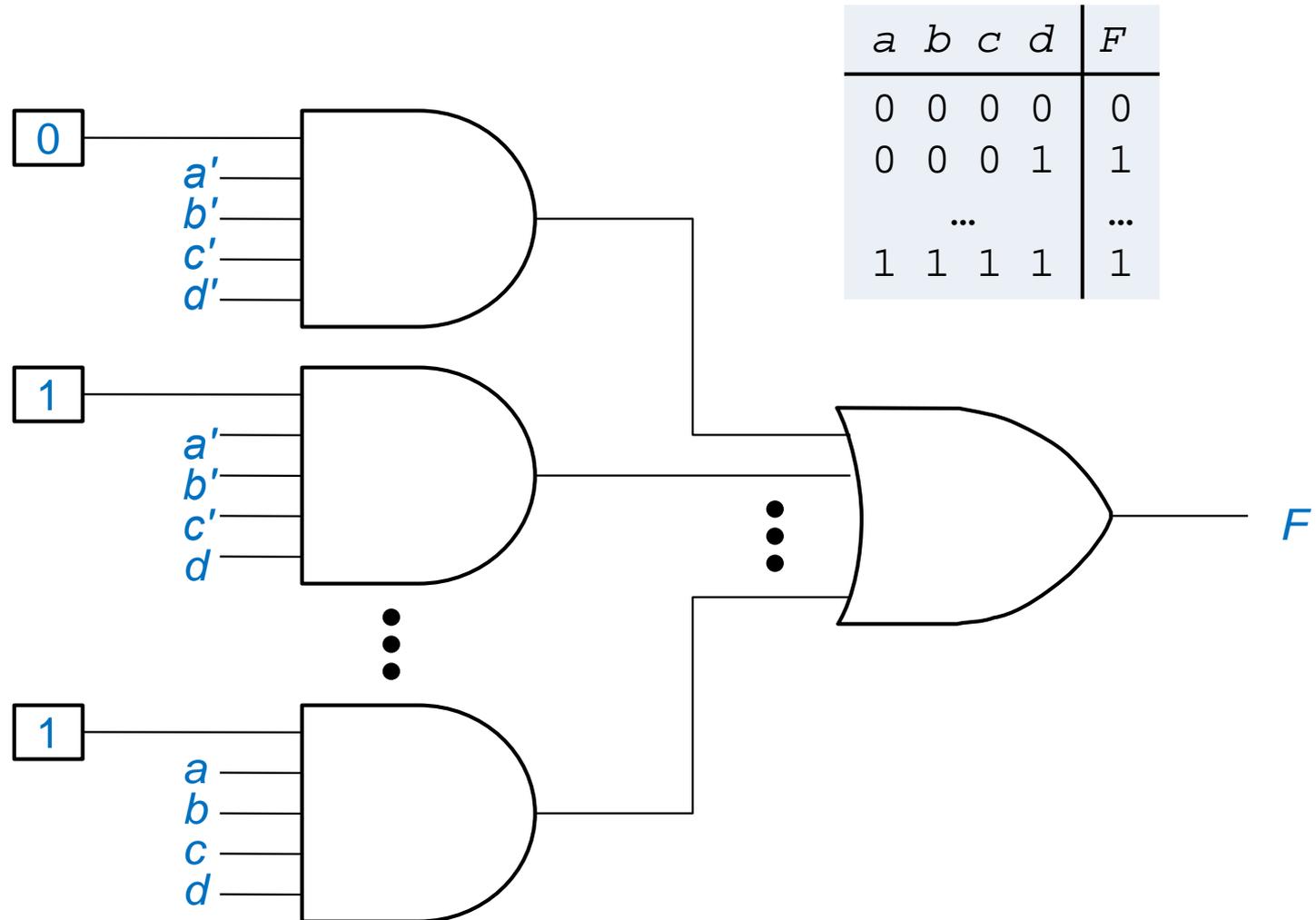


# Realization with Function Generators


## Realize a 5-variable function with 4-variable FGs:

- ▣  $F(a, b, c, d, e) = a'F(0, b, c, d, e) + aF(1, b, c, d, e) = a'F_0 + aF_1$
- ▣ 2 4-variable FGs + 2-to-1 MUX (controlled by a)

## Q: 6-variable function?

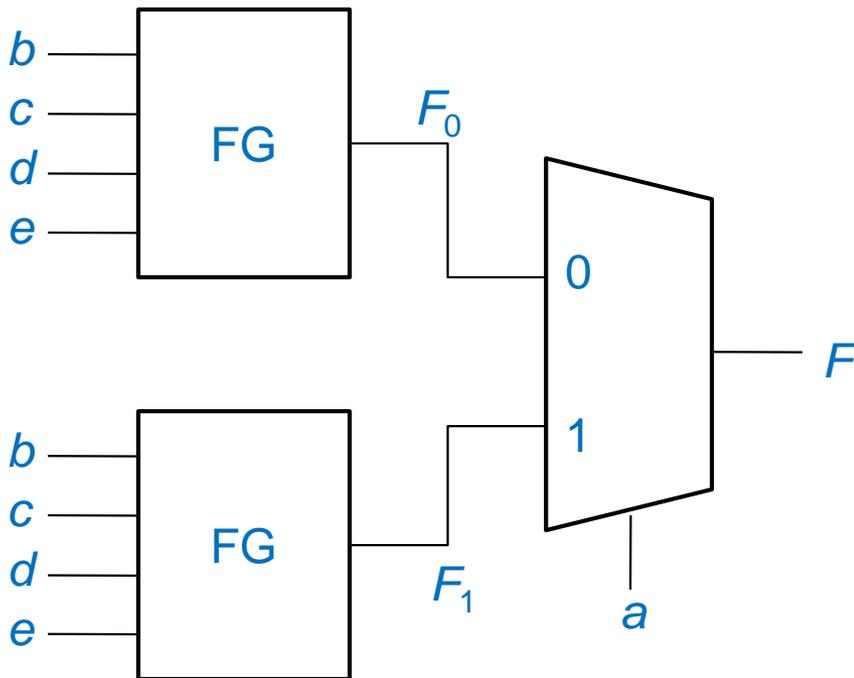

Multiplexers, decoders & PLDs

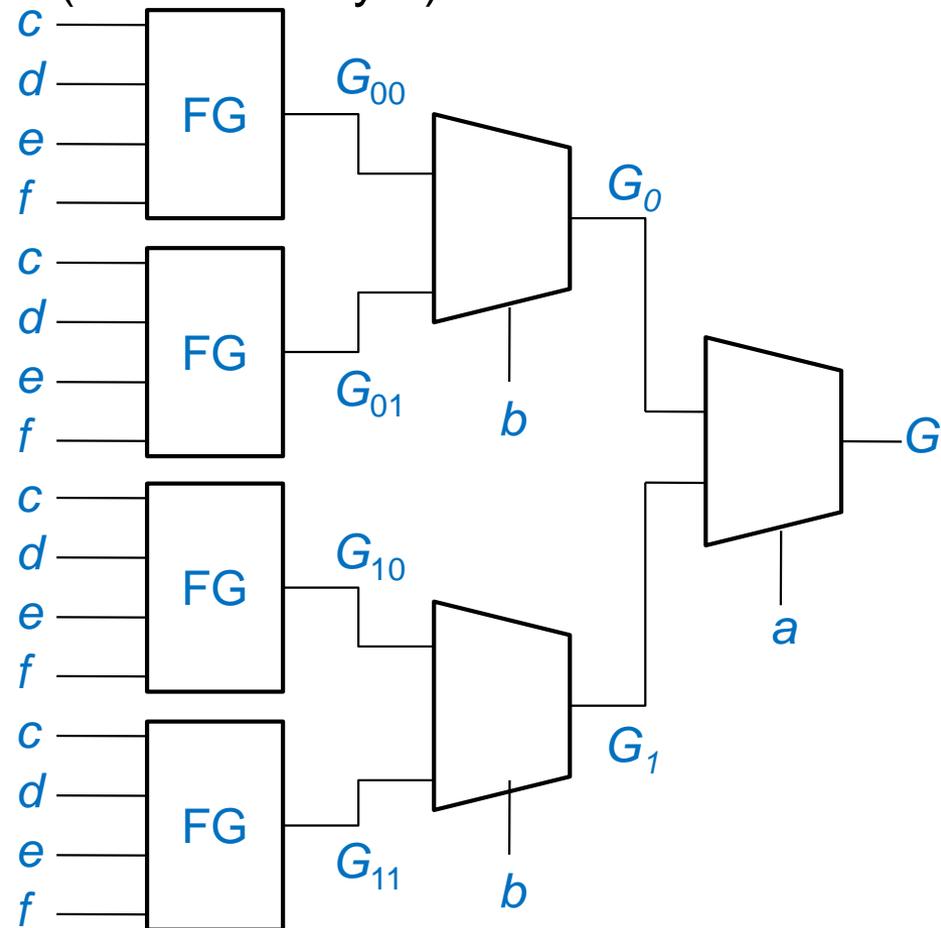

# Decomposition of Switching Functions

Shannon's expansion theorem: reduces input variables

$$f(x_1, x_2, \dots, x_{i-1}, x_i, x_{i+1}, \dots, x_n) = x'_i f_0 + x_i f_1$$

$$= x'_i f(x_1, x_2, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n) + x_i f(x_1, x_2, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n)$$

