

Logic design (2017 fall)

Quiz # 11

Name: \_\_\_\_\_ ID: \_\_\_\_\_

1. (40%) An rising-edge-triggered AB flip-flop has two inputs A, B and one output Q, which operates as follows: When A=0 and B=0, the next clock edge resets Q to 0; when A=0 and B=1, the next clock edge leaves state unchanged; when A=1 and B=0, the next clock edge complements the state; and when A=1 and B=1, the next clock edge sets Q to 1.
  - (a) (25%) Construct the state table of the AB flip-flop
  - (b) (15%) Derive and minimize the next-state equation for the AB flip-flop.

Ans:

(a)


$ABQ(t)$	$Q(t+\epsilon)$
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	1
1 0 1	0
1 1 0	1
1 1 1	1

(b)


$$Q(t+\epsilon) = AQ' + BQ$$

2. (60%) The function table and circuit of S-R latch with control input EN are shown below:

EN	SR	Operation
0	XX	No state change
1	00	No state change
1	01	Reset Q to 0
1	10	Set Q to 1
1	11	Indeterminate

 

 Complete the following timing diagram, assuming initial  $Q=0$ ,  $Q'=1$  and each NAND gate has the same propagation delay 10ns.



Ans:

