

Logic design (2017 fall)

Quiz # 14

Name: \_\_\_\_\_ ID: \_\_\_\_\_

(100%) A Mealy machine has two inputs ( $X_1$  and  $X_2$ ) and two outputs ( $Z_1$  and  $Z_2$ ). The inputs  $X_1X_2$  represent a 2-bit binary number,  $N$ , where  $X_1$  is the most significant bit. If the present value of  $N$  is greater than the previous value, then  $Z_1$  is 1. If the present value of  $N$  is less than the previous value, then  $Z_2$  is 1. Otherwise,  $Z_1$  and  $Z_2$  are 0. When the first pair of inputs is received, the “otherwise” category applies.

- (16%) List the output sequence according to the given input sequence in Table\_1.
- (20%) List the definition of each state in Table\_2. The minimum number of states, including starting state, is five.

		input sequence.								
$X_1$		0	0	1	1	0	1	1	0	1
$X_2$		1	0	1	0	0	0	1	1	0
		output sequence								
$Z_1$		0								
$Z_2$		0								


Table\_1

State	State meaning
$S_0$	Initial State
$S_1$	
$S_2$	
$S_3$	
$S_4$	

Table\_2

- (64%) Complete the state graph for this Mealy machine.

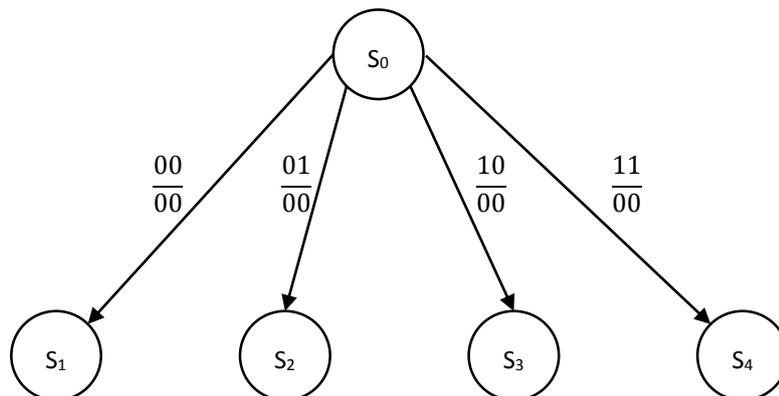You should use  $\frac{X_1 X_2}{Z_1 Z_2}$  to describe the state graph



(a)

State	State meaning
S <sub>0</sub>	Initial State
S <sub>1</sub>	Previous input was 00
S <sub>2</sub>	Previous input was 01
S <sub>3</sub>	Previous input was 10
S <sub>4</sub>	Previous input was 11

(b)

	input sequence.								
X <sub>1</sub>	0	0	1	1	0	1	1	0	1
X <sub>2</sub>	1	0	1	0	0	0	1	1	0
	output sequence								
Z <sub>1</sub>	0	0	1	0	0	1	1	0	1
Z <sub>2</sub>	0	1	0	1	1	0	0	1	0

(c)

