

Logic design (2017 Fall)

Quiz # 15

Name: \_\_\_\_\_ ID: \_\_\_\_\_

1. (60%) Given the state table


Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>7</sub>	S <sub>2</sub>	0	0
S <sub>1</sub>	S <sub>5</sub>	S <sub>4</sub>	0	0
S <sub>2</sub>	S <sub>3</sub>	S <sub>7</sub>	0	0
S <sub>3</sub>	S <sub>4</sub>	S <sub>0</sub>	0	1
S <sub>4</sub>	S <sub>0</sub>	—	0	—
S <sub>5</sub>	—	S <sub>6</sub>	1	—
S <sub>6</sub>	—	S <sub>2</sub>	0	1
S <sub>7</sub>	S <sub>1</sub>	S <sub>3</sub>	—	—

(a) (40%) Use implication table to find the equivalent states.

(b) (20%) Show the reduced state table.

Ans:


(a)

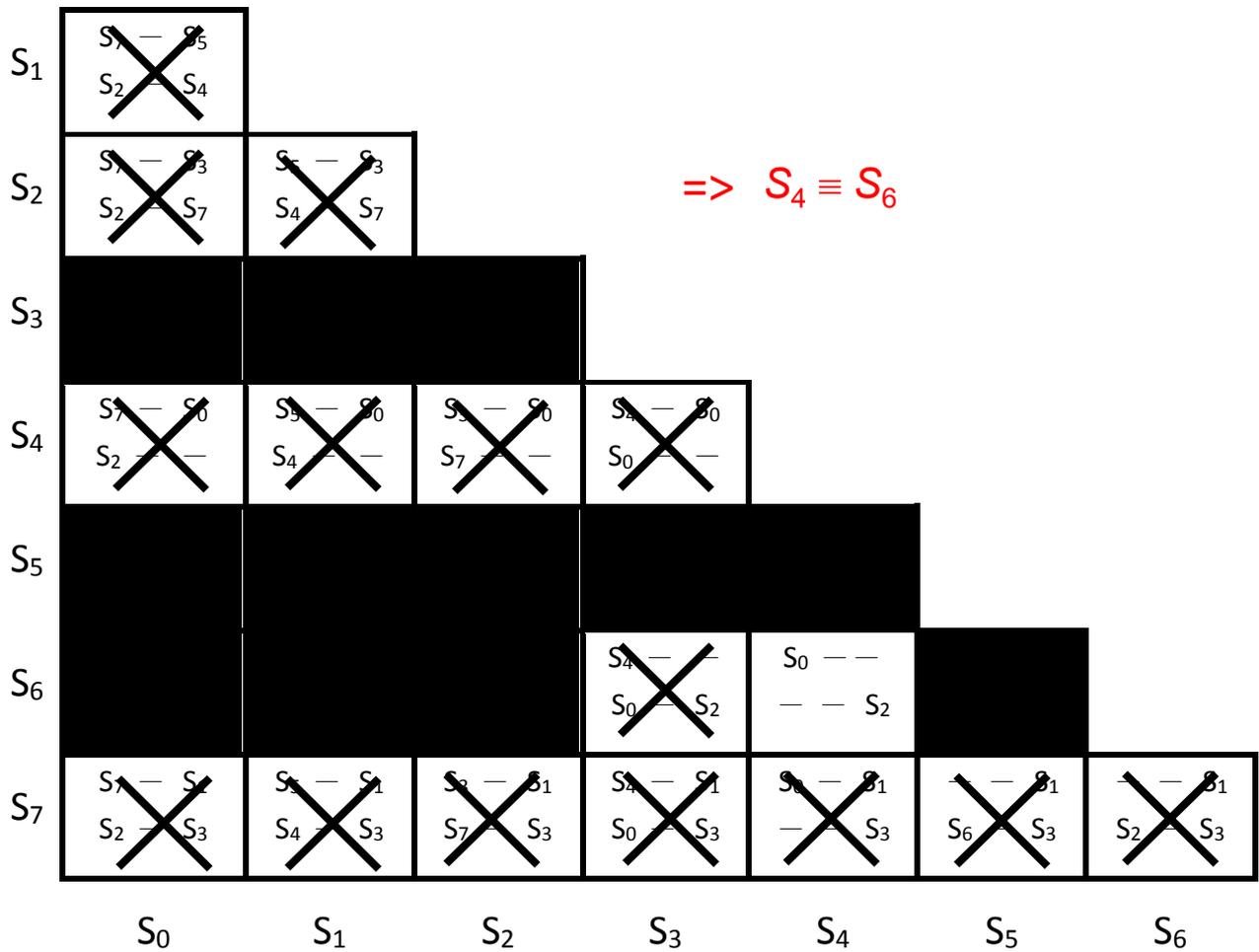

(b)

Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>7</sub>	S <sub>2</sub>	0	0
S <sub>1</sub>	S <sub>5</sub>	S <sub>4</sub>	0	0
S <sub>2</sub>	S <sub>3</sub>	S <sub>7</sub>	0	0
S <sub>3</sub>	S <sub>4</sub>	S <sub>0</sub>	0	1
S <sub>4</sub>	S <sub>0</sub>	S <sub>2</sub>	0	1
S <sub>5</sub>	—	S <sub>6</sub>	1	—
S <sub>7</sub>	S <sub>1</sub>	S <sub>3</sub>	—	—

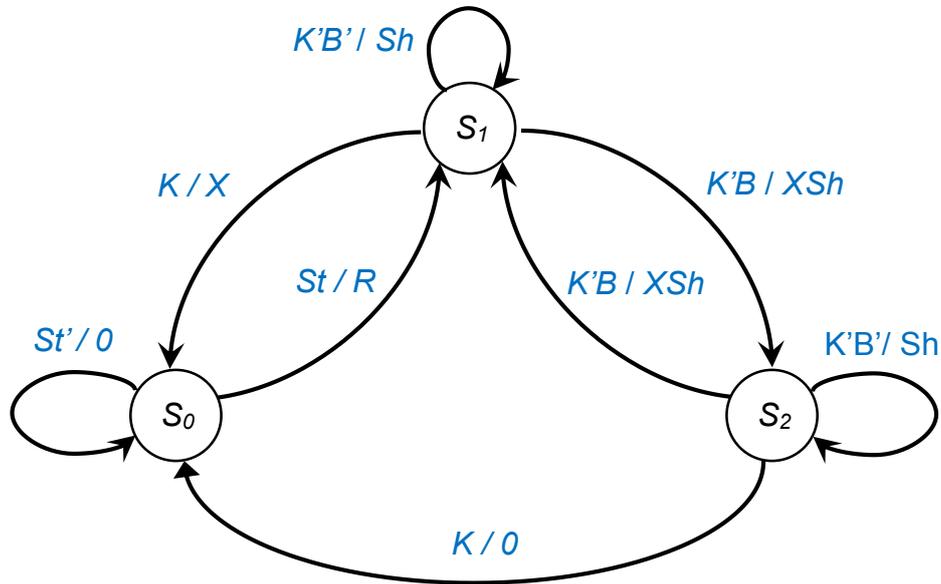2. (40%) The state graph below represents a sequential circuit that controls an odd-parity generator. The circuit has three inputs  $St$ ,  $K$ ,  $B$  and three outputs  $Sh$ ,  $R$  and  $X$ .



Assume that one-hot assignment is used as the state assignment for this sequential circuit. The three flip-flops used for this one-hot assignment are denoted as  $Q_0$ ,  $Q_1$ , and  $Q_2$ , where  $Q_0$ ,  $Q_1$ , and  $Q_2$  correspond to the states  $S_0$ ,  $S_1$ , and  $S_2$ , respectively. All flip-flop in this circuit are D flip-flops.

- (a) (20%) Derive the next-state equations for  $Q_0^+$ ,  $Q_1^+$  and  $Q_2^+$ .  
 (b) (20%) Derive the output equations for  $Sh$ ,  $R$ , and  $X$ .

Note that all equations in (a) and (b) needs to be expressed in the minimum sum-of-products form.

Ans:

$$Q_0^+ = St'Q_0 + KQ_1 + KQ_2$$

$$Q_1^+ = StQ_0 + K'B'Q_1 + K'BQ_2$$

$$Q_2^+ = K'BQ_1 + K'B'Q_2$$

$$\begin{aligned} Sh &= K'B'Q_1 + K'BQ_1 + K'B'Q_2 + K'BQ_2 \\ &= K'Q_1 + K'Q_2 \end{aligned}$$

$$R = StQ_0$$

$$\begin{aligned} X &= KQ_1 + K'BQ_1 + K'BQ_2 \\ &= KQ_1 + BQ_1 + K'BQ_2 \end{aligned}$$