

Logic design (2017 fall)

Quiz # 4

Name: \_\_\_\_\_ ID: \_\_\_\_\_

1. A combinational circuit has four binary inputs (A, B, C, D) and three binary outputs (X, Y, Z). XYZ represents a binary number whose value equals the number of 0s at the input.

For example, if ABCD = 1011 then XYZ = 001.

(a) (15%) Complete the true table for the circuit.

(b) (15%) Find the minterm expansion for Z using *m*-notation.

(c) (15%) Find the maxterm expansion for Y using *M*-notation.

Note that the order of the input variables for *m*-notation and *M*-notation is ABCD.

ABCD	X	Y	Z
0000	1	0	0
0001	0	1	1
0010	0	1	1
0011	0	1	0
0100	0	1	1
0101	0	1	0
0110	0	1	0
0111	0	0	1
1000	0	1	1
1001	0	1	0
1010	0	1	0
1011	0	0	1
1100	0	1	0
1101	0	0	1
1110	0	0	1
1111	0	0	0

$$Z = m(1, 2, 4, 7, 8, 11, 13, 14)$$

$$Y = M(0, 7, 11, 13, 14, 15)$$

2. Fig.1 shows a circuit performing binary subtraction between two 4-bit unsigned binary integers  $X(x_3x_2x_1x_0)$  and  $Y(y_3y_2y_1y_0)$ . When  $X$  is larger or equal to  $Y$ , the 4-bit output  $D(d_3d_2d_1d_0)$  will be equal to the difference of subtracting  $Y$  from  $X$  and the other output  $bor_4$  will be equal to 0. When  $X$  is smaller than  $Y$ , the output  $bor_4$  will be 1. This subtraction circuit is designed by serially connecting 4 full subtractors. Fig.2 shows the functionality of a full subtractor with 3 inputs ( $x, y, bor_{in}$ ) and two outputs ( $d, bor_{out}$ ).

- (a) (25%) Complete the true table of a full subtractor shown below.
- (b) (15%) Find the minterm expansions for the output  $d$  of the full subtractor.
- (c) (15%) Find the maxterm expansions for the output  $bor_{out}$  of the full subtractor.

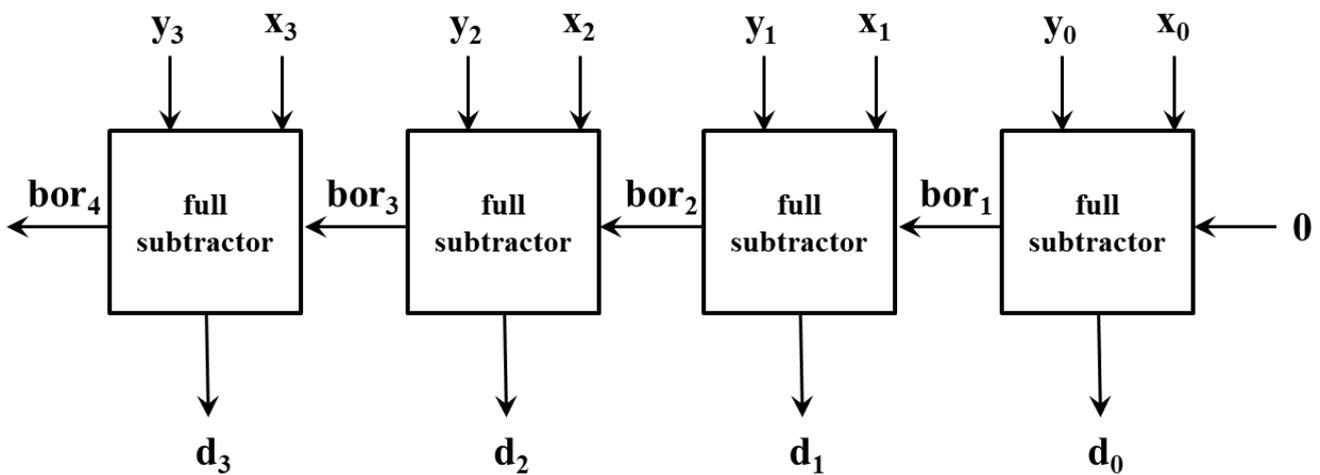


Fig.1

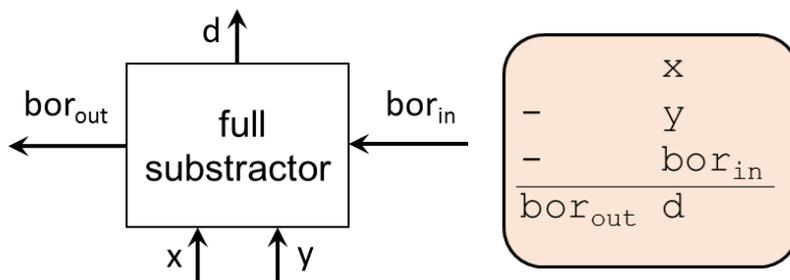


Fig.2

x	y	bor <sub>in</sub>	d	bor <sub>out</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Truth table

$$d = m(1, 2, 4, 7) = x'y'bor_{in} + x' y bor_{in}' + xy'bor_{in}' + xybor_{in}$$

$$bor_{out} = \prod M(0, 4, 5, 6) = (x + y + bor_{in})(x' + y + bor_{in})(x' + y + bor_{in}')(x' + y' + bor_{in})$$