

Logic design (2018 fall)  
Quiz # 14

Name: \_\_\_\_\_ ID: \_\_\_\_\_

(100%) A sequential circuit has an input X and outputs (Y and Z). YZ represents a 2-bit binary number equal to the number of pairs of adjacent 1's that have been received as inputs. For example, the input sequence 0110 contains one pair, the sequence 01110 two pairs, and the sequence 0110111 contains three pairs of adjacent 1's. The circuit **RESETS** when the total number of pairs of 1's received reaches four, and recalculates the number of pairs of adjacent 1's just like the beginning of the sequence (as shown in the following examples). Find a Moore state graph and table for the circuit (hint: 8 states are sufficient).

Examples:

Input sequence: X = 0 1 0 1 1 0 1 1 1 0 0 1 0 1 0 1 0 1 1 1 0 1 1 0 1 1 0 0 1 0  
 Output sequences: Y = 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 1 1 1 0 0 0 0 0 0 0 1 1 1 1 1  
 Z = 0 0 0 0 1 1 1 0 1 1 1 1 1 1 1 1 1 1 1 0 0 0 0 1 1 1 0 0 0 0 0  
 Input sequence: X = 1 1 1 1 1 1 1 1  
 Output sequences: Y = 0 0 1 1 0 0 0 1  
 Z = 0 1 0 1 0 0 1 0

(Be sure that the circuit resets as shown in the example)

a. (50%) Derive the following state table for the Moore machine.

State	Next State		YZ
	X = 0	X = 1	
S <sub>0</sub>			
S <sub>1</sub>			
S <sub>2</sub>			
S <sub>3</sub>			
S <sub>4</sub>			
S <sub>5</sub>			
S <sub>6</sub>			
S <sub>7</sub>			

- b. (50%) Complete the state graph for this Moore machine.

a. (50%) Derive the following state table for the Moore machine.

State	Next State		YZ
	X = 0	X = 1	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	00
S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	00
S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>	01
S <sub>3</sub>	S <sub>3</sub>	S <sub>2</sub>	01
S <sub>4</sub>	S <sub>5</sub>	S <sub>6</sub>	10
S <sub>5</sub>	S <sub>5</sub>	S <sub>4</sub>	10
S <sub>6</sub>	S <sub>7</sub>	S <sub>0</sub>	11
S <sub>7</sub>	S <sub>7</sub>	S <sub>6</sub>	11

b. (50%) Complete the state graph for this Moore machine.

