

Logic design (2018 FALL)

Quiz # 8

Name: _____ ID: _____

1. (100%) Given the following logic function.

$$F(A, B, C, D) = \sum m(2,3,6,7,8,9,13,15)$$

(a)(20%) Find a minimum OR-AND circuit for F. Note that you don't need to draw the OR-AND circuit.


Listing the corresponding Boolean expression for the circuit would be enough.

(b)(30%) Assuming that only one input signal can change each time, identify all pairs of input patterns that may result in static-0 hazards. Note that you only need to list the pairs of input patterns.

The order of the patterns in a pair doesn't matter.

(c)(50%) Find an OR-AND circuit for F which has no static-0 hazards. Note that you don't need to draw the OR-AND circuit. Listing the corresponding Boolean expression for the circuit would be enough.

Ans:

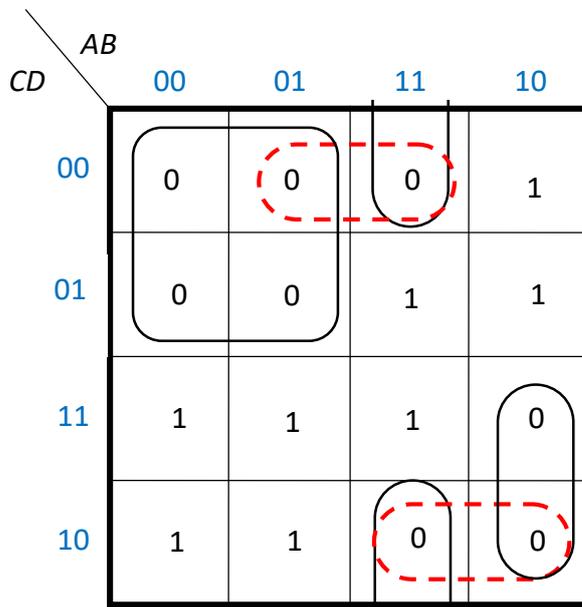

(a) $F = (A + C)(A' + B' + D)(A' + B + C')$

(b) (A,B,C,D): (0,1,0,0) -> (1,1,0,0)

(A,B,C,D): (1,0,1,0) -> (1,1,1,0)

(c) $F = (A + C)(A' + B' + D)(A' + B + C')\underline{(B' + C + D)(A' + C' + D)}$