

# UNIT 2

## BOOLEAN ALGEBRA



Spring 2011

# Boolean Algebra

## □ Contents

- Introduction
- Basic operations
- Boolean expressions and truth tables
- Theorems and laws
  - Basic theorems
  - Commutative, associative, and distributive laws
  - Simplification theorems
  - Multiplying out and factoring
  - DeMorgan's laws

## □ Reading


- Unit 2

# Introduction

- **Boolean algebra**
  - Is the basic mathematics for logic design of digital systems
  - Differs from ordinary algebra in the **values, operations, and laws**
- **History**
  - **George Boole** developed Boolean algebra in 1847 and used it to solve problems in mathematical logic
    - British mathematician and philosopher
  - **Claude Shannon** first applied Boolean algebra to the design of switching circuits in 1939
    - American electrical engineer and mathematician
    - Master's thesis (21 years-old)
- **In this unit, you will learn how to...**
  - Use a truth table
  - Manipulate basic operations and apply laws of Boolean algebra
  - Relate Boolean expressions to basic logic gates
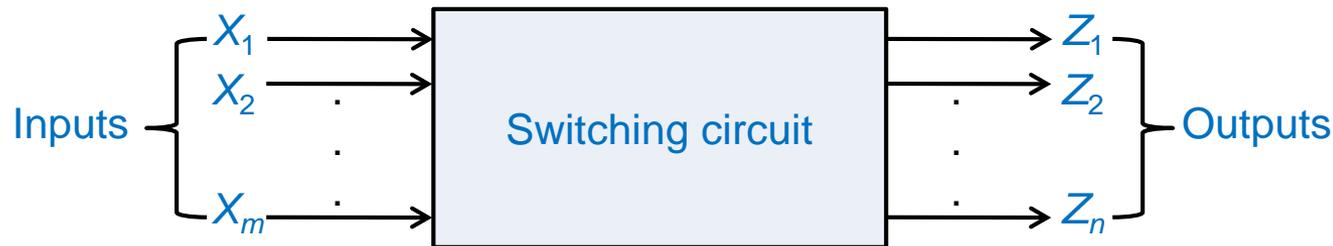
# Switching Circuit & Boolean Variables

- A switching circuit has one or more inputs and one or more outputs that take on discrete values (**two-value** in general)



- We usually use a Boolean variable, such as  $X$ ,  $Y$ ,  $Z$ , to represent an input or output of a switching circuit
  - ▣ Usually take on only two different values
  - ▣ 1/0 for **High/Low** or **True/False** or **Yes/No**
    - Just symbols, **NO numeric values**
  - ▣ A two-value Boolean variable is also called a switching variable

Boolean algebra differs from ordinary algebra in **values**, operations, laws

Boolean algebra differs from ordinary algebra in values, **operations**, laws

5

## Basic Operations


**NOT, AND, OR**

# Operation -- Logic NOT

## □ Complement = Inverse = Negate = NOT (' ; $\bar{\quad}$ ; $\sim$ ; $\neg$ )

□  $0' = 1, 1' = 0$

□ Symbol


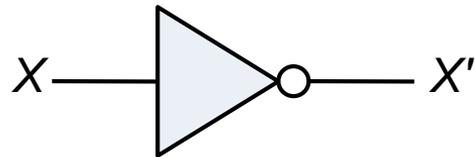


NOT gate  
Inverter

□ Truth table

Inputs		Outputs
$X$		$X'$
0		1
1		0

Input combinations      Output values

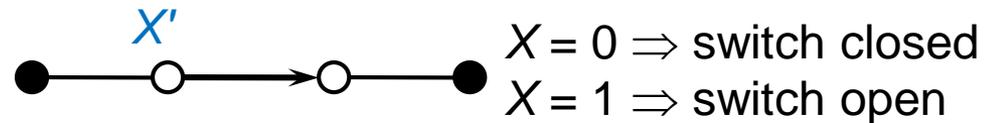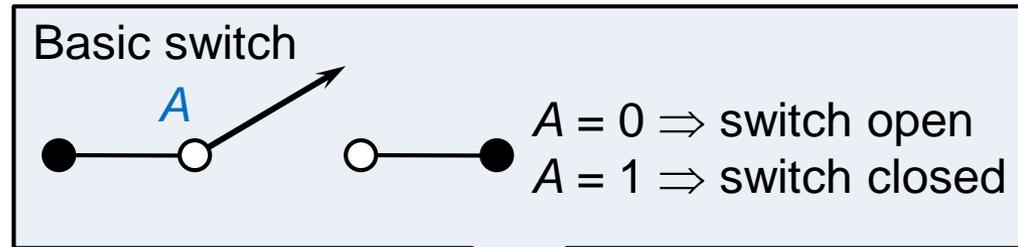


# Operation -- Logic AND

## AND ( $\bullet$ ; $\wedge$ )

- $0 \bullet 0 = 0, 0 \bullet 1 = 0, 1 \bullet 0 = 0, 1 \bullet 1 = 1$

### Symbol

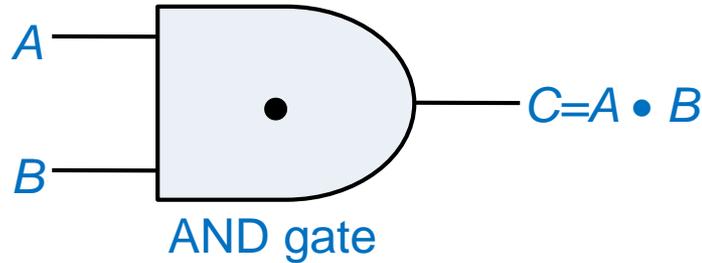


### Truth table

A	B	C = A • B
0	0	0
0	1	0
1	0	0
1	1	1

Omit " $\bullet$ "

If one input is 0  
 $\Rightarrow$  output is 0

### Switch (in series)

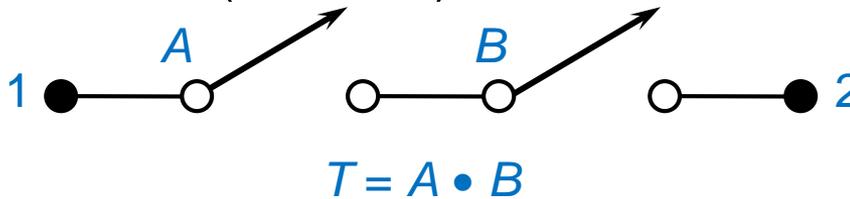

$T = 0 \Rightarrow 1 \rightarrow 2$  open  
 $T = 1 \Rightarrow 1 \rightarrow 2$  closed


Switch A closed and switch B closed

# Operation -- Logic OR

## OR (+; ∨)

0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, 1 + 1 = 1

Symbol

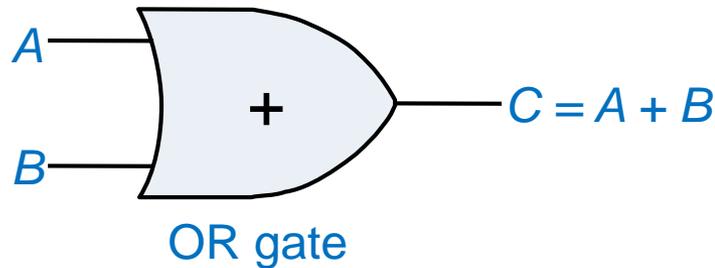


Truth table

A	B	C = A+B
0	0	0
0	1	1
1	0	1
1	1	1

If one input is 1  
⇒ output is 1


Switch (in parallel)

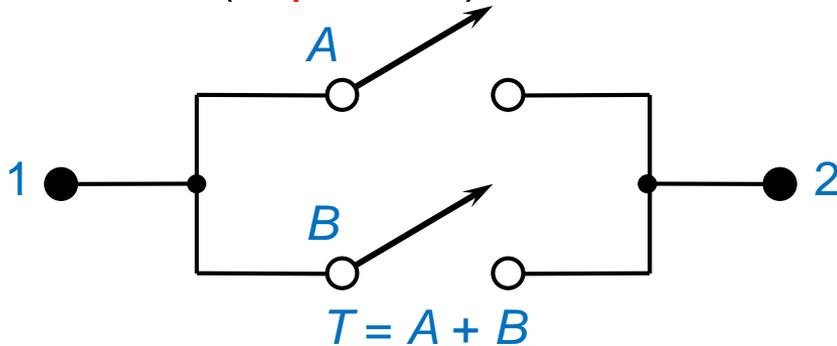

$T = 0 \Rightarrow 1 \rightarrow 2$  open  
 $T = 1 \Rightarrow 1 \rightarrow 2$  closed

Switch A closed or switch B closed


# Boolean Expressions and Truth Tables

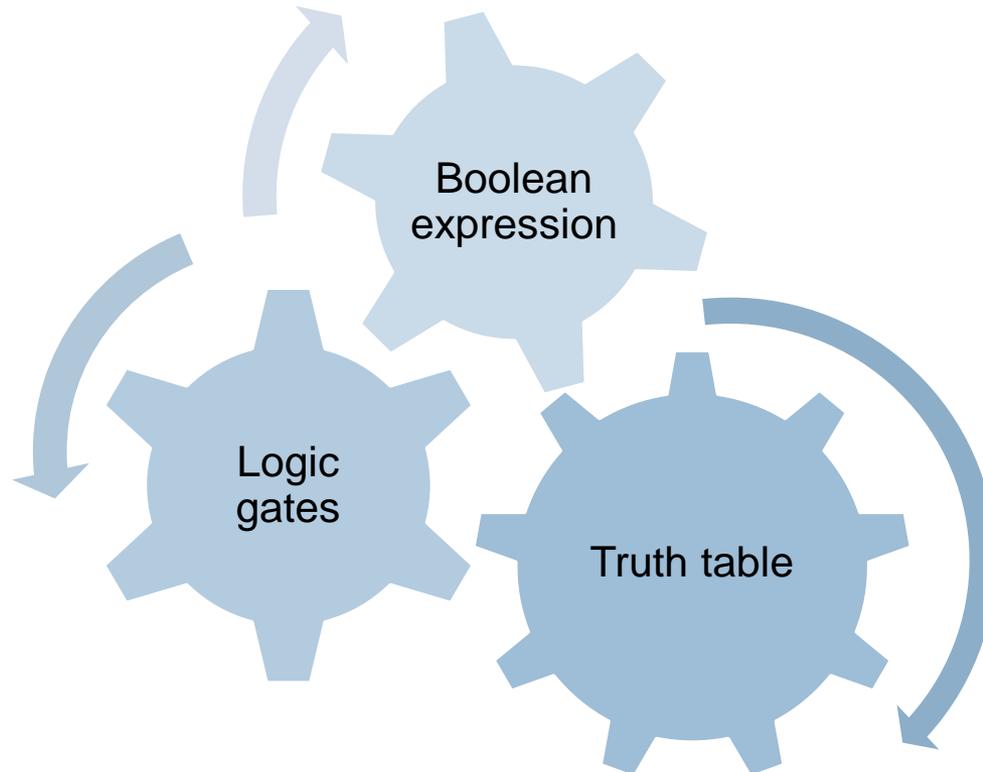

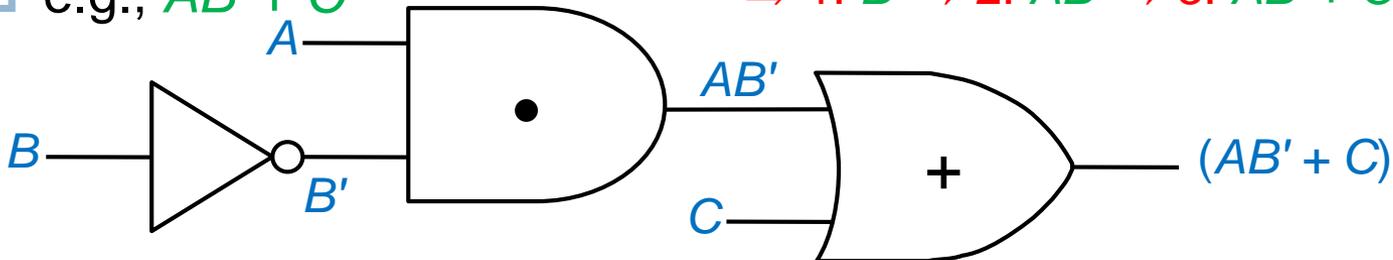
# Boolean Expressions vs. Logic Gates

- A **Boolean expression** is formed by basic operations on variables or constants, e.g., the simplest one: 0, 1, X, Y
- Realize a Boolean expression by a circuit of logic gates
  - Perform operations in order: **Parentheses** → **NOT** → **AND** → **OR**

□ e.g.,  $AB' + C$   $\Rightarrow$  1.  $B'$   $\rightarrow$  2.  $AB'$   $\rightarrow$  3.  $AB' + C$



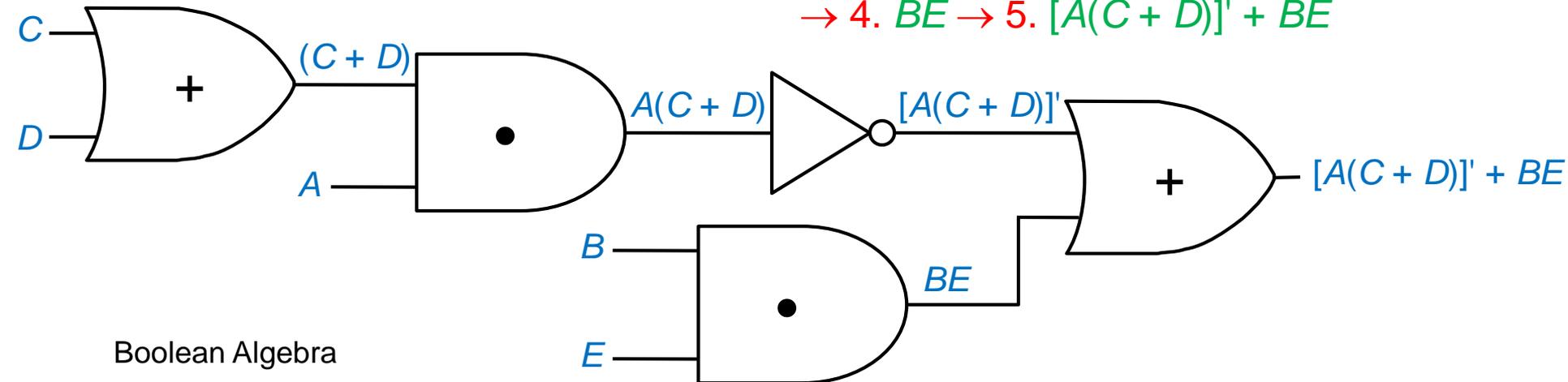□ e.g.,  $[A(C + D)]' + BE$   $\Rightarrow$  1.  $C + D$   $\rightarrow$  2.  $A(C + D)$   $\rightarrow$  3.  $[A(C + D)]'$   $\rightarrow$  4.  $BE$   $\rightarrow$  5.  $[A(C + D)]' + BE$




# Boolean Expressions vs. Truth Tables

$n$  variables  
 $\Rightarrow 2^n$  rows

- A **truth table** specifies the output values of a Boolean expression for **all possible combinations of input values**
- $\Rightarrow$  Check the **equivalence** between two expressions

□ e.g.,  $AB' + C = (A + C)(B' + C)$

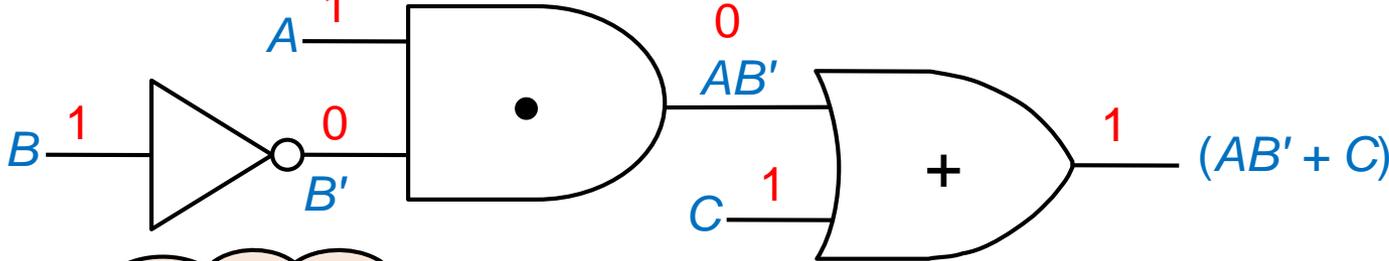


One function has different expressions

Expressions show the condition to make output == 1

A	B	C	B'	AB'	AB' + C	A+C	B'+C	(A+C)(B'+C)
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	1	1

# Example: $F = A' + B$

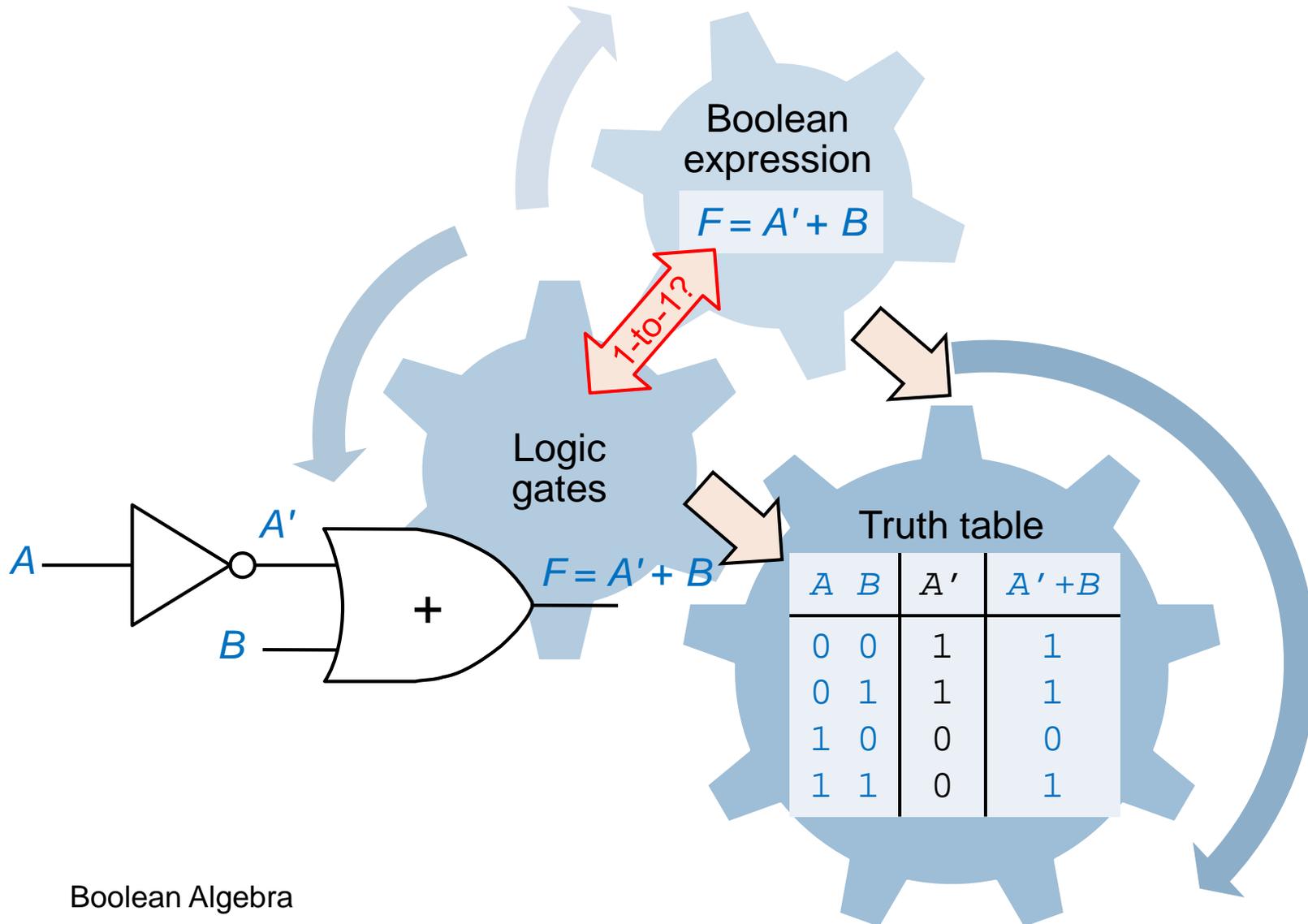

Boolean algebra differs from ordinary algebra in values, operations, **laws**

13

## Theorems and Laws

# Basic Theorems (1/3)

## Operations with 0 and 1

- $X + 0 = X$



- $X \cdot 1 = X$

- $X + 1 = 1$

- $X \cdot 0 = 0$

- e.g.,  $(AB' + D)E + 1 = 1$

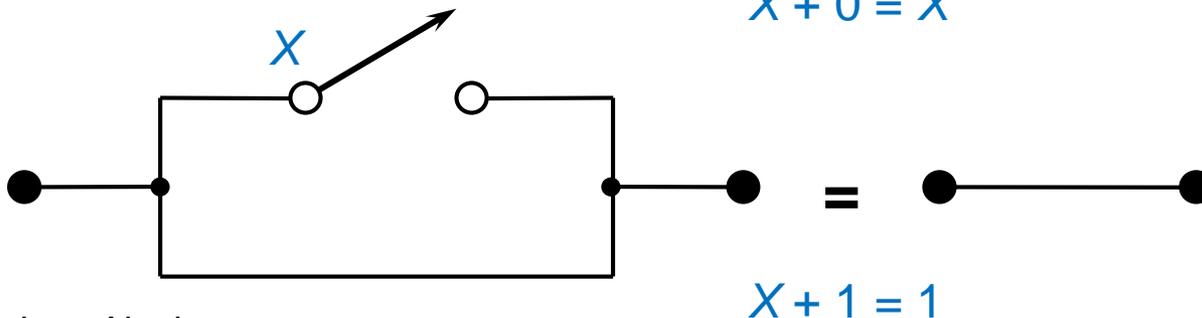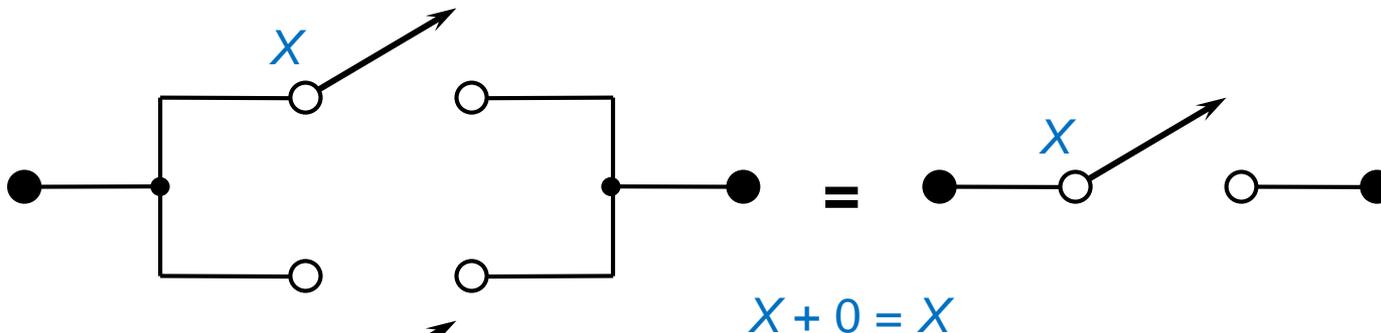The variable  $X$   
can be substituted  
by any expression





# Basic Theorems (2/3)

## □ Idempotent laws



- $X + X = X$

- $X \cdot X = X$

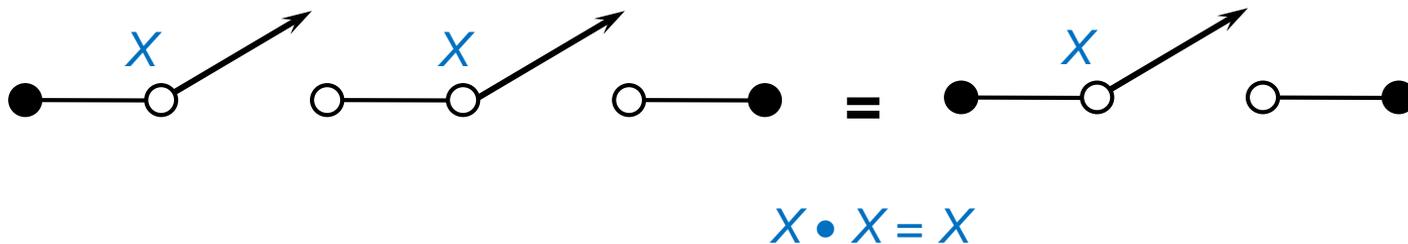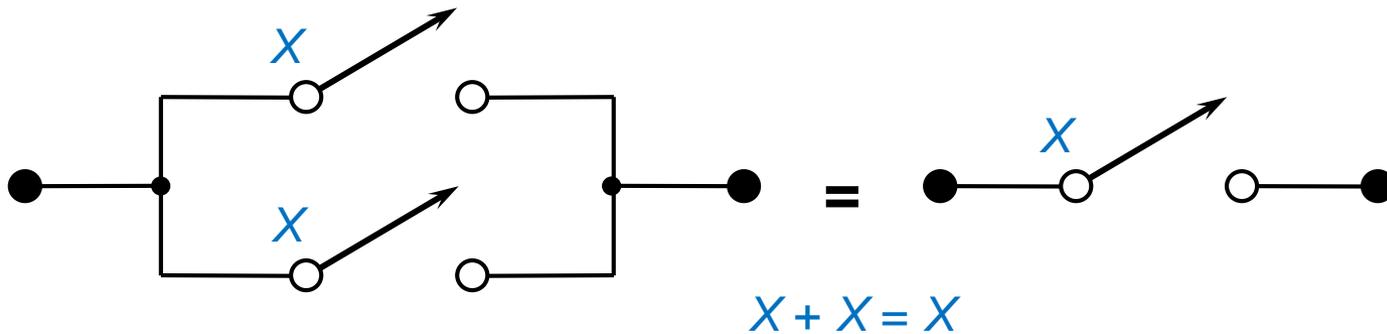

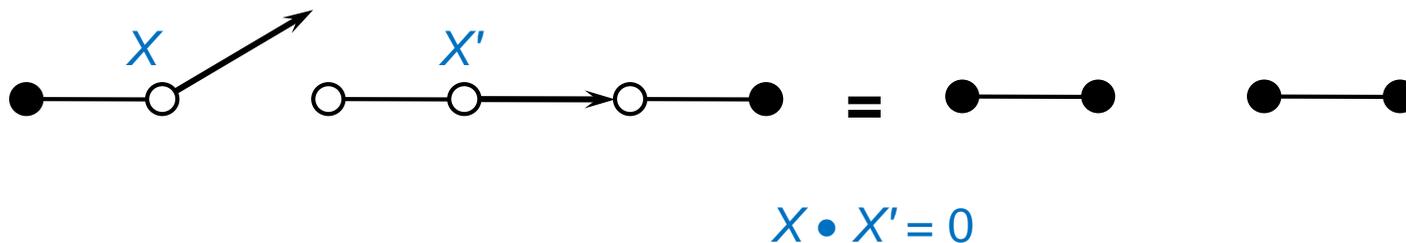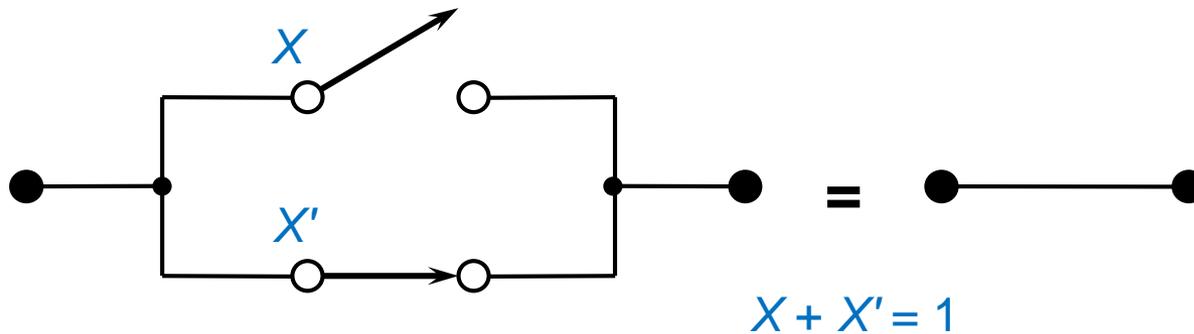
# Basic Theorems (3/3)

- **Involution law**
  - $(X')' = X$
- **Laws of complementarity**
  - $X + X' = 1$
  - $X \cdot X' = 0$
  - e.g.,  $(AB' + D)(AB' + D)' = 0$


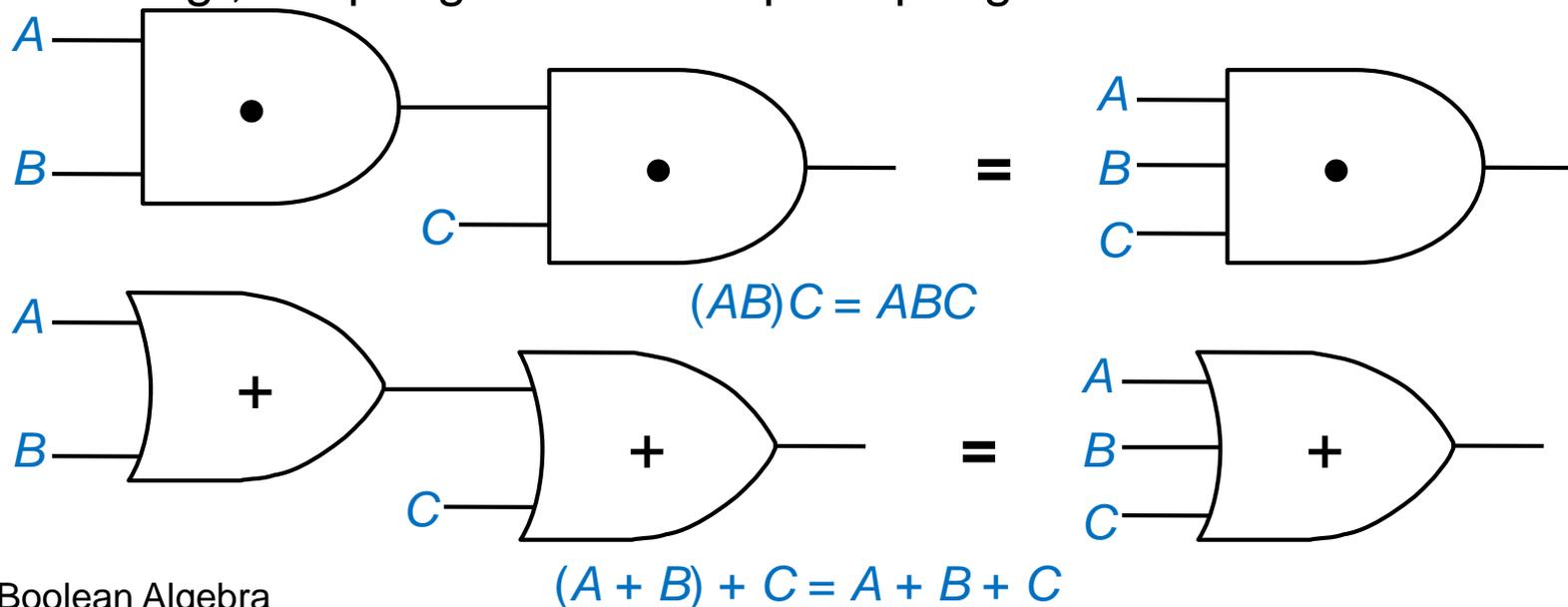
# Commutative/Associative Laws

- **Commutative laws for AND and OR**
  - $XY = YX$
  - $X + Y = Y + X$
- **Associative laws for AND and OR**
  - $(XY)Z = X(YZ) = XYZ$
  - $(X + Y) + Z = X + (Y + Z) = X + Y + Z$
  - e.g., 2-input gates  $\Rightarrow$  multiple-input gates



# Distributive Laws (1/2)

- **Ordinary distributive law**

- $X(Y + Z) = XY + XZ$



- **Second distributive law (Important !)**

- $X + YZ = (X + Y)(X + Z)$



- Proof?

Only valid for  
Boolean algebra

# Distributive Laws (2/2)

□ Prove a Boolean theorem/law by:

1. Truth table

$$X + YZ = (X + Y)(X + Z)$$

=?

X	Y	Z	YZ	X+YZ	X+Y	X+Z	(X+Y)(X+Z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

2. Basic theorems

$$\begin{aligned}
 & (X + Y)(X + Z) \\
 &= X(X + Z) + Y(X + Z) \\
 &= XX + XZ + YX + YZ \\
 &= X + XZ + XY + YZ \\
 &= X \cdot 1 + XZ + XY + YZ \\
 &= X(1 + Z + Y) + YZ \\
 &= X \cdot 1 + YZ \\
 &= X + YZ
 \end{aligned}$$


# Simplification Theorems

## Useful simplification theorems

$XY + XY' = X$

$X + XY = X$

$(X + Y')Y = XY$

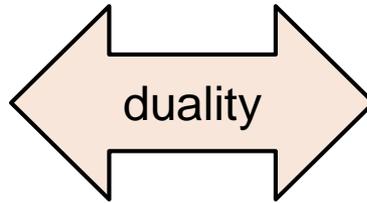

$(X + Y)(X + Y') = X$

$X(X + Y) = X$

$XY' + Y = X + Y$


## Proof:

$X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$

$X(X + Y) = XX + XY = X + XY = X$

$XY' + Y = Y + XY' = (Y + X)(Y + Y') = (Y + X) \cdot 1 = Y + X$


Use switches

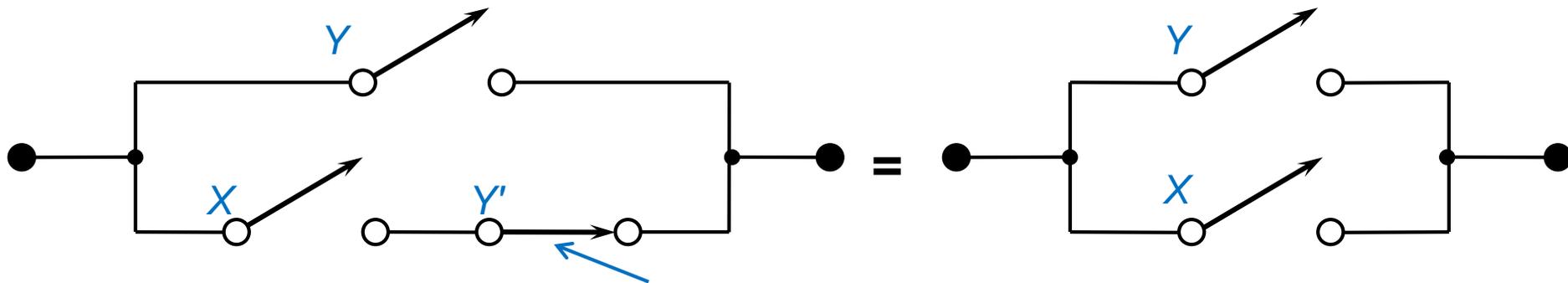

If switch  $Y$  open  $\Rightarrow$  switch  $Y'$  closed


# Simplification Examples

1.  $A(A'+B) = AB$

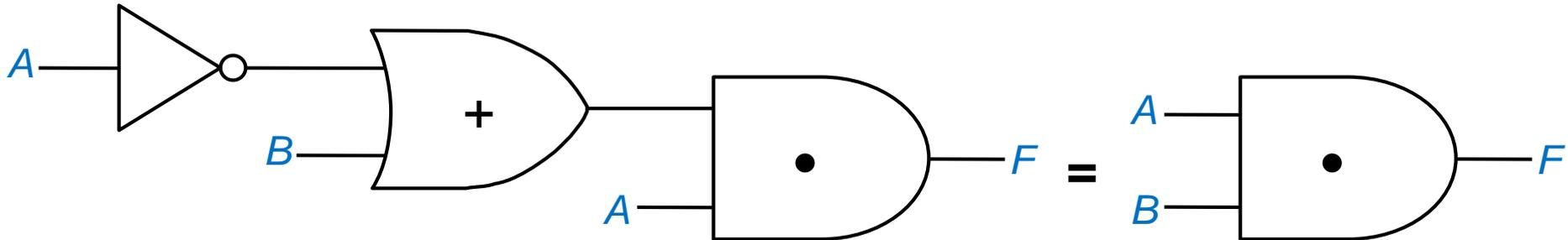

2.  $Z = [A + B'C + D + EF][A + B'C + (D + EF)']$   
 $= [A + B'C + D + EF][A + B'C + (D + EF)']$   
 $= [X + Y][X + Y']$   
 $= X = A + B'C$

3.  $Z = (AB + C)(B'D + C'E) + (AB + C)'$   
 $= (AB + C)(B'D + C'E) + (AB + C)'$   
 $= X Y + X'$   
 $= XY + X' + X'Y = (X+X')Y + X'$   
 $= Y + X' = B'D + C'E + (AB + C)'$

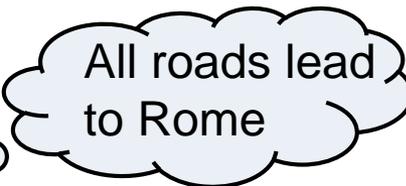  
 $= XY + X' \cdot 1 = XY + X'(1+Y)$

# Multiplying Out

22

- Use the ordinary distributive law

$$X(Y + Z) = XY + XZ$$

to multiply out an expression to obtain a **sum-of-products** form

- e.g.,

$$AB' + CD'E + AC'E' \quad (V)$$

$$A + B' + C + D'E \quad (V)$$

$$(A + B)CD + EF \quad (X)$$



**SOP**: Sum of products of only **single** variables


# Example: Multiplying Out $(A+BC)(A+D+E)$

1. **Multiply out completely and then eliminate redundant terms**

$$\begin{aligned}(A+BC)(A+D+E) &= A+AD+AE+ABC+BCD+BCE \\ &= A(1+D+E+BC)+BCD+BCE \\ &= A+BCD+BCE\end{aligned}$$

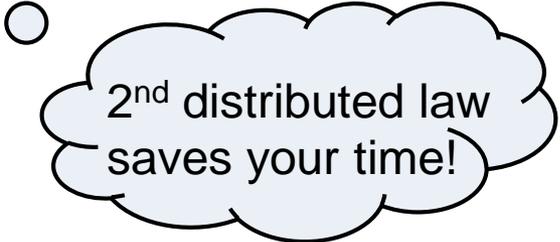2. **Or, apply 2<sup>nd</sup> distributive law first:  $(X+Y)(X+Z)=X+YZ$**

$$\begin{aligned}(A+BC)(A+D+E) &= A+BC(D+E) \\ &= A+BCD+BCE\end{aligned}$$



2<sup>nd</sup> distributed law  
saves your time!

# Factoring

24

- Use the second distributive law

$$X + YZ = (X + Y)(X + Z)$$

to factor an expression to obtain a **product-of-sums** form


- e.g.,

$$(A + B')(C + D + E)(A + C' + E') \quad (V)$$

$$(A + B)(C + D + E)F \quad (V)$$

$$AB'C(D' + E) \quad (V)$$

$$(A + B)(C + D) + EF \quad (X)$$

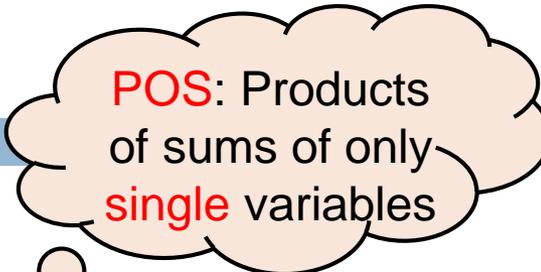

POS: Products of sums of only **single** variables

# Example: Factoring

## 1. Factor $A + B'CD$

$$A + B'CD = (A + B')(A + CD) = (A + B')(A + C)(A + D)$$


## 2. Factor $AB' + C'D$

$$AB' + C'D = (AB' + C')(AB' + D) = (A + C')(B' + C')(A + D)(B' + D)$$


## 3. DIY: Factor $C'D + C'E' + G'H$

Iteratively apply  
2<sup>nd</sup> distributed law


# SOP vs. Logic Gates

## Realize SOPs by two-level circuits (AND-OR)

▣  $AB' + CD'E + AC'E'$

AND


OR

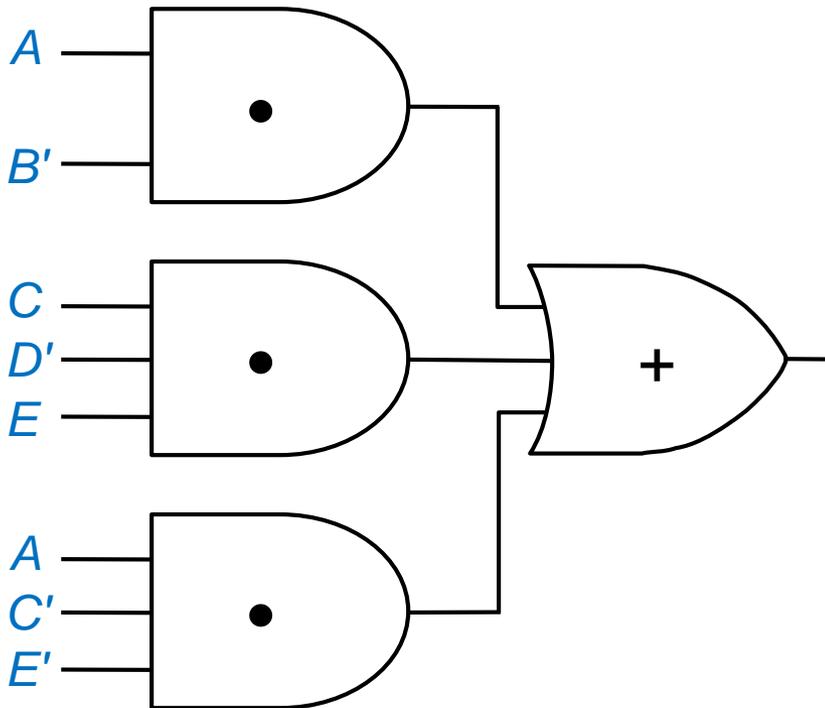

▣  $A + B' + C + D'E$

AND

OR

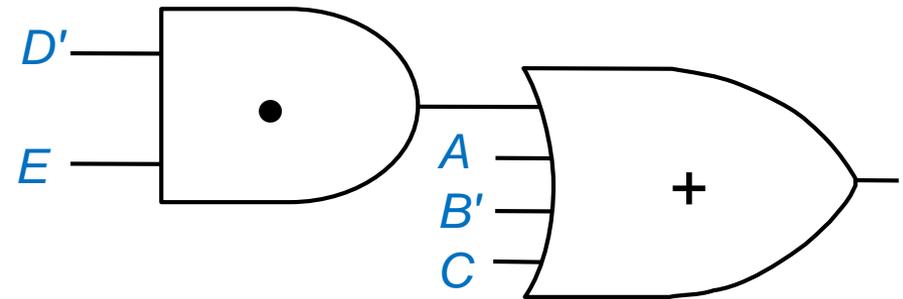


# POS vs. Logic Gates

□ Realize POSs by **two-level** circuits (**OR-AND**)

□  $(A + B')(C + D + E)(A + C' + E')$

OR


AND

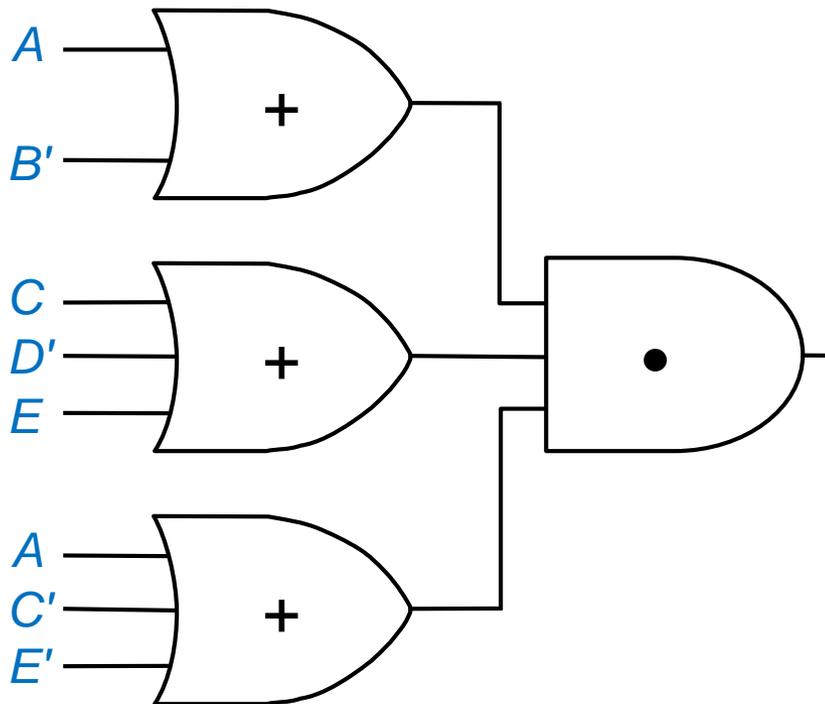

□  $AB'C(D' + E)$

OR

AND

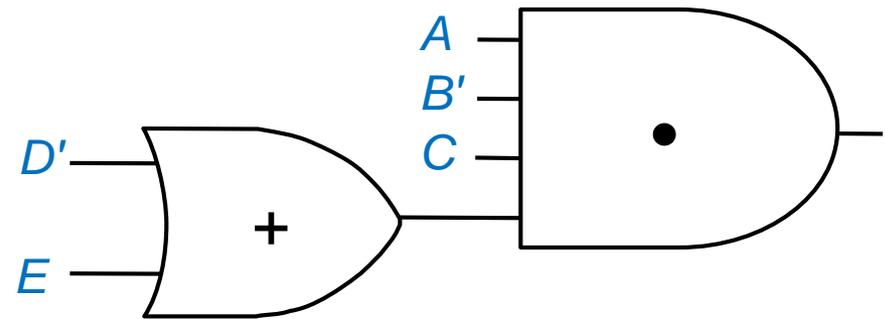

# DeMorgan's Laws

## □ Complement a Boolean expression by **DeMorgan's laws**

$$\square (X + Y)' = X'Y'$$

$$\square (XY)' = X' + Y'$$

□ Proof: By truth table

$X$	$Y$	$X'$	$Y'$	$X+Y$	$(X+Y)'$	$X'Y'$	$XY$	$(XY)'$	$X'+Y'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

## □ Generalize to $n$ variables:

$$\square (X_1 + X_2 + \dots + X_n)' = X_1' X_2' \dots X_n'$$

$$\square (X_1 X_2 \dots X_n)' = X_1' + X_2' + \dots + X_n'$$

## □ One-step rule:


$$\square [f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]' = f(x_1', x_2', \dots, x_n', 1, 0, \bullet, +)$$

$$\square x \leftrightarrow x'; + \leftrightarrow \bullet; 0 \leftrightarrow 1$$

# Example: Complementing $(AB' + C)D' + E$

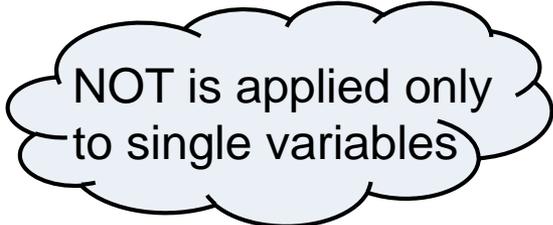1. Iteratively apply DeMorgan's laws:

$$\begin{aligned} [(AB' + C)D' + E]' &= [(AB' + C)D']'E' \\ &= [(AB' + C)' + D]E' \\ &= [(AB')'C' + D]E' \\ &= [(A' + B)C' + D]E' \end{aligned}$$



NOT is applied only to single variables

2. Or, use one-step rule:

$$\begin{aligned} [(AB' + C)D' + E]' &= [(((A \bullet B') + C) \bullet D') + E]' \\ &= (((A' + B) \bullet C') + D) \bullet E' \end{aligned}$$

# Duality

- **Dual:**
  - $[f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]^D = f(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)$ 
    - $+ \leftrightarrow \bullet; 0 \leftrightarrow 1$
- **Cf. DeMorgan's laws:**
  - $[f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]' = f(x_1', x_2', \dots, x_n', 1, 0, \bullet, +)$ 
    - $x \leftrightarrow x'; + \leftrightarrow \bullet; 0 \leftrightarrow 1$
- $\Rightarrow$  **Find the dual of an expression:**
  - Complement the entire expression
  - Complement each individual variable
- e.g.,  $(XYZ\dots)^D = X + Y + Z + \dots$
- e.g.,  $(AB' + C)^D = ?$   
 $(AB' + C)' = (A'+B)C' \Rightarrow (AB' + C)^D = (A+B)C$
- **Application:  $F = G \Leftrightarrow F^D = G^D$**