

Logic design (Fall 2021)

Quiz # 11

Name: \_\_\_\_\_ ID: \_\_\_\_\_

1. (40%) An rising-edge-triggered AB flip-flop has two inputs A, B and one output Q, which operates as follows: When A=0 and B=0, the next clock edge resets Q to 0; when A=1 and B=0, the next clock edge leaves state unchanged; when A=0 and B=1, the next clock edge complements the state; and when A=1 and B=1, the next clock edge sets Q to 1.

(40%) An rising-edge-triggered AB flip-flop has two inputs A, B and one output Q, which operates as follows: When A=0 and B=0, the next clock edge resets Q to 0; when A=0 and B=1, the next clock edge leaves state unchanged; when A=1 and B=0, the next clock edge complements the state; and when A=1 and B=1, the next clock edge sets Q to 1.

(a) (24%) Construct the state table of the AB flip-flop.

(b) (16%) Derive and minimize the next-state equation for the AB flip-flop

Ans:

(a)

A	B	Q(t)	Q(t+ε)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a)

A	B	Q(t)	Q(t+ε)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

(b)  $Q(t+\epsilon) = BQ' + AQ$

(b)  $Q(t+\epsilon) = AQ' + BQ$


Each wrong term would deduct 8 points

Not minimize the equation would deduct 4 points.


e.g.  $Q(t+\epsilon) = BQ + AQ + AB$  would deduct (8+4) points



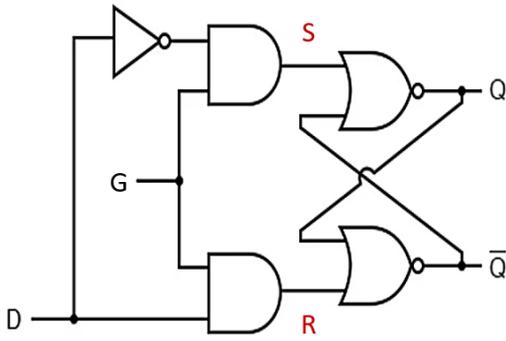Ans: (each wrong signal would deduct 2 points)




Question A

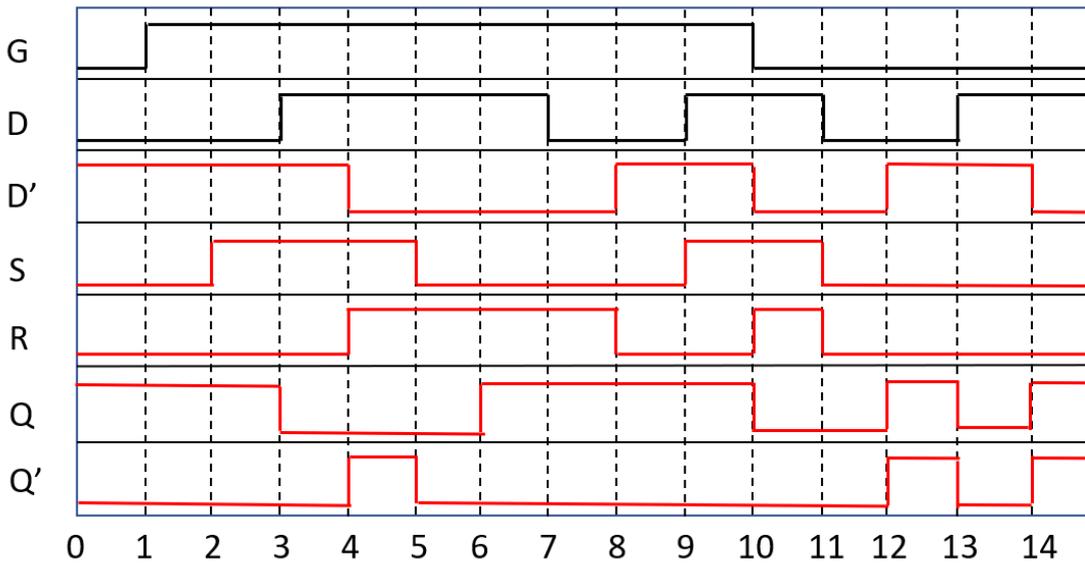

Q: 11100011110010 (1)

Q': 00001000000010 (1)

Question B

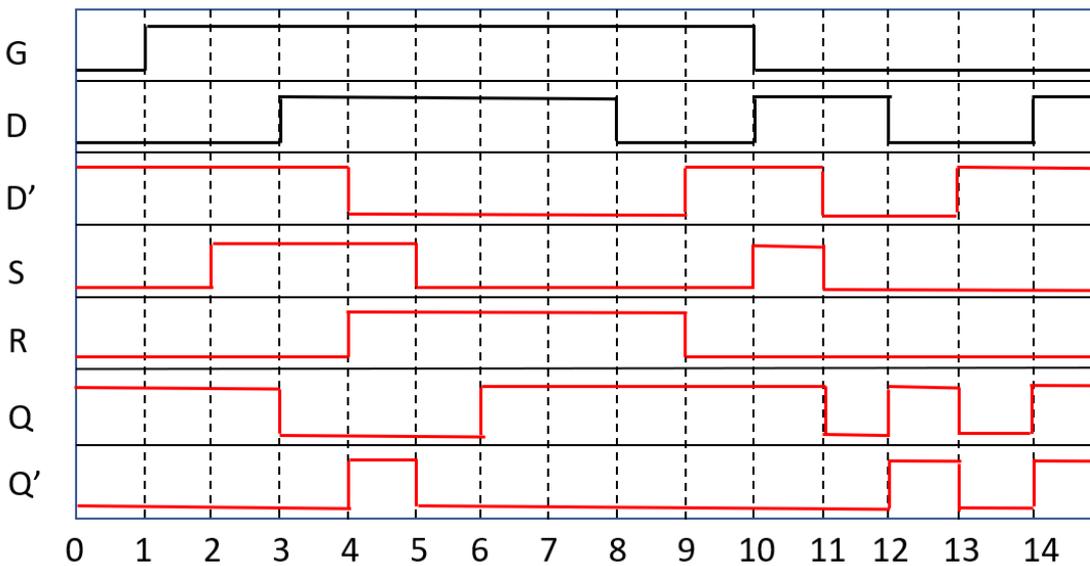

Q: 1110001111010 (1)

Q': 00001000000010 (1)