

Logic design (Fall 2021)  
Quiz # 8

Name: \_\_\_\_\_ ID: \_\_\_\_\_

1. (100%) Given that  $F = \prod M(0, 1, 5, 8, 10, 13, 14, 15)$ , /  $F = \prod M(0, 2, 4, 5, 7, 10, 11, 15)$ ,
- (20%) Find a minimum AND-OR circuit for F. Note that you don't need to draw the AND-OR circuit. Listing the corresponding Boolean expression for the circuit would be enough.
  - (40%) Assuming that only one input signal can change each time, identify all pairs of input patterns that may result in static-1 hazards.
  - (40%) Find an AND-OR circuit for F which has no static-1 hazards. Note that you don't need to draw the AND-OR circuit. Listing the corresponding Boolean expression for the circuit would be enough.

Ans:

(a).  $F = A'C + BC'D' + AB'D$

AB \ CD	00	01	11	10
00	0	1	1	0
01	0	0	0	1
11	1	1	0	1
10	1	1	0	0

- (A, B, C, D): (1, 0, 1, 1) → (0, 0, 1, 1)  
(A, B, C, D): (0, 1, 1, 0) → (0, 1, 0, 0)
- $F = A'C + BC'D' + AB'D + B'CD + A'BD'$

Ans:

(a).  $F = AC' + A'B'D + BCD'$

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	0	1	1
11	1	0	0	0
10	0	1	1	0

(b). (A, B, C, D): (1, 1, 1, 0) → (1, 1, 0, 0)

(A, B, C, D): (1, 0, 0, 1) → (0, 0, 0, 1)

(c).  $F = AC' + A'B'D + BCD' + ABD' + B'C'D$