

Logic design (Fall 2021)

Quiz # 9

Name: _____ ID: _____

1. (40%) Realize the function

$$F(A,B,C,D) = BCD + AB'C' + AB'CD' + ABC'D + AB'C'D'$$


$$F(A,B,C,D) = BCD + AB'C'D + AB'C'D' + AB'D' + ABC'D$$

using only AND gates and NOT(INV) gates and a 4-to-1 multiplexer with A and B as the select inputs where A is the most significant bit and B is the least significant bit. Note that complement inputs are not allowed.

(a) (28%) What is the **logic expression** in each mux inputs?

(using A/B/C/D/A'/B'/C'/D'/0/1 to represent the *logic expression (a) ~ logic expression (d)*)

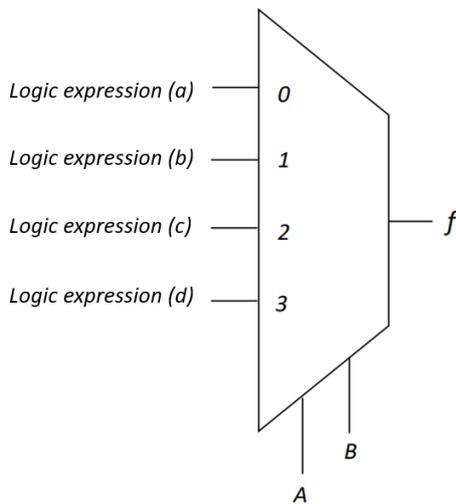(b) (12%) You should use the **minimum** total number of AND gates and NOT gates. How many AND gate and NOT gate you need to use respectively?



Ans:

(a) Logic expression (a): 0

Logic expression (b): CD

Logic expression (c): C'+D'


Logic expression (d): D

(each term would deduct 7 points)

P.s. please simplify the logic expression next time!

(b) 1 AND gate and 1 NOT gate

(each answer would deduct 6 points)

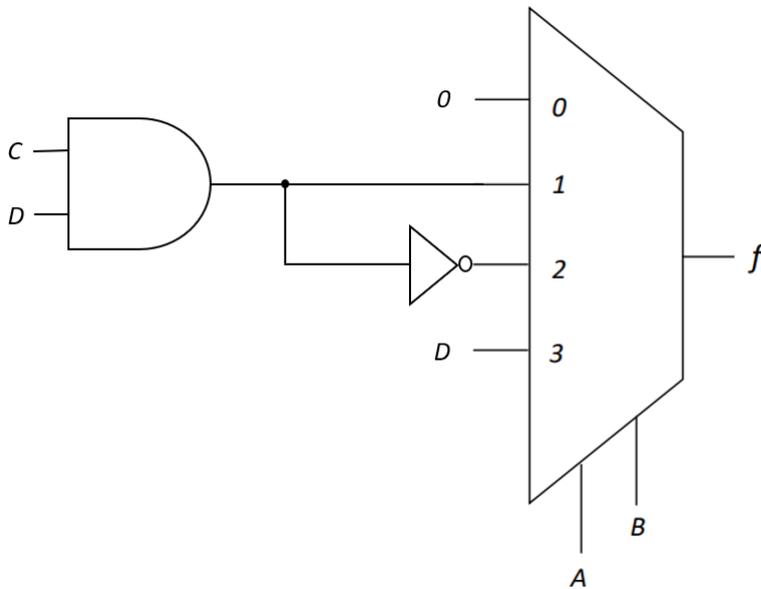

2. (60%) Implement the following equations using the PLA with four product terms only.

$$F1(A,B,C,D) = \prod M(1, 3, 5, 6, 7, 8, 9, 11, 12, 14)$$


$$F2(A,B,C,D) = \prod M(0, 3, 4, 6, 7, 8, 11, 12, 14)$$

$$F1(A,B,C,D) = \sum m(0, 2, 4, 10, 13, 15)$$

$$F2(A,B,C,D) = \sum m(1, 2, 5, 9, 10, 13, 15)$$

(a) (40%) List the four product terms used in the PLA

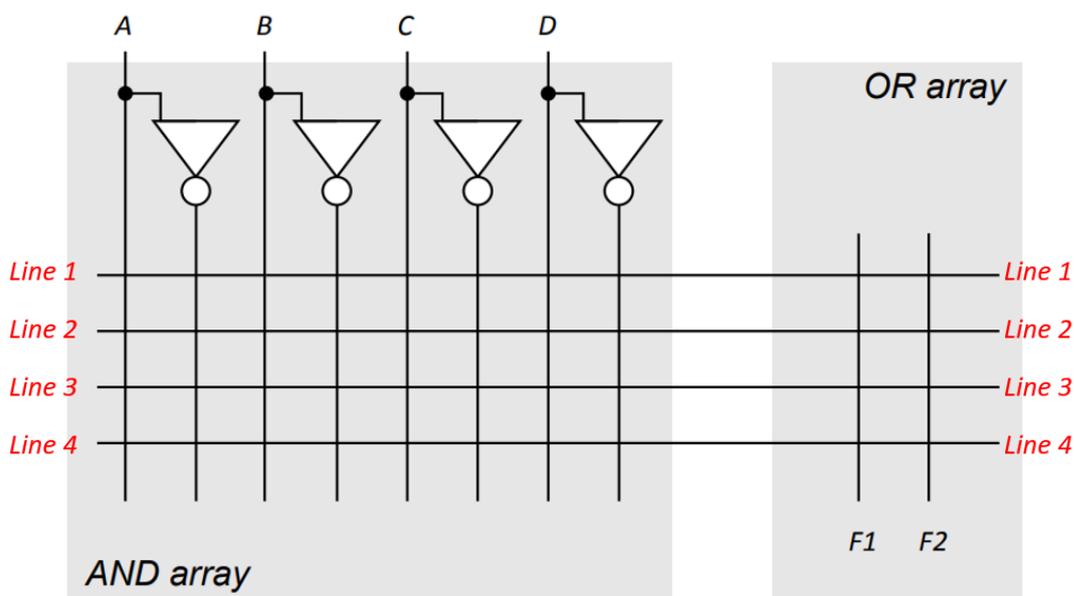(b) (20%) Following shows the PLA structure, of which left and right side are AND array and OR array respectively. The intersection of a row and input or output lines indicates the presence of a switching element in the array. Indicate the connections which will be made to program the PLA
If **Line 1** intersects **A'** and **Line 1** intersects **F1**, use **1A' 1F1** to represent it.



Ans:

$$F1 = A'C'D' + B'CD' + ABD$$

$$F2 = C'D + B'CD' + ABD$$

→ $A'C'D' + B'CD' + ABD + C'D$ (each term deducts 10 points)

	AB			
CD	00	01	11	10
00	1	1	0	0
	0	4	12	8
01	0	0	1	0
	1	5	13	9
11	0	0	1	0
	3	7	15	11
10	1	0	0	1
	2	6	14	10

	AB			
CD	00	01	11	10
00	0	0	0	0
	0	4	12	8
01	1	1	1	1
	1	5	13	9
11	0	0	1	0
	3	7	15	11
10	1	0	0	1
	2	6	14	10

1A' 1C' 1D' 1F1

2B' 2C 2D' 2F1 2F2

3A 3B 3D 3F1 3F2

4C' 4D 4F2

(each line deducts 5 points)

