

UNIT 13

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS



Fall 2021


Clocked Sequential Circuits

2

© Iris H.-R. Jiang


- **Contents**
 - ▣ Analysis by signal tracing & **timing charts**
 - ▣ **State tables and graphs**
 - ▣ General models for sequential circuits
 - ▣ A sequential parity checker
- **Reading**
 - ▣ Unit 13

Basically,
no inputs

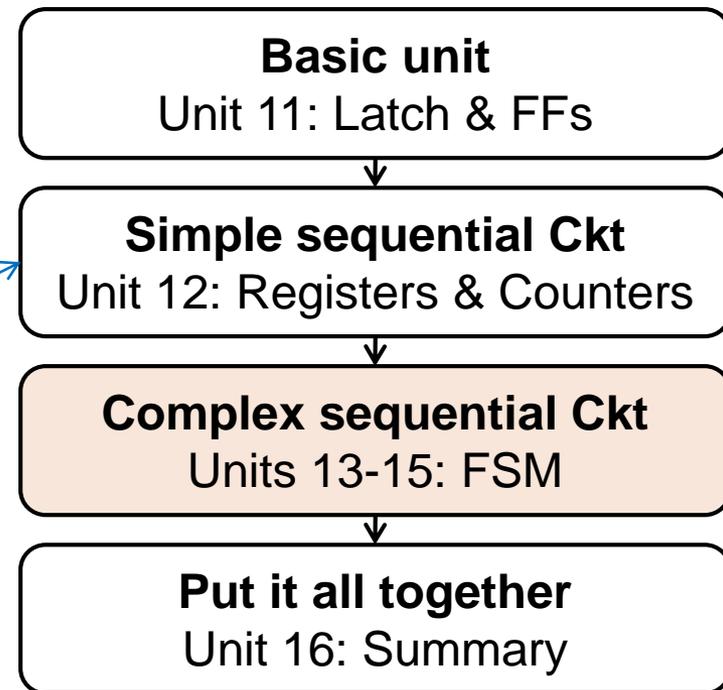

Analysis of Clocked Sequential Circuits

- Find the output sequence resulting from a given input one
 - ⇒ Draw a timing chart to show **inputs**, **clock**, **FF states**, **outputs**
 - 1. Assume an initial state of FFs (reset to 0)
 - 2. Determine the circuit outputs & FF inputs for 1st input pattern
 - 3. Determine the new FF states after the next active clock edge
 - 4. Determine the outputs for the new states
 - 5. Repeat 2—4 for each input pattern

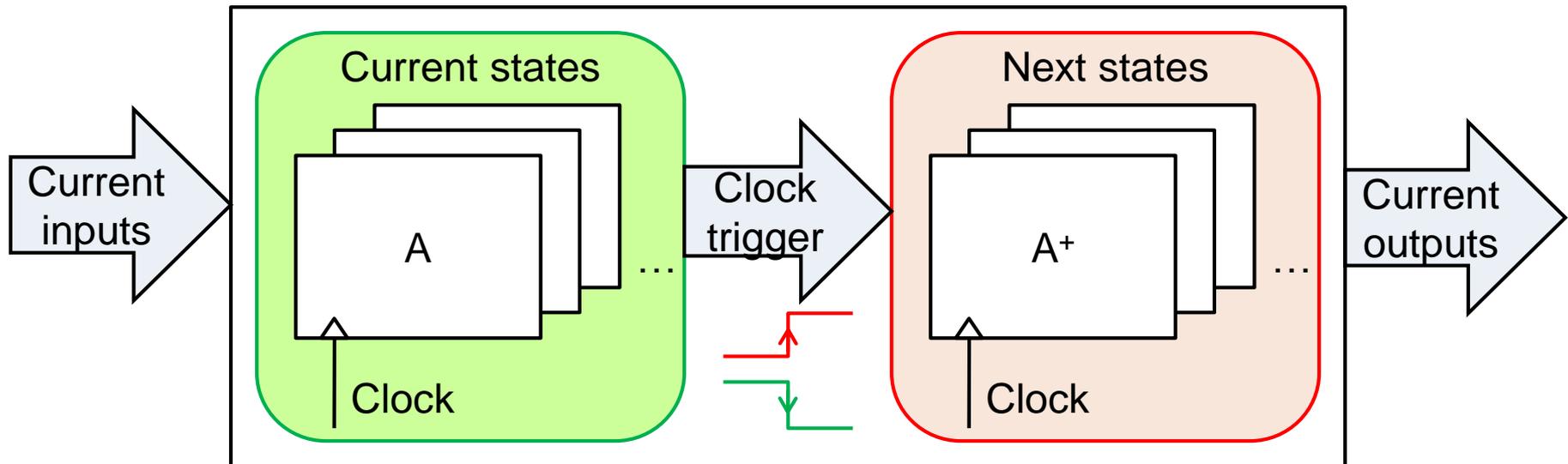

Clocked sequential ckt


4

Two Types of Sequential Circuits & their Timing Charts


Clocked sequential ckt

Type I: Moore Machine

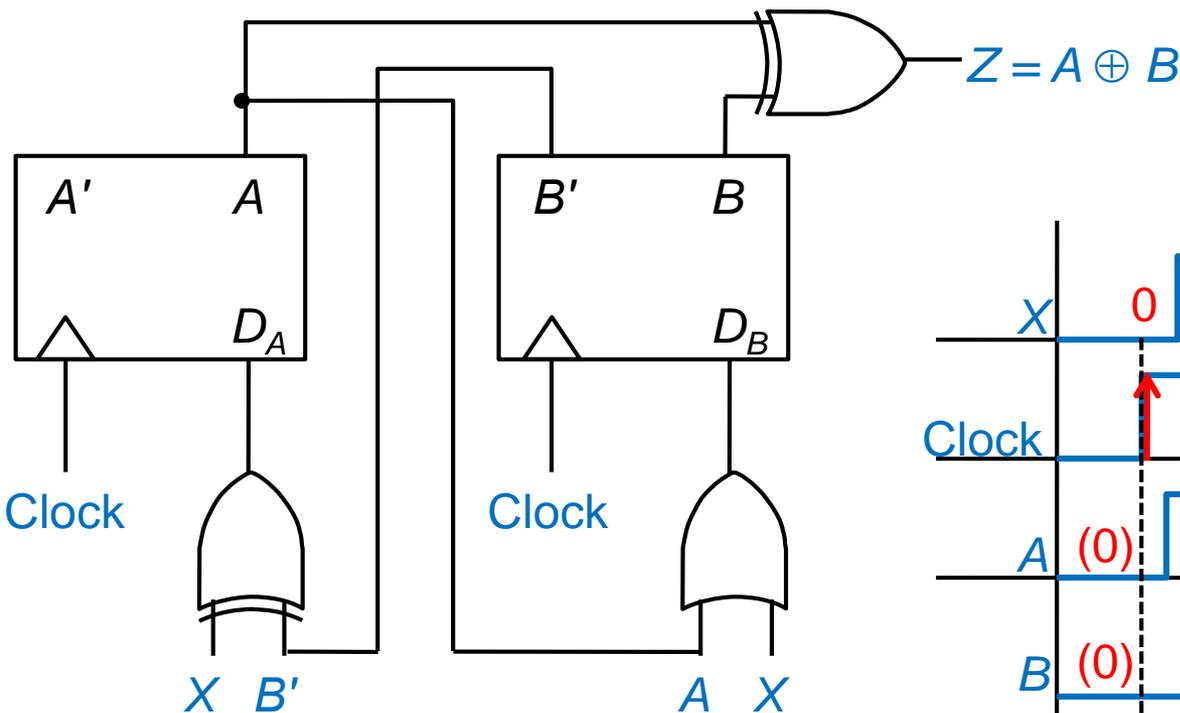- Moore machine: the output depends only on the present state
 - The output which corresponds to a given input appears until after the active clock edge




Clocked sequential ckt

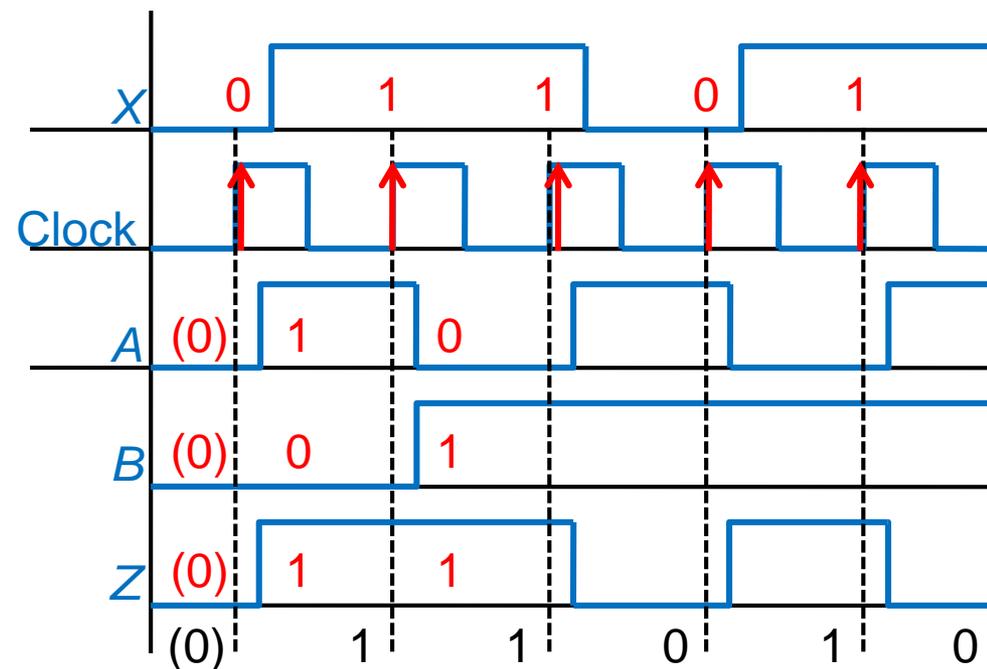


Type II: Mealy Machine

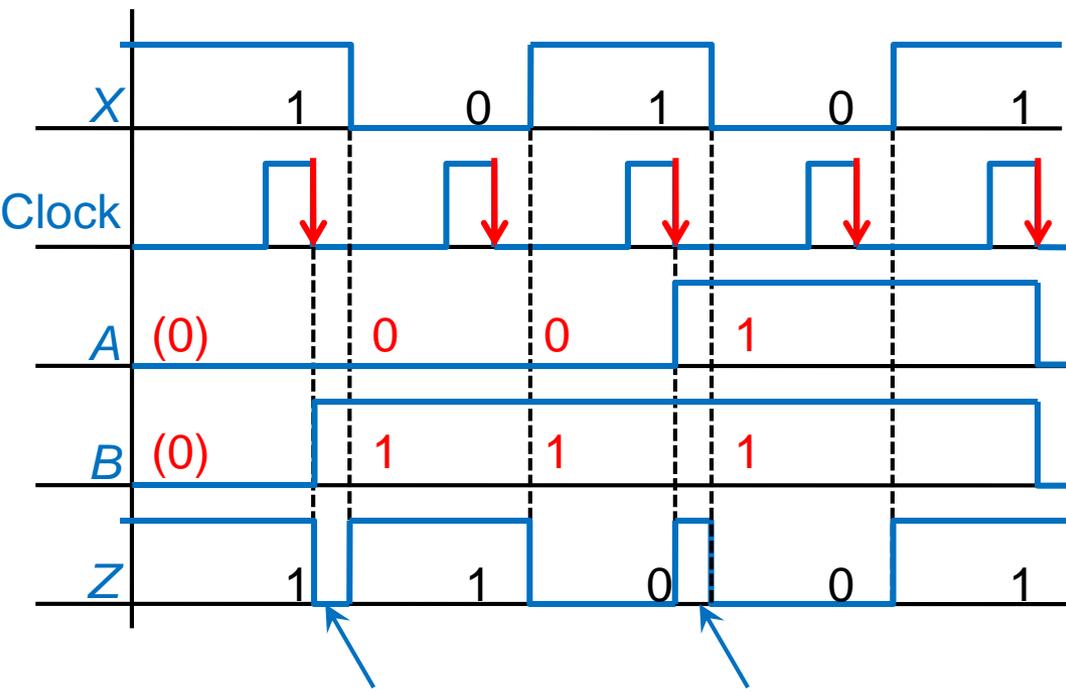- Mealy machine: the output depends on **both the present state and on the inputs**
 - False outputs may occur
 - Glitches and spikes



"False" 0 output "False" 1 output

Clocked sequential ckt

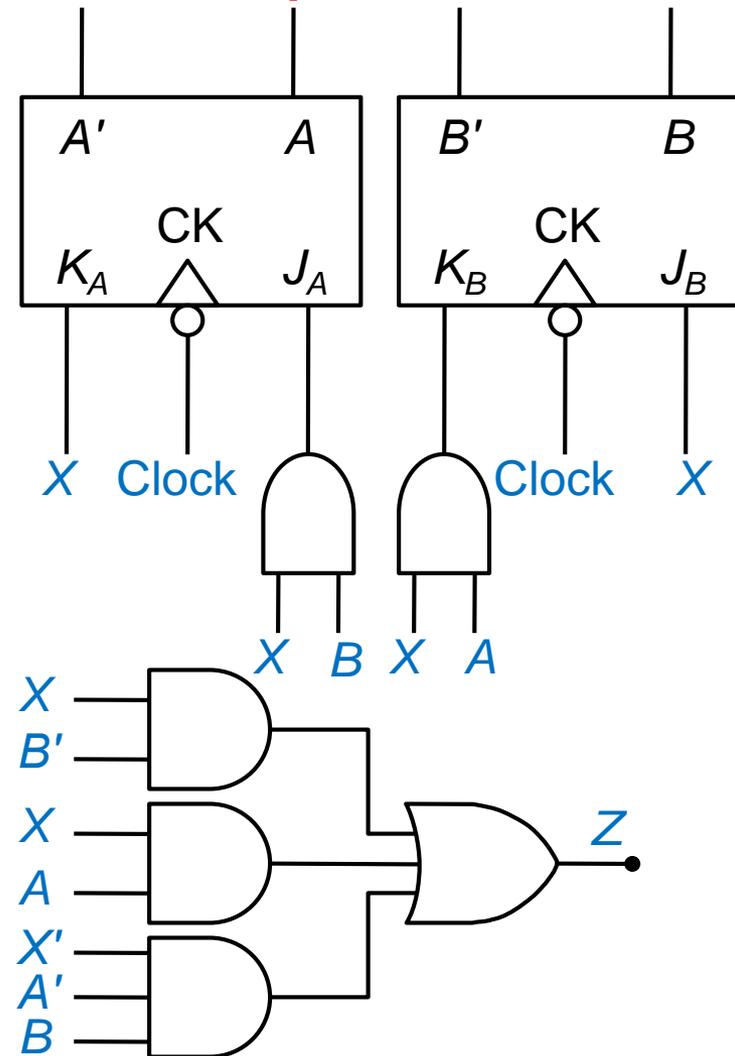


7

State Tables and Graphs

Clocked sequential ckt

How to Construct the State Table?

- The state table specifies

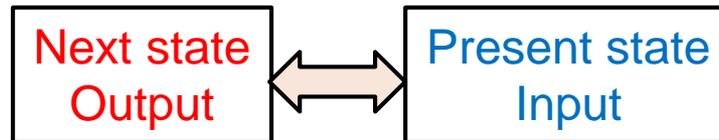


- Procedure to construct the state table **for a given circuit**
 1. Determine the **flip-flop input equations** and the **output equations** from the circuit
 2. Derive the **next-state equation** for each FF from its **input equations**
 3. Plot a **next-state map** for each flip-flop
 4. Combine these maps to form **the state table**

Recap Next-State Equations

Type	Q^+
D FF	$Q^+ = D$
D-CE FF	$Q^+ = D \cdot CE + Q \cdot CE'$
T FF	$Q^+ = T \oplus Q$
S-R FF	$Q^+ = S + R'Q \quad (SR = 0)$
J-K FF	$Q^+ = JQ' + K'Q$

Example: Moore Machine (1/2)

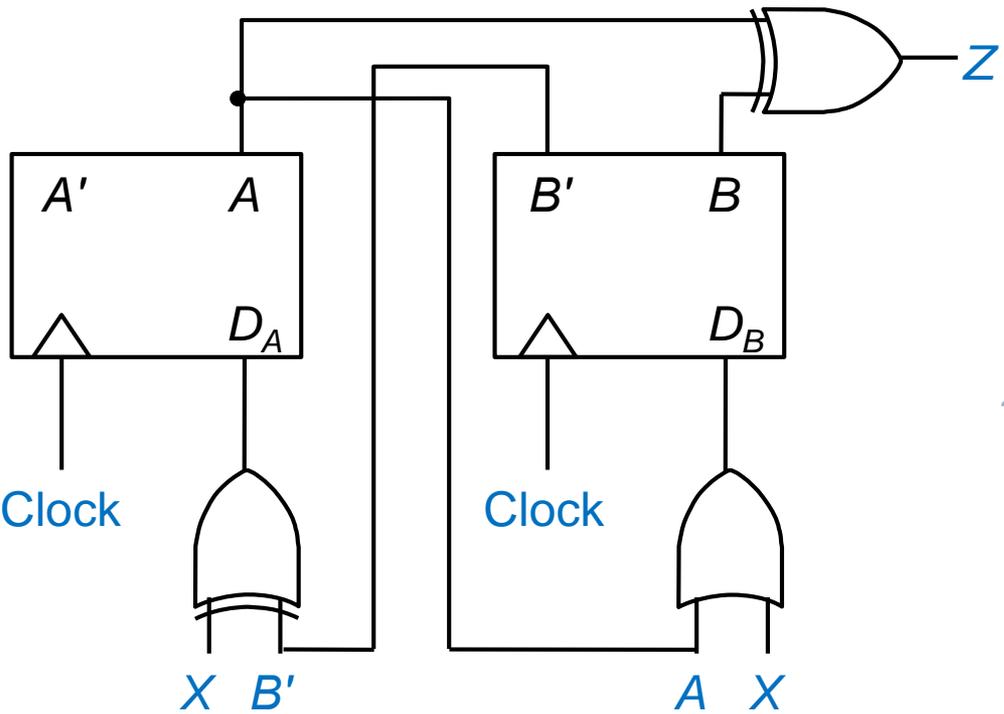1. $D_A = X \oplus B'$ 2. $A^+ = X \oplus B'$
 $D_B = A + X$ $B^+ = A + X$
 $Z = A \oplus B$



3.

AB	X		AB	X	
	0	1		0	1
00	1	0	00	0	1
01	0	1	01	0	1
11	0	1	11	1	1
10	1	0	10	1	1


A^+ B^+

4.

AB	A^+B^+		Z
	X = 0	X = 1	
00	10	01	0
01	00	11	1
11	01	11	0
10	11	01	1

Example: Moore Machine (2/2)


AB	A+B+		Z
	X = 0	X = 1	
00	10	01	0
01	00	11	1
11	01	11	0
10	11	01	1

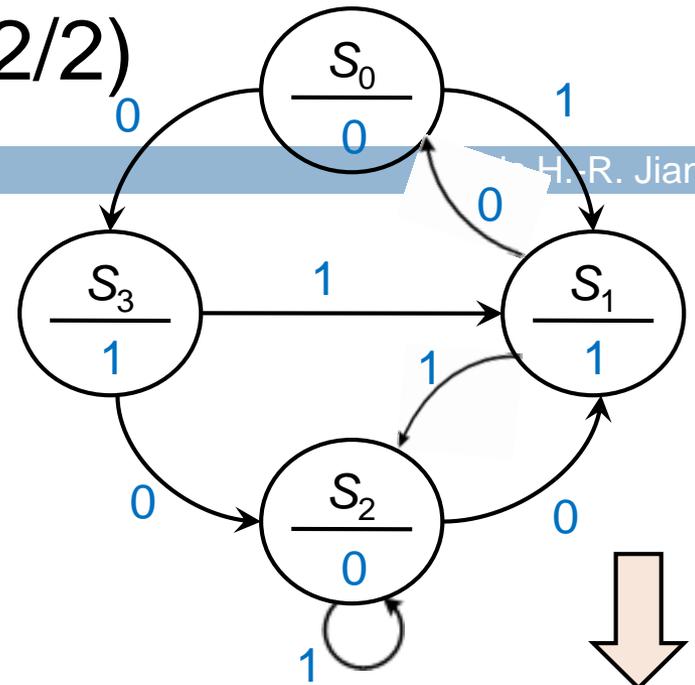

State assignment

State graph


Present state	Next state		Present output (Z)
	X = 0	X = 1	
S ₀	S ₃	S ₁	0
S ₁	S ₀	S ₂	1
S ₂	S ₁	S ₂	0
S ₃	S ₂	S ₁	1

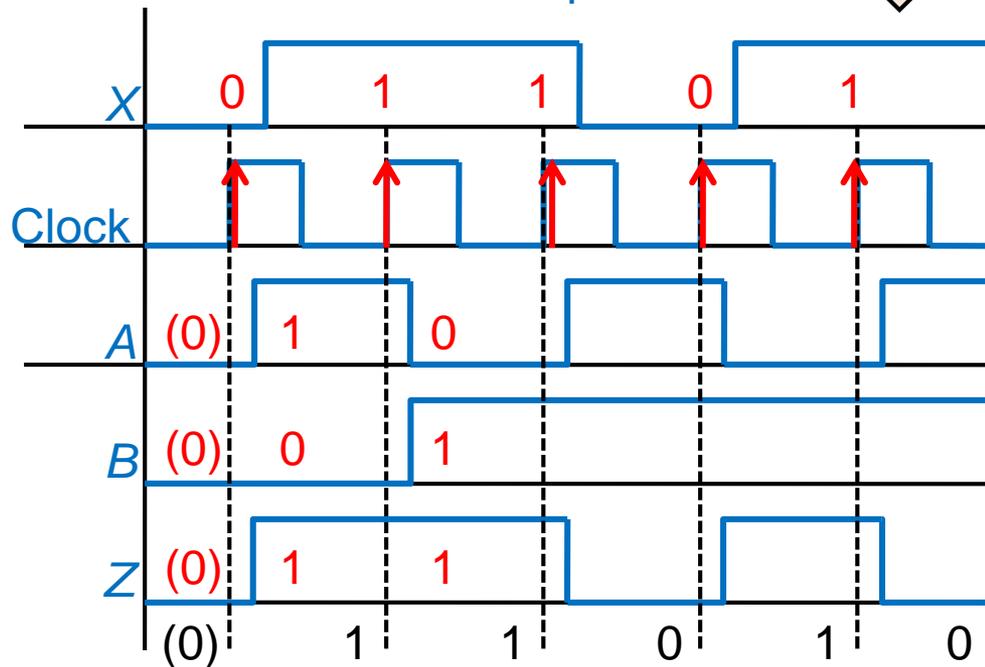

Clocked sequential ckt

Example: Mealy Machine (1/3)

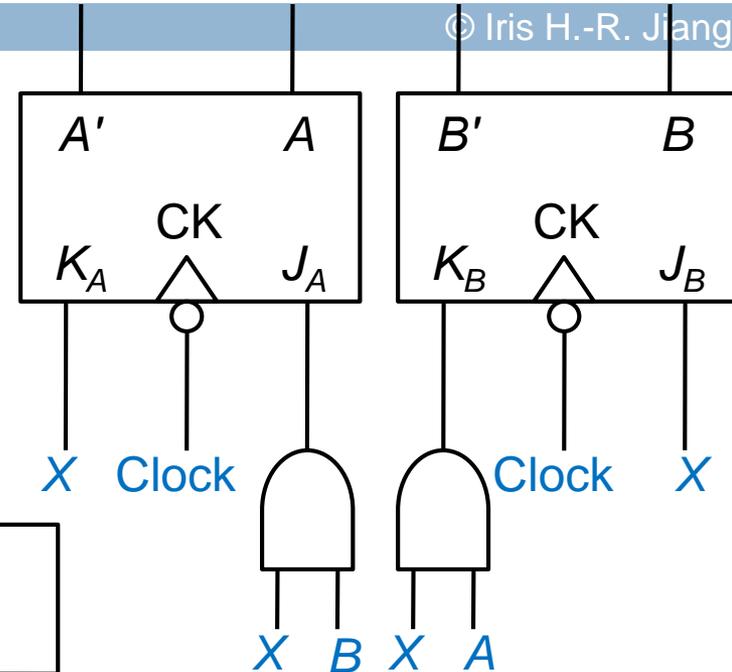1.&2. $A^+ = J_A A' + K_A A = XBA' + X'A$
 $B^+ = J_B B' + K_B B = XB' + (AX)'B$
 $= XB' + A'B + X'B$
 $Z = X'A'B + XA + XB'$



3.

AB \ X	0		1	
	0	1	0	1
00	0	0	0	1
01	0	1	1	1
11	1	0	1	0
10	1	0	0	1


A^+

AB \ X	0		1	
	0	1	0	1
00	0	1	1	1
01	1	1	1	1
11	1	0	1	0
10	0	1	0	1

B^+



AB \ X	0		1	
	0	1	0	1
00	0	1	1	1
01	1	0	1	0
11	0	1	0	1
10	0	1	0	1

Z

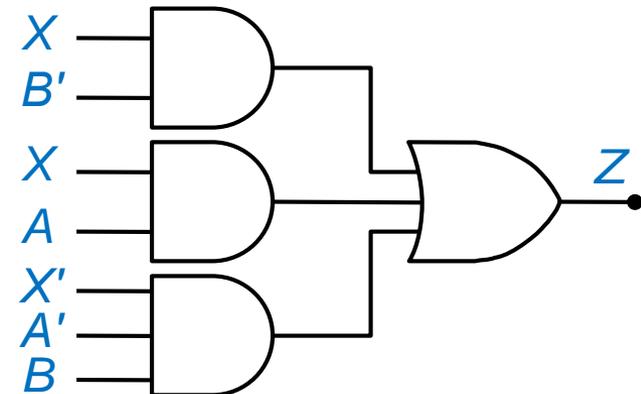

Example: Mealy Machine (2/3)

	X=0		X=1			X=0		X=1			X=0		X=1		
AB	0	1	0	1	AB	0	1	0	1	AB	0	1	0	1	
00	0	0	0	1	00	0	1	0	1	00	0	1	0	1	
01	0	1	1	1	01	1	1	01	1	0	01	1	0	01	0
11	1	0	1	0	11	1	0	11	0	1	11	0	1	11	1
10	1	0	0	1	10	0	1	10	0	1	10	0	1	10	1
	A ⁺					B ⁺					Z				

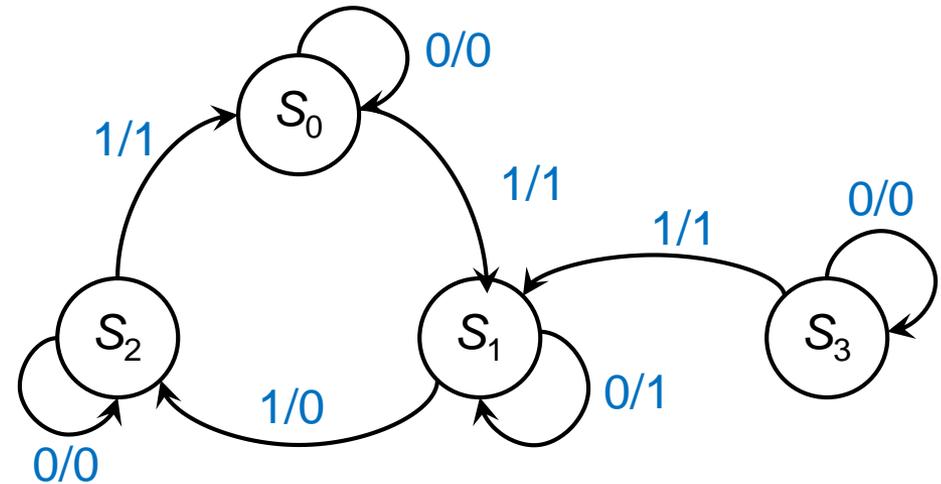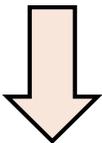

State graph

4.

	A ⁺ B ⁺		Z	
AB	X=0	X=1	X=0	X=1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1


State assignment




Present state	Next state		Present output (Z)	
	X=0	X=1	X=0	X=1
S ₀	S ₀	S ₁	0	1
S ₁	S ₁	S ₂	1	0
S ₂	S ₂	S ₀	0	1
S ₃	S ₃	S ₁	0	1

Clocked sequential ckt

Example: Mealy Machine (3/3)

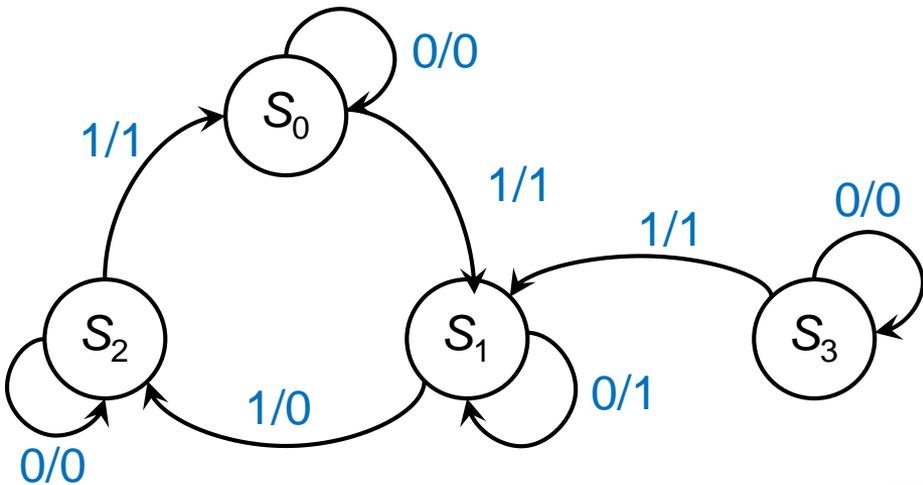

State	AB
S ₀	00
S ₁	01
S ₂	11
S ₃	10

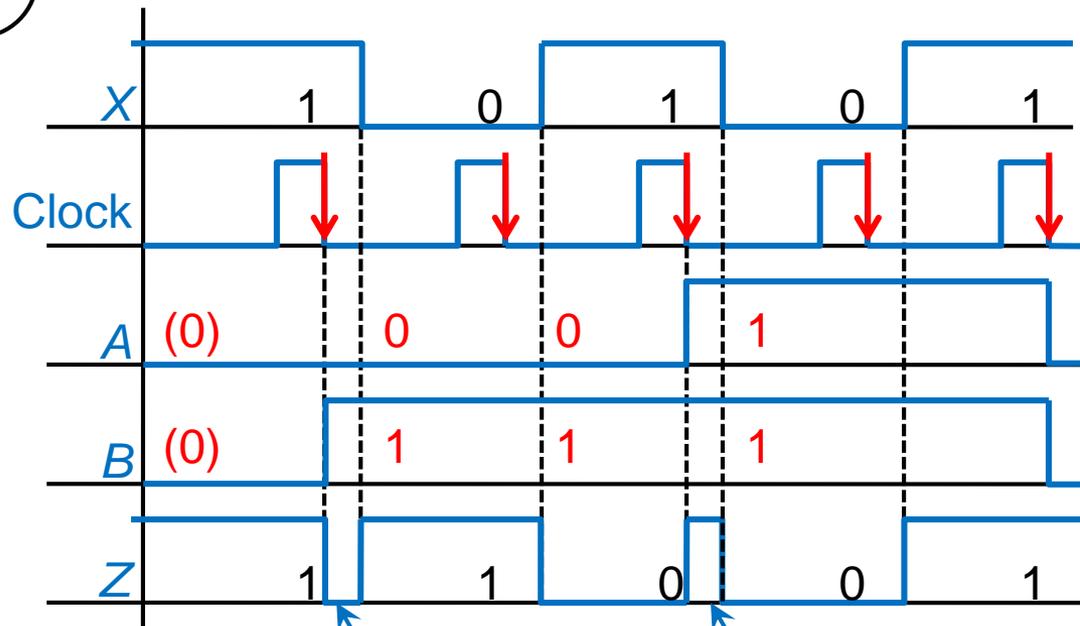


“False” 0 output “False” 1 output

Example: Serial Adder

00/0, 01/1, 10/1

01/0, 10/0, 11/1


$x_i y_i / s_i$

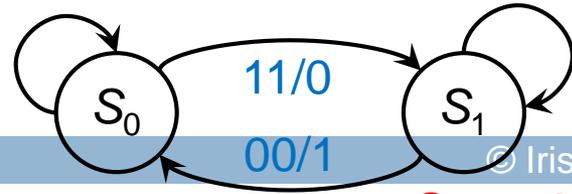

© Iris H.-R. Jiang


$S_0: c_i=0; S_1: c_i=1$

15

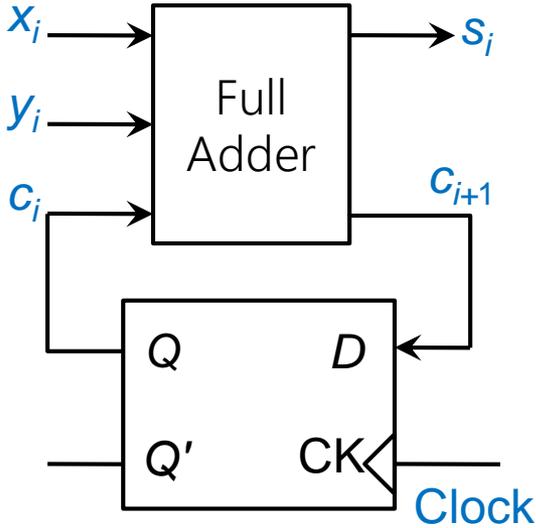

Carry_out (c_{i+1}) is latched in the DFF
The latched Carry_out will be added with the next x_i and y_i


x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

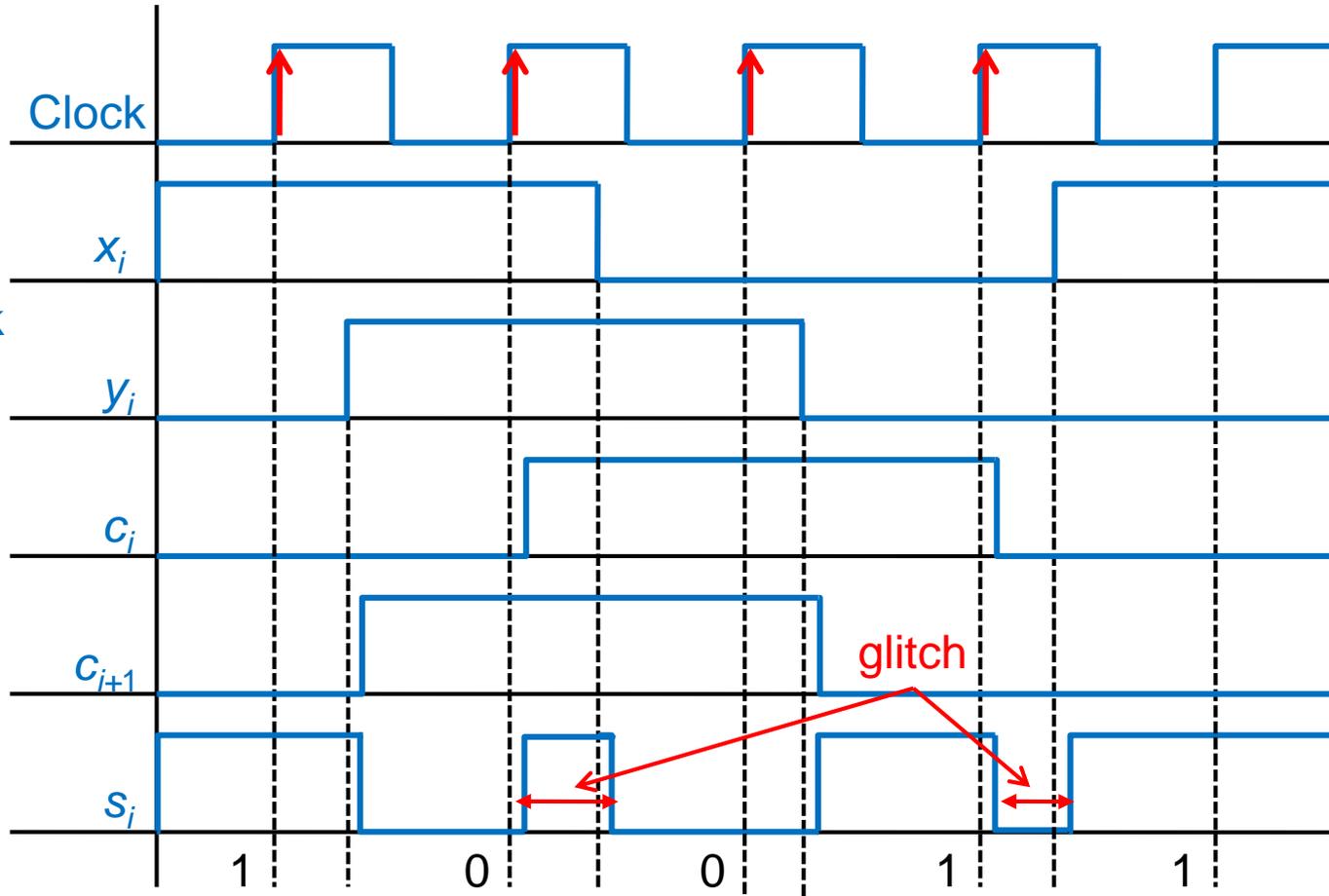

Example: Multiple Inputs and Outputs

Present state	Next state				Present output (Z_1Z_2)			
	$X_1X_2 = 00$	01	10	11	$X_1X_2 = 00$	01	10	11
S_0	S_3	S_2	S_1	S_0	00	10	11	01
S_1	S_0	S_1	S_2	S_3	10	10	11	11
S_2	S_3	S_0	S_1	S_1	00	10	11	01
S_3	S_2	S_2	S_1	S_0	00	00	01	01

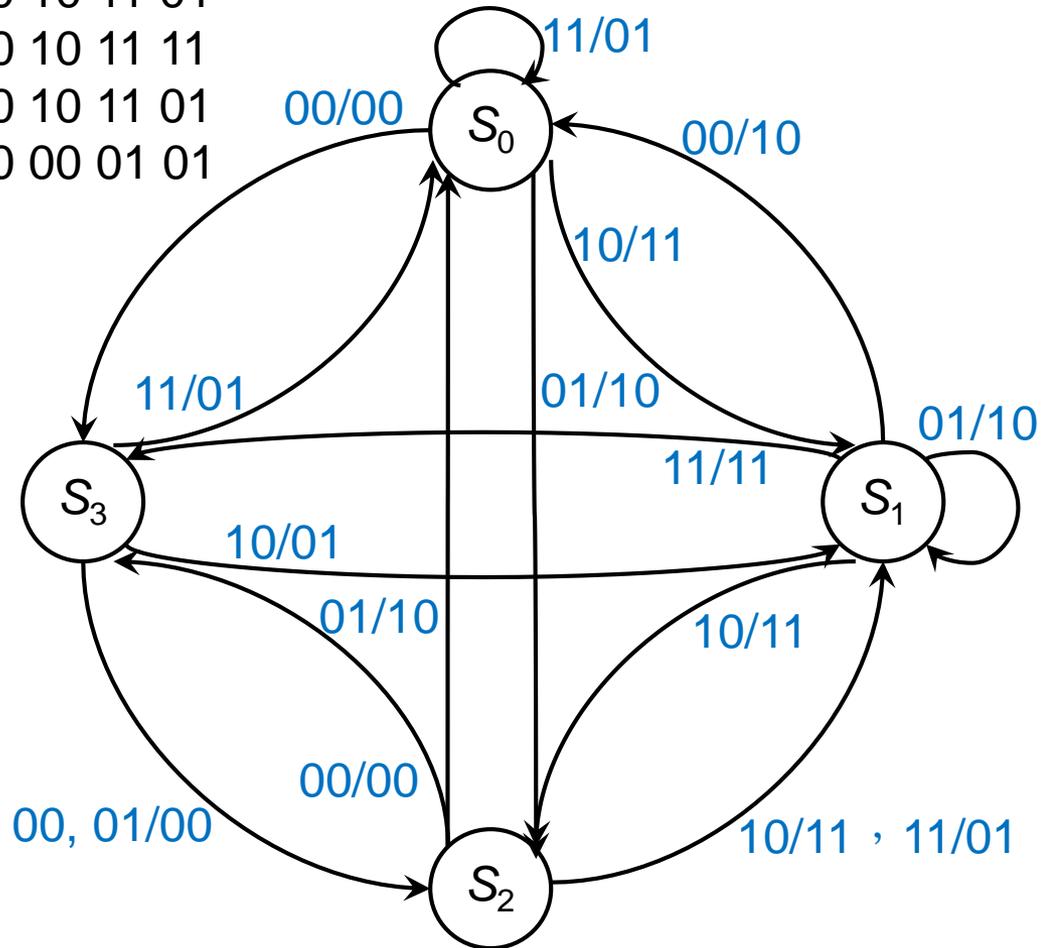Q: Input $X = 03211231122$
 Output $Z = ?$ (check by yourself)
 State transition : $S_0S_3S_0S_1S_1 \dots$



17

General Models


Moore vs. Mealy

General Model for Mealy Machines

18

© Iris H.-R. Jiang

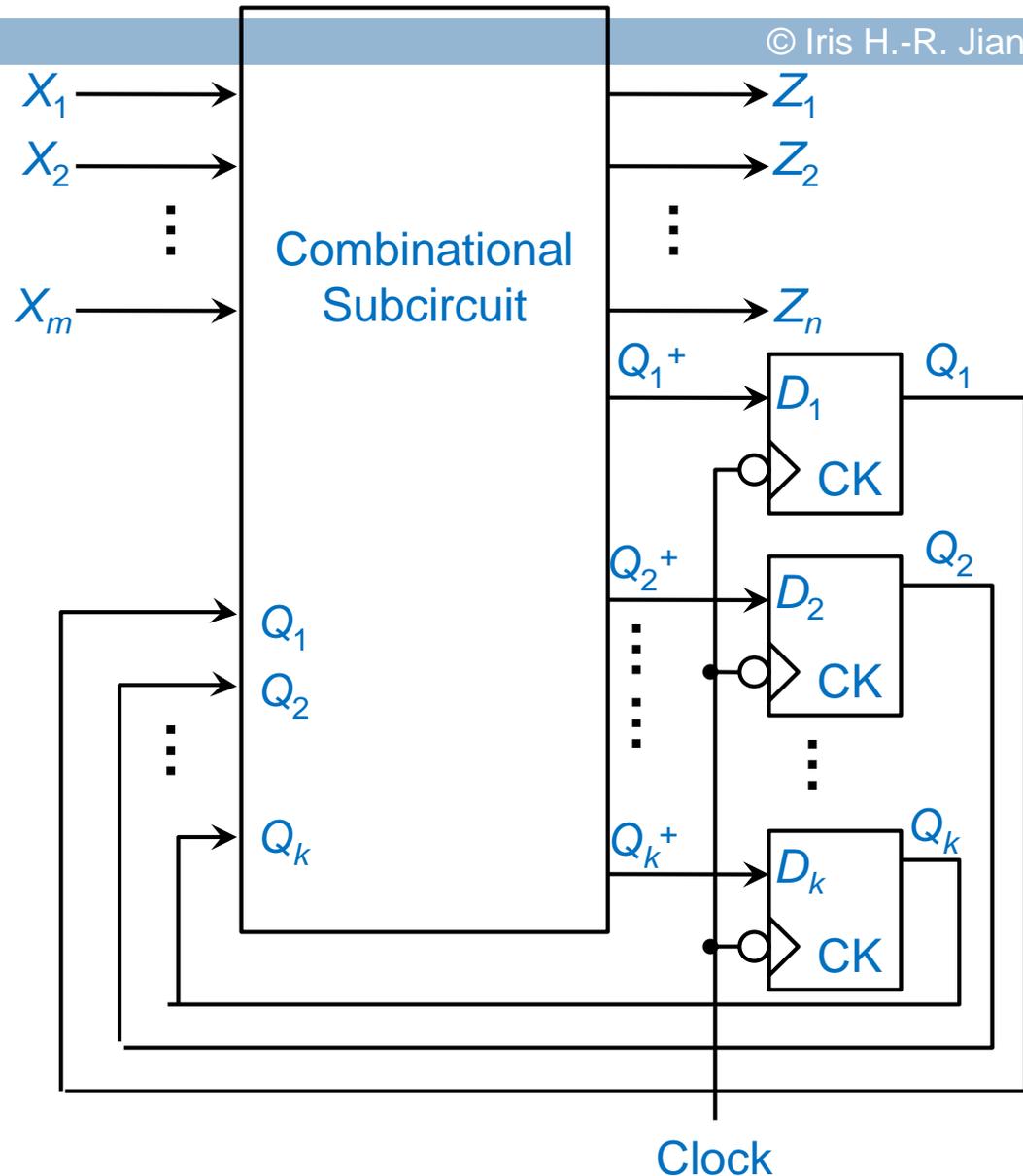
- An output is a function of **states and inputs**



Clocked sequential ckt

General Model for Moore Machines

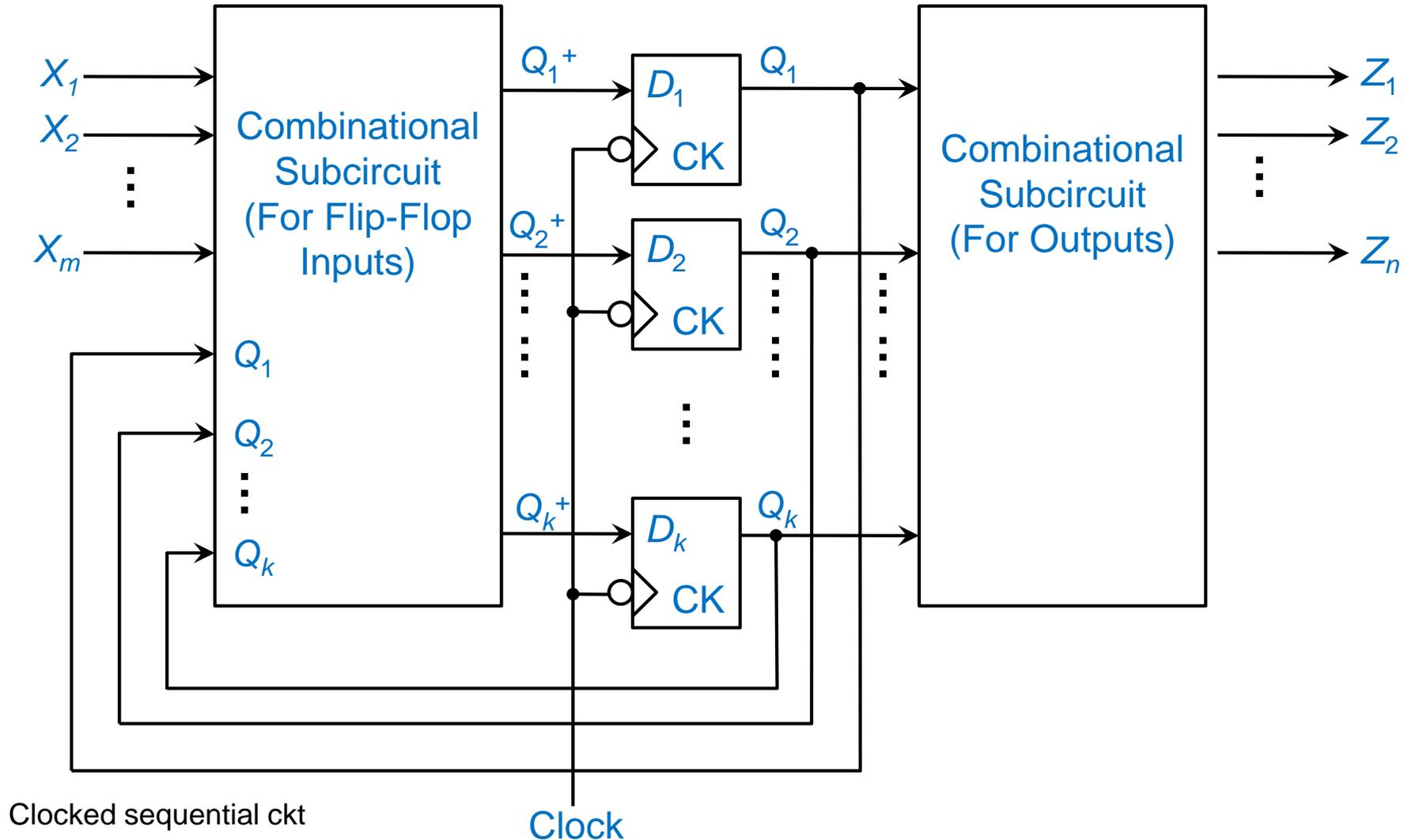- An output is a function of **only states**



20

Case Study: A Sequential Parity Checker

Clocked sequential ckt

Parity Checker (1/3)

- **Error detection:** add an extra bit (**parity bit**) when transmitting or storing binary data
 - ▣ When the **total # of 1 bits** in the block (data bits + parity bit) is **odd** (**even**), we say the parity is **odd** (**even**)


Even parity		Odd parity	
0000000	0	0000000	1
0000001	1	0000001	0
0110110	0	0110110	1
1010101	0	1010101	1
0111000	1	0111000	0

Data bits Parity bits


Parity Checker (2/3)

□ Design an odd-parity checker

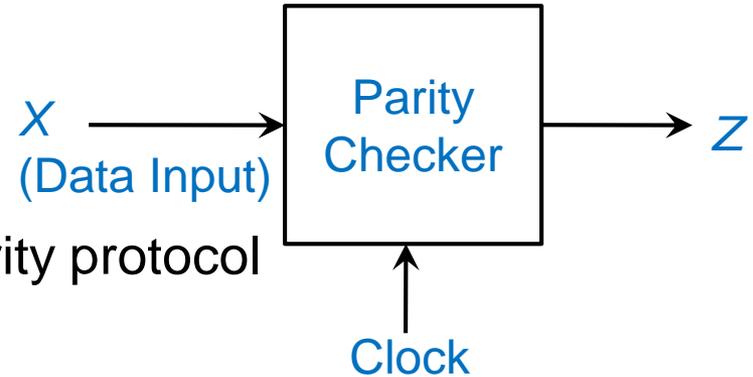- $Z=1$ if total # of 1's is **odd**
- $Z=0$ if total # of 1's is **even**
 - $Z=0 \Rightarrow$ **an error** occurs in odd-parity protocol
 - Initially, $Z = 0$




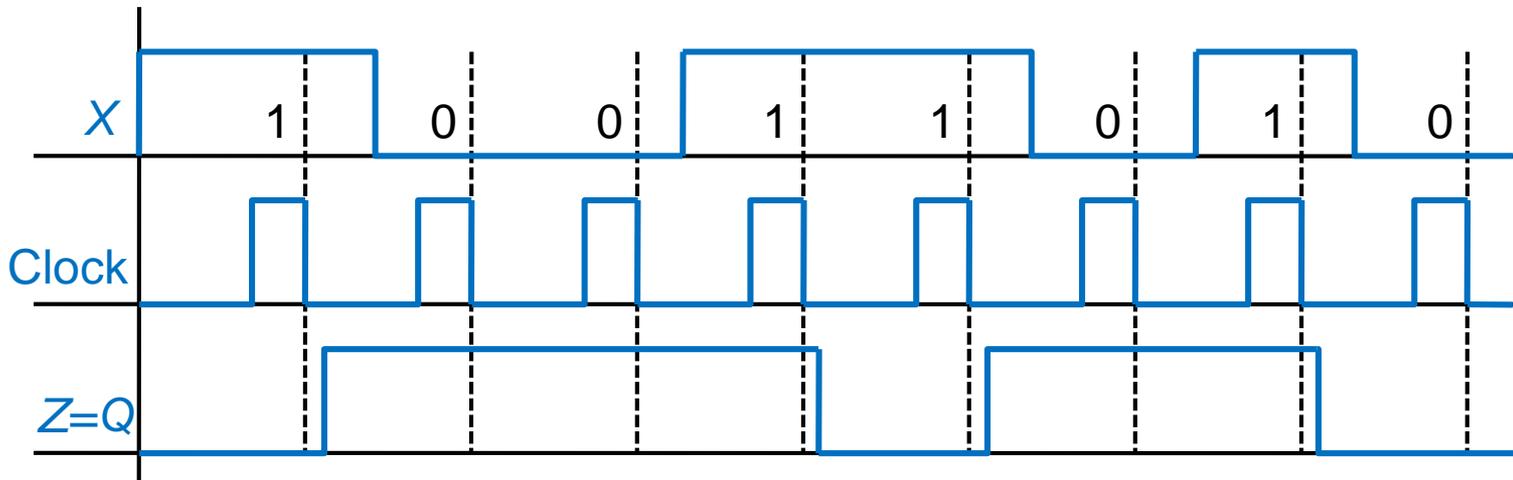□ Timing chart of the odd parity checker (active-low)




Parity Checker (3/3)

State graph

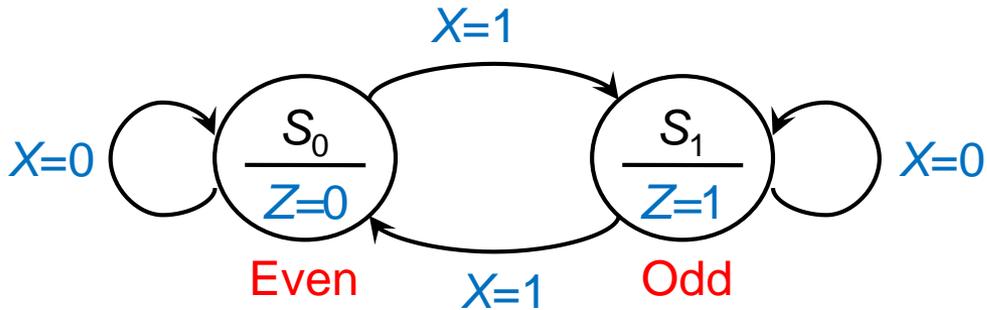

State table

Present state	Next state		Present output (Z)
	$X=0$	$X=1$	
S_0	S_0	S_1	0
S_1	S_1	S_0	1

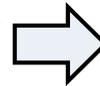

Q	Q^+		Z
	$X=0$	$X=1$	
0	0	1	0
1	1	0	1

Implementation

