

UNIT 16

SEQUENTIAL CIRCUIT DESIGN



Fall 2021


Sequential Circuit Design

- **Contents**


- Summary of design procedure for sequential circuits
- Design example—code converter
 - Design of sequential circuits using ROMs and PLAs
- Design of iterative circuits
 - Design of a comparator

- **Reading**

- Unit 16

 

Designing a Sequential Circuit

 


4 Design Example—Code Converter

BCD to Excess-3 Conversion

□ **BCD \Rightarrow excess-3**

 - ▣ Add 3 to BCD (0~9)
- ▣ Serial I/O with the **LSB** first
 - $X_0 \rightarrow X_1 \rightarrow X_2 \rightarrow X_3$
 - $Z_0 \rightarrow Z_1 \rightarrow Z_2 \rightarrow Z_3$
- ▣ Reset to initial state after receiving 4 inputs




X Input (BCD)	Z Output (excess-3)
time: $t_3 t_2 t_1 t_0$	$t_3 t_2 t_1 t_0$
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
(1010~1111)	x x x x

Serial Code Conversion (2/8)

□ **State table**

time	Input	Present state	Next state		Present Output (Z)	
	sequence (LSB first)		X = 0	X = 1	X = 0	X = 1
t_0	reset	A	B	C	1	0
t_1	0	B	D	F	1	0
	1	C	E	G	0	1
t_2	00	D	H	L	0	1
	01	E	I	M	1	0
	10	F	J	N	1	0
	11	G	K	P	1	0
t_3	000	H	A	A	0	1
	001	I	A	A	0	1
	010	J	A	-	0	-
	011	K	A	-	0	-
	100	L	A	-	0	-
	101	M	A	-	1	-
	110	N	A	-	1	-
	111	P	A	-	1	-

 

Seq. ckt design

Serial Code Conversion (3/8)

State reduction

- ▣ Row matching
- ▣ Use don't cares
 - $M \equiv N \equiv P$
 - $H \equiv I \equiv J \equiv K \equiv L$
 - $E \equiv F \equiv G$

time	Input	Present state	Next state		Present Output (Z)	
	sequence (LSB first)		X = 0	X = 1	X = 0	X = 1
t_0	reset	A	B	C	1	0
t_1	0	B	D	E F	1	0
	1	C	E	E G	0	1
t_2	00	D	H	H L	0	1
	01	E	H V	M	1	0
	10	F	H V	M N	1	0
	11	G	H K	M P	1	0
t_3	000	H	A	A	0	1
	001	I	A	A	0	1
	010	J	A	-	0	-
	011	K	A	-	0	-
	100	L	A	-	0	-
	101	M	A	-	1	-
	110	N	A	-	1	-
	111	P	A	-	1	-

Serial Code Conversion (4/8)

- **Reduced state table**
 - 7 states

time	Present state	Next state		Present Output (Z)	
		X = 0	X = 1	X = 0	X = 1
t_0	A	B	C	1	0
t_1	B	D	E	1	0
	C	E	E	0	1
t_2	D	H	H	0	1
	E	H	M	1	0
t_3	H	A	A	0	1
	M	A	-	1	-

Serial Code Conversion (5/8)

10

00

01

11

10

	Q_1	0	1
$Q_2 Q_3$	00	A	B
	01		C
	11	H	D
	10	M	E

H.-R. Jiang

State assignment

7 states \Rightarrow 3 FFs

time	Present state	Next state		Output (Z)	
		X=0	X=1	X=0	X=1
t_0	A	B	C	1	0
t_1	B	D	E	1	0
	C	E	E	0	1
t_2	D	H	H	0	1
	E	H	M	1	0
t_3	H	A	A	0	1
	M	A	-	1	-

\Rightarrow Transition table

	$Q_1 Q_2 Q_3$	$Q_1^+ Q_2^+ Q_3^+$		Z	
		X=0	X=1	X=0	X=1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	x x x	1	x
-	001	x x x	x x x	x	x

(6/8)

11

- Choose D FFs
- Derive FF input eq. & output eq.

	$Q_1 Q_2 Q_3$	$Q_1^+ Q_2^+ Q_3^+$		Z	
		X=0	X=1	X=0	X=1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	xxx	1	x
-	001	xxx	xxx	x	x

© Iris H.-R. Jiang

$Q_2 Q_3 \backslash XQ_1$	00	01	11	10
00	1	1	1	1
01	x	1	1	x
11	0	0	0	0
10	0	0	0	x

$Q_2 Q_3 \backslash XQ_1$	00	01	11	10
00	0	1	1	0
01	x	1	1	x
11	0	1	1	0
10	0	1	1	x

$$D_1 = Q_1^+ = Q_2'$$

$$D_2 = Q_2^+ = Q_1$$

Seq. ckt design

(7/8)

12

- Choose D FFs
- Derive FF input eq. & output eq.

	$Q_1 Q_2 Q_3$	$Q_1^+ Q_2^+ Q_3^+$		Z	
		X=0	X=1	X=0	X=1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	xxx	1	x
-	001	xxx	xxx	x	x

© Iris H.-R. Jiang

$Q_2 Q_3 \backslash XQ_1$	00	01	11	10
00	0	1	0	1
01	x	0	0	x
11	0	1	1	0
10	0	1	0	x

$Q_2 Q_3 \backslash XQ_1$	00	01	11	10
00	1	1	0	0
01	x	0	1	x
11	0	0	1	1
10	1	1	0	x


$$D_3 = Q_3^+ = Q_1 Q_2 Q_3 + X' Q_1 Q_3' + X Q_1' Q_2'$$

Seq. ckt des

$$Z = X' Q_3' + X Q_3$$

Serial Code Conversion (8/8)

Realize circuit

 

Sequential CKTs Using ROMs and PLAs

Combinational circuits

ROM/PLA

States

FFs

Output function

ROM/PLA

Sequential Circuit Design with ROMs/PLAs

□ BCD to excess-3 code converter

□ State table


Present state	Next state		Present Output (Z)	
	X = 0	X = 1	X = 0	X = 1
A	B	C	1	0
B	D	E	1	0
C	E	E	0	1
D	H	H	0	1
E	H	M	1	0
H	A	A	0	1
M	A	-	1	-

□ Transition table

	$Q_1 Q_2 Q_3$	$Q_1^+ Q_2^+ Q_3^+$		Z	
		X = 0	X = 1	X = 0	X = 1
A	000	001	010	1	0
B	001	011	100	1	0
C	010	100	100	0	1
D	011	101	101	0	1
E	100	101	110	1	0
H	101	000	000	0	1
M	110	000	x x x	1	x
-	111	x x x	x x x	x	x


Using a ROM and D FFs? (1/2)

 - Realize it using a ROM and D FFs
 - ▣ Realize D FF input eq. and output eq. by a ROM



X	Q_1	Q_2	Q_3	Z	D_1	D_2	D_3
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	1
0	1	0	0	1	1	0	1
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	x	x	x	x
1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	1	1	0
1	1	0	1	1	0	0	0
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

Using a ROM and D FFs? (2/2)

 

Using a PLA and D FFs? (1/2)

- Realize it using a PLA and D FFs
 - ▣ Realize D FF input eq. by a PLA

XQ_1		00	01	11	10
Q_2Q_3	00	1	1	1	1
	01	x	1	1	x
	11	0	0	0	0
	10	0	0	0	x

$$D_1 = Q_1 + Q_2'$$

XQ_1		00	01	11	10
Q_2Q_3	00	0	1	1	0
	01	x	1	1	x
	11	0	1	1	0
	10	0	1	1	x

$$D_2 = Q_2 + Q_1$$

XQ_1		00	01	11	10
Q_2Q_3	00	0	1	0	1
	01	x	0	0	x
	11	0	1	1	0
	10	0	1	0	x

$$D_3 = Q_3 + Q_1 Q_2 Q_3 + X' Q_1 Q_3' + X Q_1' Q_2'$$

XQ_1		00	01	11	10
Q_2Q_3	00	1	1	0	0
	01	x	0	1	x
	11	0	0	1	1
	10	1	1	0	x

$$Z = X' Q_3' + X Q_3$$

$$D_1 = Q_1 + Q_2'$$

$$D_2 = Q_2 + Q_1$$

$$D_3 = Q_3 + Q_1 Q_2 Q_3 + X' Q_1 Q_3' + X Q_1' Q_2'$$

$$Z = X' Q_3' + X Q_3$$

Using a PLA and D FFs? (2/2)

$$D_1 = Q_1 + Q_2'$$


$$D_2 = Q_2 + Q_1$$

$$D_3 = Q_3 + Q_1 Q_2 Q_3 + X' Q_1 Q_3' + X Q_1' Q_2'$$

$$Z = X' Q_3' + X Q_3$$

Product term	Inputs				Outputs			
	<i>X</i>	<i>Q</i> ₁	<i>Q</i> ₂	<i>Q</i> ₃	<i>Z</i>	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
<i>Q</i> ₂ '	-	-	0	-	0	1	0	0
<i>Q</i> ₁	-	1	-	-	0	0	1	0
<i>Q</i> ₁ <i>Q</i> ₂ <i>Q</i> ₃	-	1	1	1	0	0	0	1
<i>X</i> ' <i>Q</i> ₁ <i>Q</i> ₃ '	0	1	-	0	0	0	0	1
<i>X</i> <i>Q</i> ₁ ' <i>Q</i> ₂ '	1	0	0	-	0	0	0	1
<i>X</i> ' <i>Q</i> ₃ '	0	-	-	0	1	0	0	0
<i>X</i> <i>Q</i> ₃	1	-	-	1	1	0	0	0

AND plane
OR plane

 


20

Design of Iterative Circuits

A comparator

Iterative Circuits

 - An **iterative circuit** consists of a number of **identical cells** interconnected by a **regular structure**
 - ▣ The design is very similar to that of a sequential circuit
 - ▣ The simplest form: a unilateral iterative circuit
 - A linear array of combinational cells
 - Signals between cells traveling in only one direction
 - **Parallel-input parallel-output**



Design of a Sequential Comparator (1/5)


Form of iterative circuit for comparing binary numbers

- $X = x_1x_2x_3 \dots x_n$

- $Y = y_1y_2y_3 \dots y_n$

time $t_1 t_2 t_3 \dots t_n$

x_1, y_1 : MSB (most significant bit)

 

Have to wait for
 a_i and b_i and
then compare

Design of a Sequential Comparator (2/5)

□ **State table**

S_i	S_{i+1}				$Z_1 Z_2 Z_3$
	$x_i y_i = 00$	01	11	10	
$X=Y$ S_0	S_0	S_2	S_0	S_1	0 1 0
$X>Y$ S_1	S_1	S_1	S_1	S_1	0 0 1
$X<Y$ S_2	S_2	S_2	S_2	S_2	1 0 0

$Z_1(X < Y)$
 $Z_2(X = Y)$
 $Z_3(X > Y)$


□ **Transition table**

▣ State assignment: $S_0:00$ $S_1:01$ $S_2:10$


$a_i b_i$	$a_{i+1} b_{i+1}$				$Z_1 Z_2 Z_3$
	$x_i y_i = 00$	01	11	10	
$X=Y$ 00	00 10	00 01			0 1 0
$X>Y$ 01	01 01	01 01			0 0 1
$X<Y$ 10	10 10	10 10			1 0 0

Design of a Sequential Comparator (3/5)

□ **Typical cell**

 


□ **Output**

 


Design of a Sequential Comparator (4/5)

- **Circuit**
 - ▣ Typical cell

 

- ▣ Output ckt

 

Design of a Sequential Comparator (5/5)

Complete circuit


- $X = x_1x_2x_3 \dots x_n$

- $Y = y_1y_2y_3 \dots y_n$

time $t_1 t_2 t_3 \dots t_n$

x_1, y_1 : MSB (most significant bit)

x_n, y_n : LSB (least significant bit)

 

Summary: Designing a Sequential Circuit

