

UNIT 2

BOOLEAN ALGEBRA



Fall 2021

Boolean Algebra

- **Contents**
 - ▣ Introduction
 - ▣ Basic operations
 - ▣ Boolean expressions and truth tables
 - ▣ Theorems and laws
 - Basic theorems
 - Commutative, associative, and distributive laws
 - Simplification theorems
 - Multiplying out and factoring
 - DeMorgan's laws
- **Reading**
 - ▣ Unit 2

Introduction

□ Boolean algebra

- Is the basic mathematics for logic design of digital systems
- Differs from ordinary algebra in the **values**, **operations**, and **laws**

□ History


- **George Boole** developed Boolean algebra in 1847 and used it to solve problems in mathematical logic
 - British mathematician and philosopher
- **Claude Shannon** first applied Boolean algebra to the design of switching circuits in 1939
 - American electrical engineer and mathematician
 - Master's thesis (21 years-old)

□ In this unit, you will learn how to...

- Use a truth table
- Manipulate basic operations and apply laws of Boolean algebra
- Relate Boolean expressions to basic logic gates

Switching Circuit & Boolean Variables

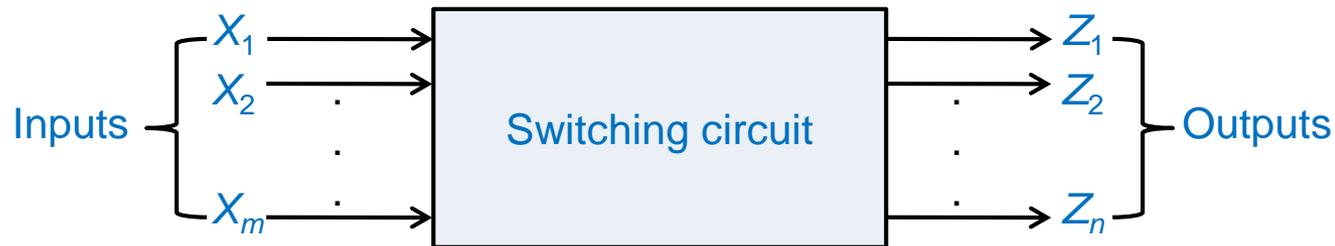- A switching circuit has one or more inputs and one or more outputs that take on discrete values (**two-value** in general)



- We usually use a Boolean variable, such as X , Y , Z , to represent an input or output of a switching circuit
 - Usually take on only two different values
 - 1/0 for High/Low or True/False or Yes/No
 - Just symbols, NO numeric values
 - A two-value Boolean variable is also called a switching variable

Boolean algebra differs from ordinary algebra in **values**, operations, laws

Boolean algebra differs from ordinary algebra in values, **operations**, laws

5

Basic Operations


NOT, AND, OR

Operation -- Logic NOT

Complement = Inverse = Negate = NOT (' ; $\bar{\quad}$; \sim ; \neg)

- $0' = 1, 1' = 0$

- Symbol


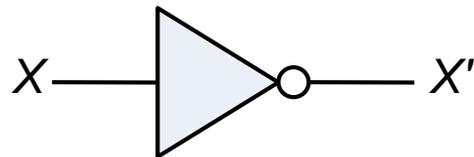


NOT gate
Inverter

- Truth table

Inputs		Outputs
X		X'
0		1
1		0

Input combinations Output values

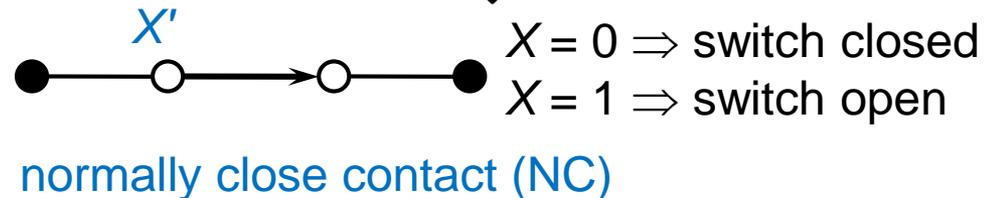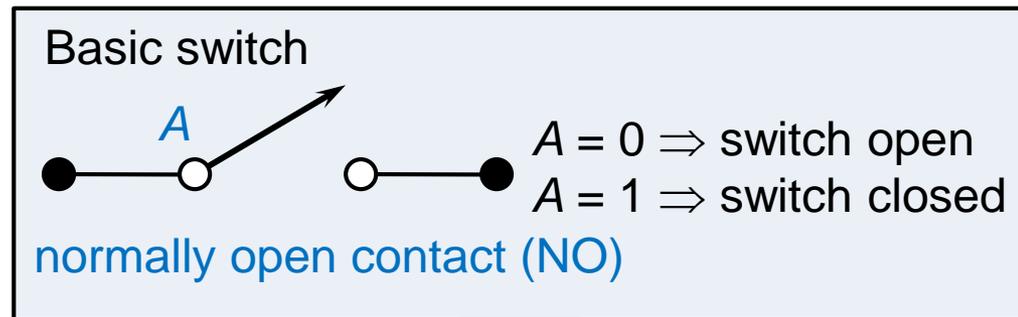


Operation -- Logic AND

AND (\bullet ; \wedge)

- $0 \bullet 0 = 0, 0 \bullet 1 = 0, 1 \bullet 0 = 0, 1 \bullet 1 = 1$

Symbol

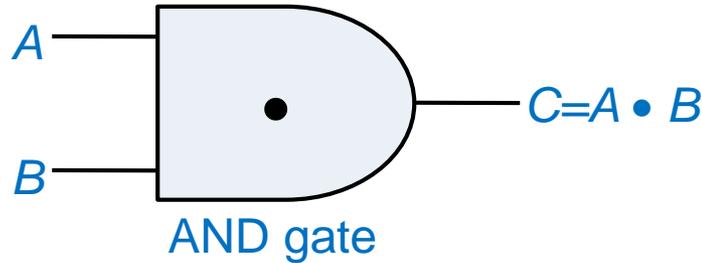


Truth table

A	B	C = A B
0	0	0
0	1	0
1	0	0
1	1	1

Omit " \bullet "

If one input is 0
 \Rightarrow output is 0

Switch (in series)

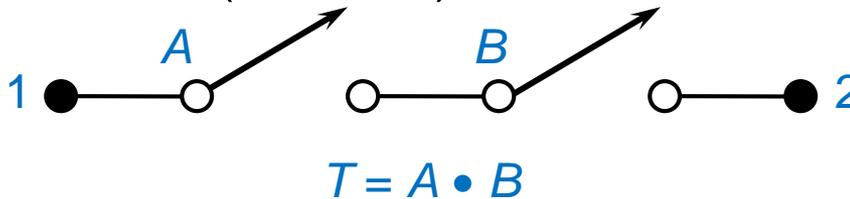

$T = 0 \Rightarrow 1 \rightarrow 2$ open
 $T = 1 \Rightarrow 1 \rightarrow 2$ closed


Switch A closed and switch B closed

Operation -- Logic OR

OR (+; \vee)

- 0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, 1 + 1 = 1

Symbol

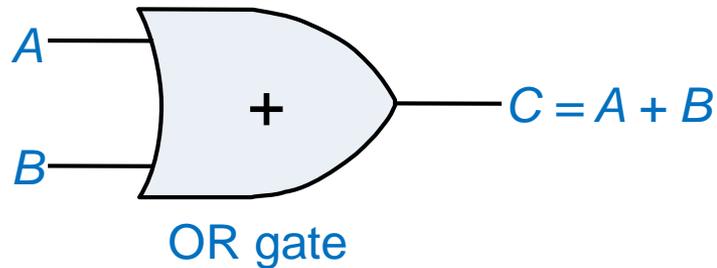


Truth table

A	B	C = A+B
0	0	0
0	1	1
1	0	1
1	1	1


If one input is 1
 \Rightarrow output is 1

Switch (in parallel)

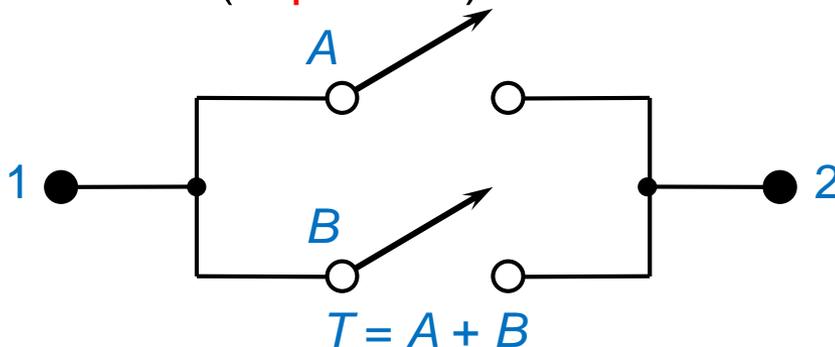

$T = 0 \Rightarrow 1 \rightarrow 2$ open
 $T = 1 \Rightarrow 1 \rightarrow 2$ closed


Switch A closed or switch B closed

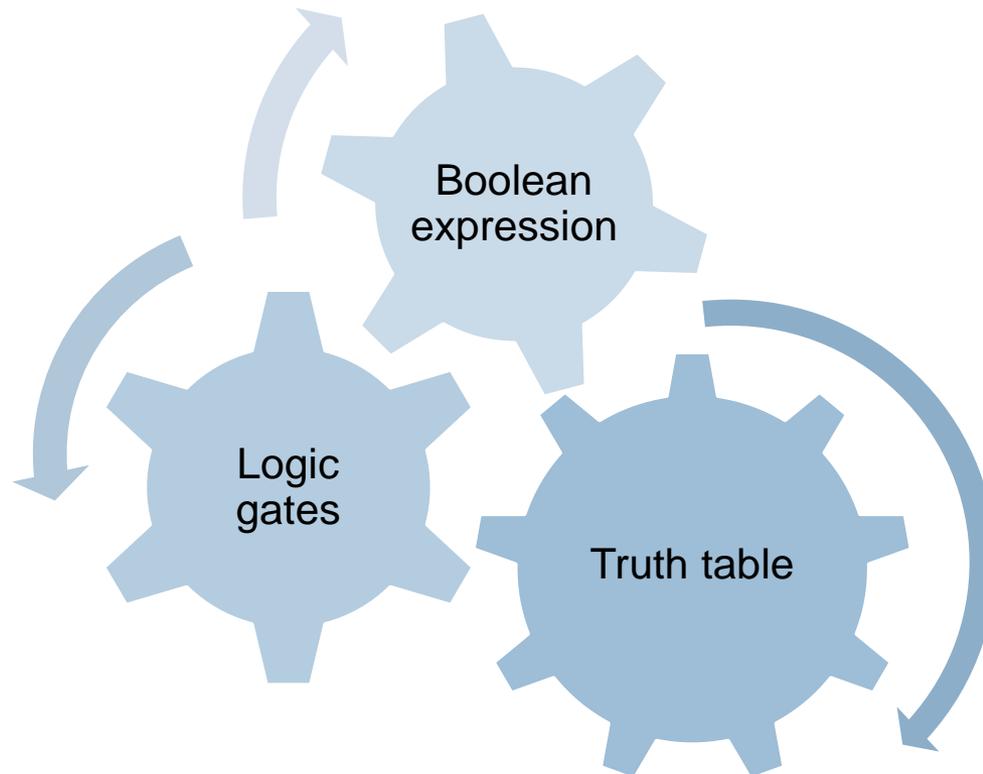


Boolean Expressions vs. Logic Gates

- A **Boolean expression** is formed by basic operations on variables or constants, e.g., the simplest one: 0, 1, X, Y
- Realize a Boolean expression by a circuit of logic gates
 - Perform operations in order: **Parentheses** → **NOT** → **AND** → **OR**

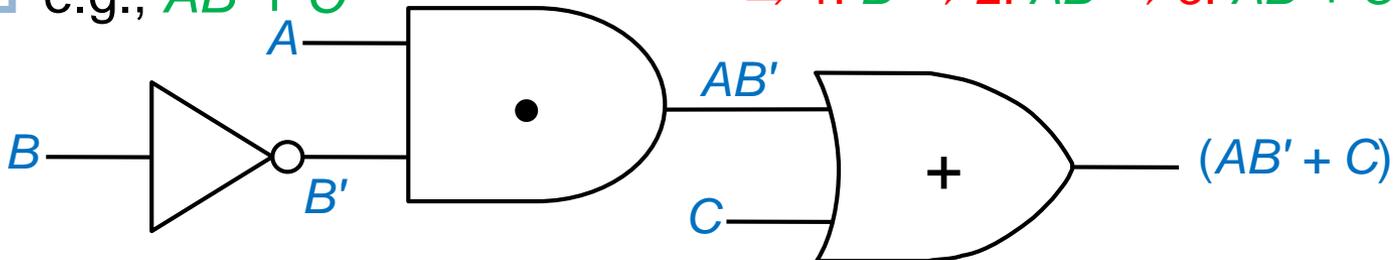□ e.g., $AB' + C$ \Rightarrow 1. B' \rightarrow 2. AB' \rightarrow 3. $AB' + C$



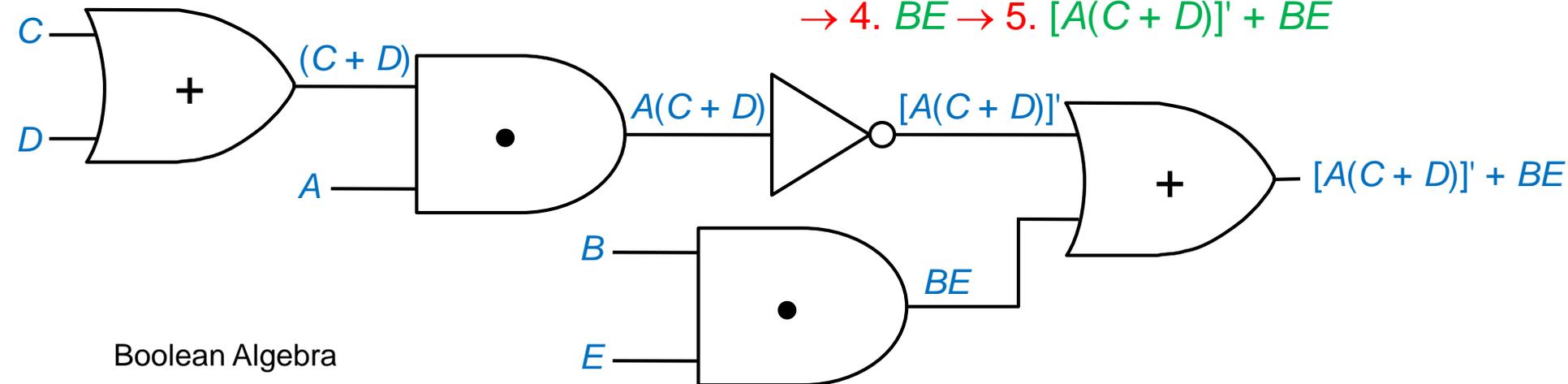□ e.g., $[A(C + D)]' + BE$ \Rightarrow 1. $C + D$ \rightarrow 2. $A(C + D)$ \rightarrow 3. $[A(C + D)]'$ \rightarrow 4. BE \rightarrow 5. $[A(C + D)]' + BE$




Boolean Expressions vs. Truth Tables

n variables
 $\Rightarrow 2^n$ rows

- A **truth table** specifies the output values of a Boolean expression for **all possible combinations of input values**
- \Rightarrow Check the **equivalence** between two expressions

□ e.g., $AB' + C = (A + C)(B' + C)$

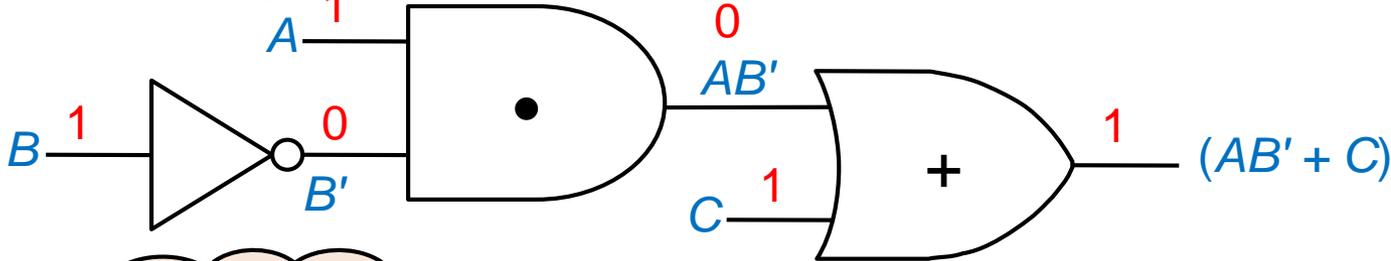


One function has different expressions

Expressions show the condition to make output == 1

A	B	C	B'	AB'	AB' + C	A+C	B' + C	(A+C)(B' + C)
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	1	1

Example: $F = A' + B$

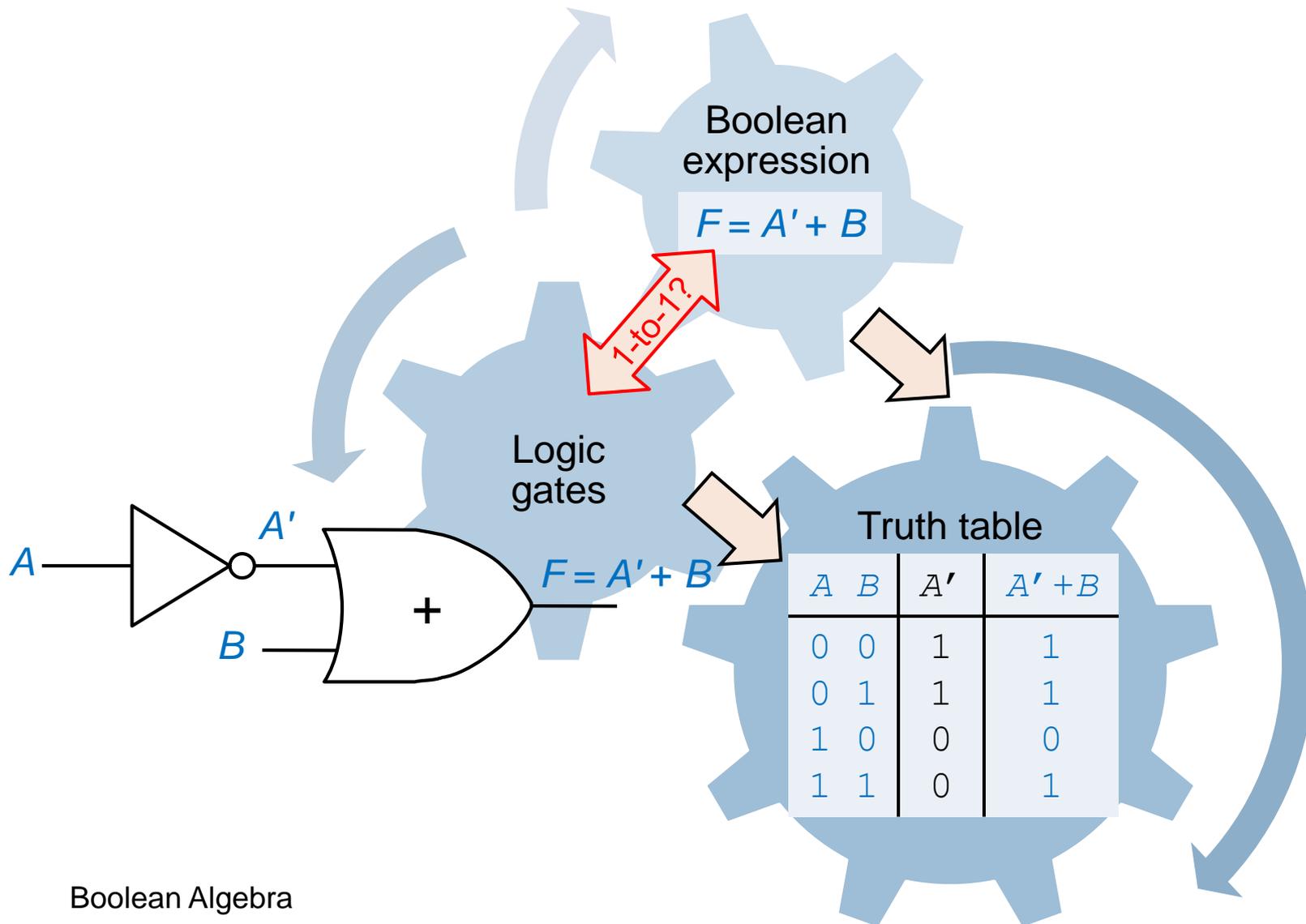

Boolean algebra differs from ordinary algebra in values, operations, **laws**

13

Theorems and Laws

Basic Theorems (1/3)

Operations with 0 and 1




- $X + 0 = X$

- $X \cdot 1 = X$

- $X + 1 = 1$

- $X \cdot 0 = 0$

- e.g., $(AB' + D)E + 1 = 1$

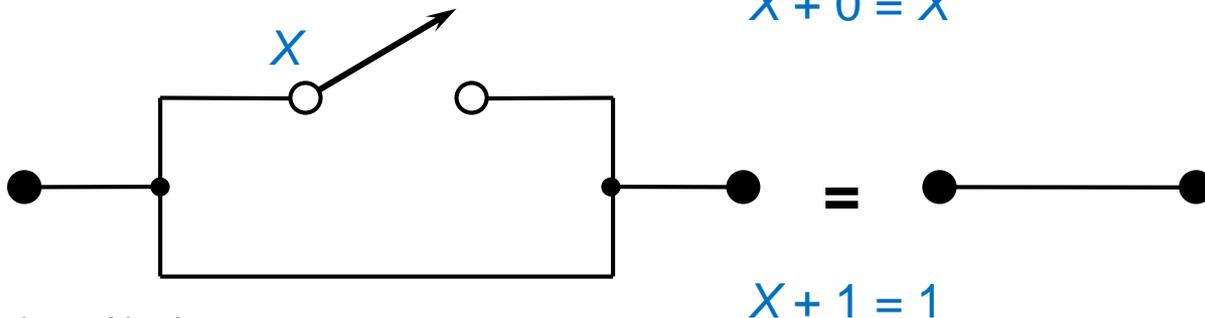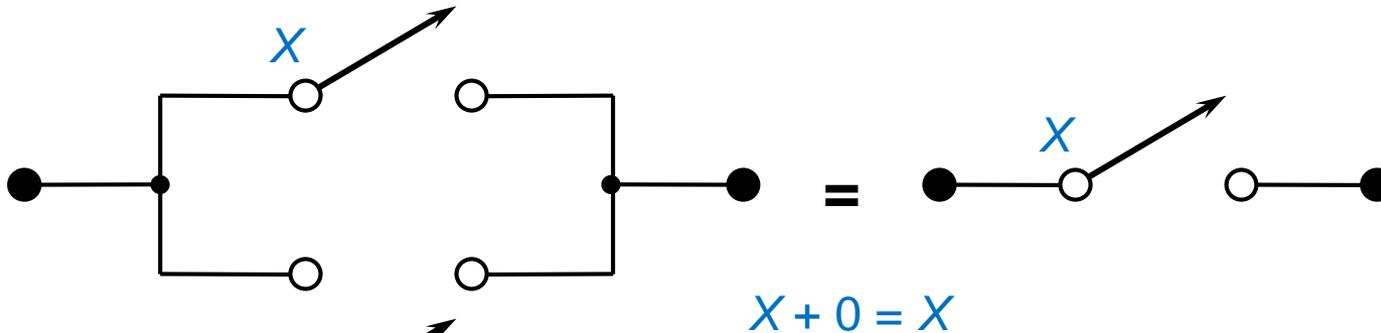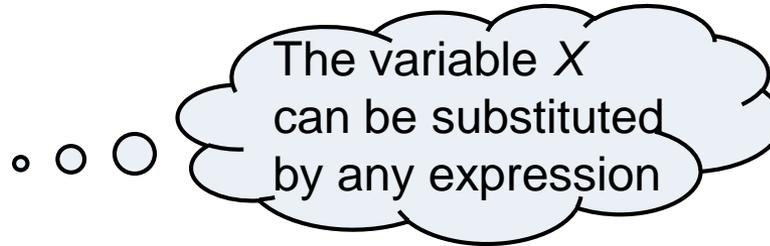

Basic Theorems (2/3)



15

© Iris H.-R. Jiang

□ Idempotent laws

□ $X + X = X$

□ $X \cdot X = X$

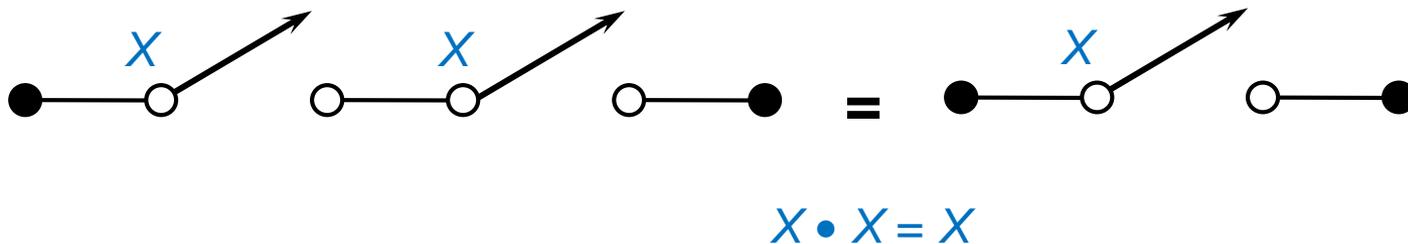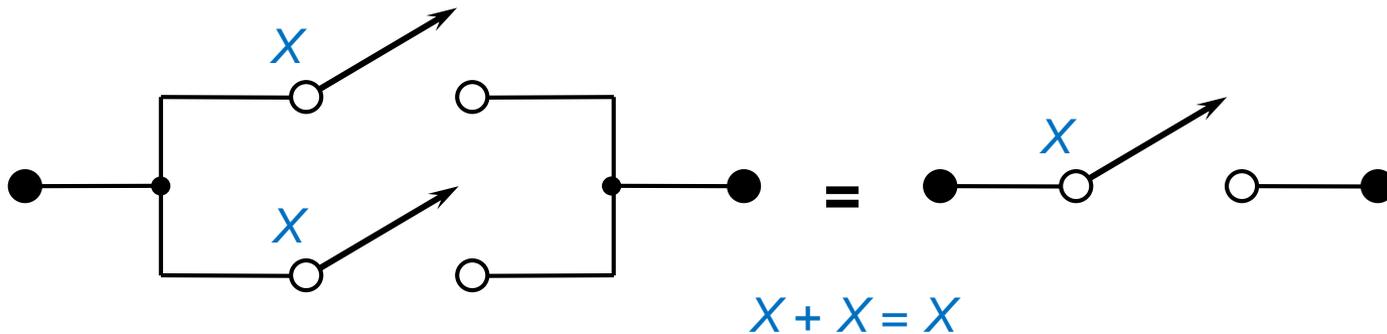

Basic Theorems (3/3)

□ Involution law



- $(X')' = X$

□ Laws of complementarity

- $X + X' = 1$


- $X \cdot X' = 0$

- e.g., $(AB' + D)(AB' + D)' = 0$

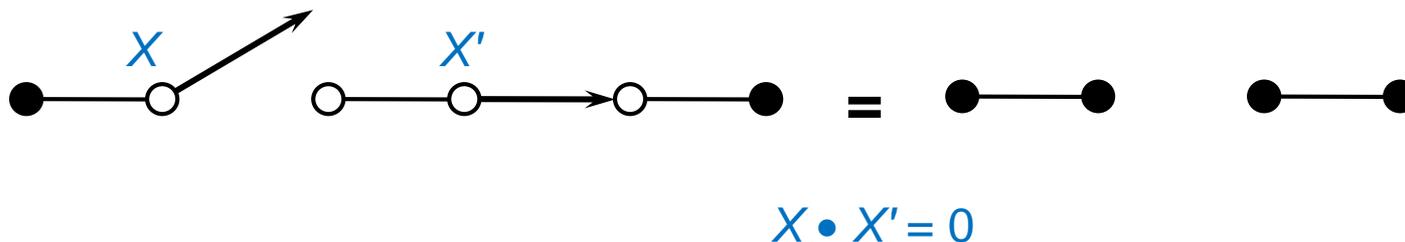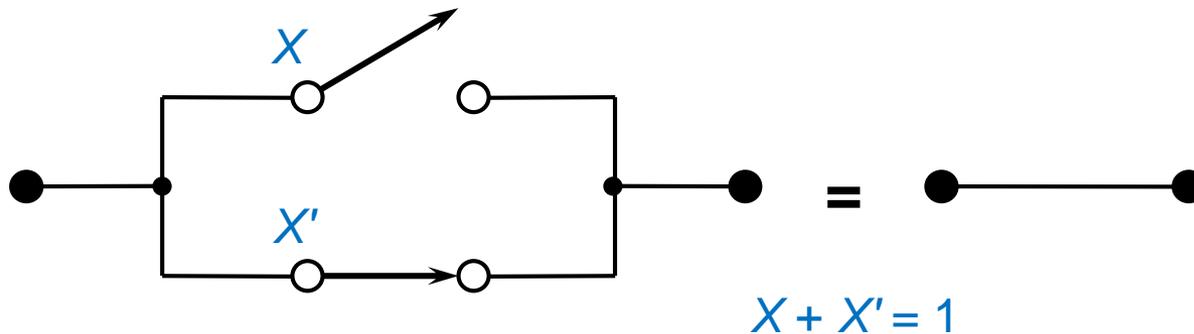

Commutative/Associative Laws

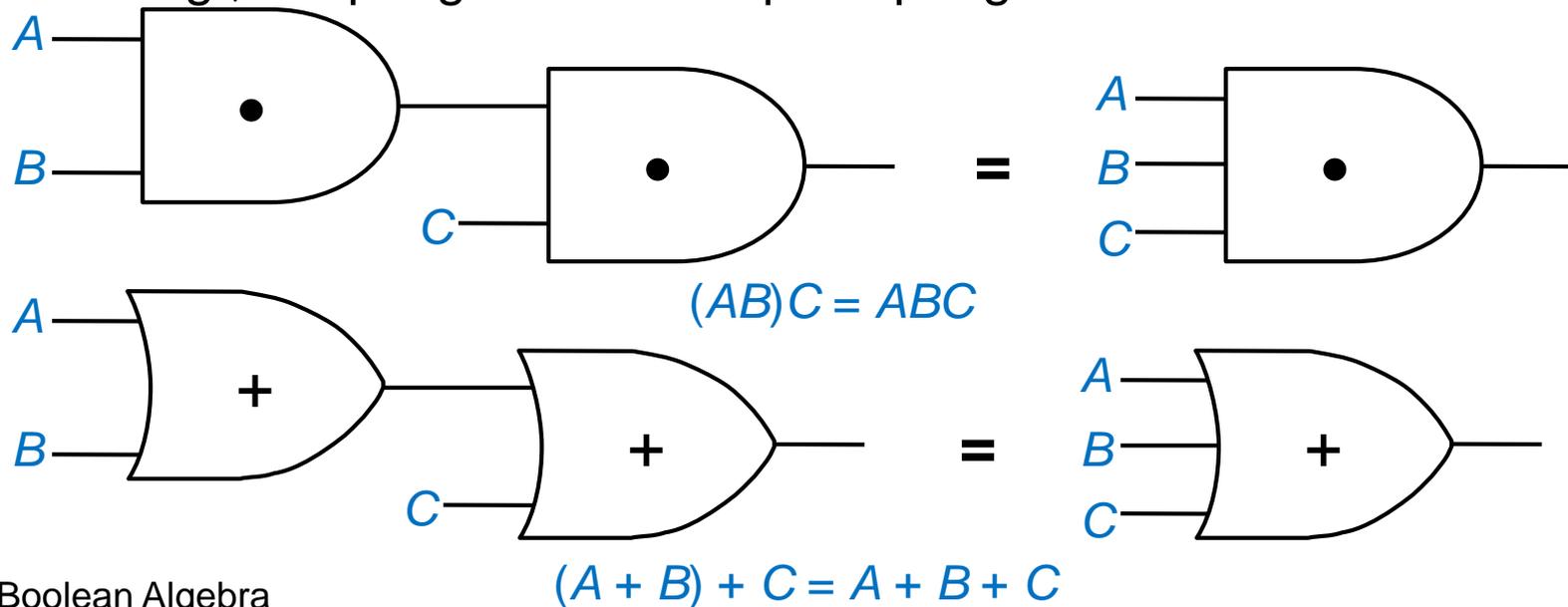- **Commutative laws for AND and OR**
 - $XY = YX$
 - $X + Y = Y + X$
- **Associative laws for AND and OR**
 - $(XY)Z = X(YZ) = XYZ$
 - $(X + Y) + Z = X + (Y + Z) = X + Y + Z$
 - e.g., 2-input gates \Rightarrow multiple-input gates



Distributive Laws (1/2)

- **Ordinary distributive law**

- $X(Y + Z) = XY + XZ$



- **Second distributive law (Important !)**

- $X + YZ = (X + Y)(X + Z)$



- Proof?

Only valid for Boolean algebra

Distributive Laws (2/2)

□ Prove a Boolean theorem/law by:

1. Truth table

$$X + YZ = (X + Y)(X + Z) \quad =?$$

X	Y	Z	YZ	X+YZ	X+Y	X+Z	(X+Y)(X+Z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

2. Basic theorems

$$\begin{aligned}
 & (X + Y)(X + Z) \\
 &= X(X + Z) + Y(X + Z) \\
 &= XX + XZ + YX + YZ \\
 &= X + XZ + XY + YZ \\
 &= X \cdot 1 + XZ + XY + YZ \\
 &= X(1 + Z + Y) + YZ \\
 &= X \cdot 1 + YZ \\
 &= X + YZ
 \end{aligned}$$


Simplification Theorems

□ **Useful simplification theorems**

□ $XY + XY' = X$

□ $X + XY = X$

□ $(X + Y')Y = XY$

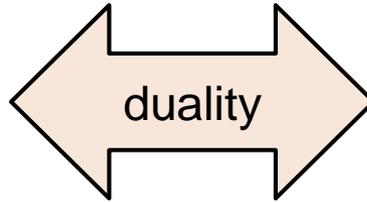

□ $(X + Y)(X + Y') = X$

□ $X(X + Y) = X$

□ $XY' + Y = X + Y$


□ **Proof:**

□ $X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$

□ $X(X + Y) = XX + XY = X + XY = X$

□ $XY' + Y = Y + XY' = (Y + X)(Y + Y') = (Y + X) \cdot 1 = Y + X$


■ Use switches

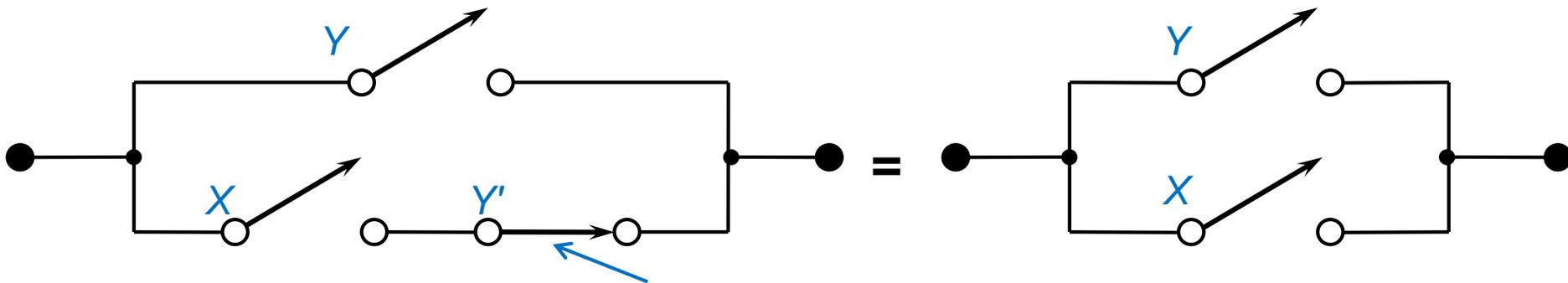

If switch Y open \Rightarrow switch Y' closed


Simplification Examples

1. $A(A'+B) = AB$

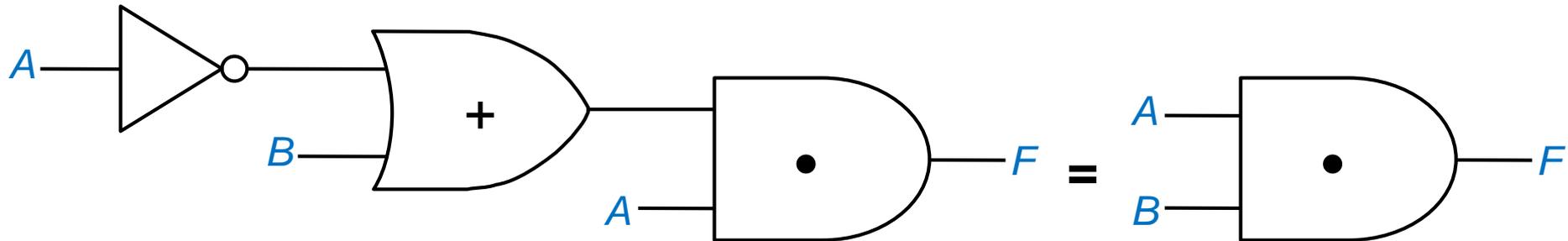

2. $Z = [A + B'C + D + EF][A + B'C + (D + EF)']$
 $= [A + B'C + D + EF][A + B'C + (D + EF)']$
 $= [X + Y][X + Y']$
 $= X = A + B'C$

3. $Z = (AB + C)(B'D + C'E) + (AB + C)'$
 $= (AB + C)(B'D + C'E) + (AB + C)'$
 $= X Y + X'$
 $= XY + X' + X'Y = (X+X')Y + X'$
 $= Y + X' = B'D + C'E + (AB + C)'$

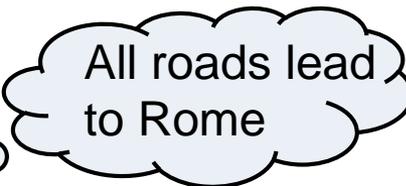
 $= XY + X' \cdot 1 = XY + X'(1 + Y)$

Multiplying Out

22

- Use the ordinary distributive law

$$X(Y + Z) = XY + XZ$$


to multiply out an expression to obtain a **sum-of-products** form

- e.g.,

$$AB' + CD'E + AC'E' \quad (V)$$

$$A + B' + C + D'E \quad (V)$$

$$(A + B)CD + EF \quad (X)$$

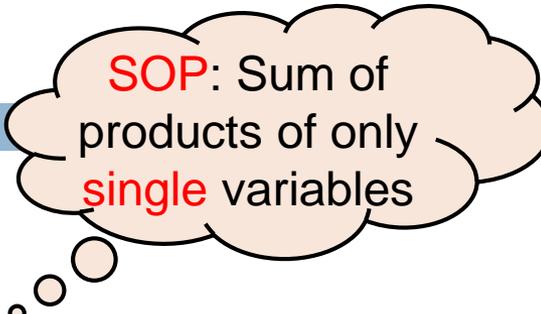

SOP: Sum of products of only **single** variables


Example: Multiplying Out $(A+BC)(A+D+E)$

1. **Multiply out completely and then eliminate redundant terms**

$$\begin{aligned}(A+BC)(A+D+E) &= A+AD+AE+ABC+BCD+BCE \\ &= A(1+D+E+BC)+BCD+BCE \\ &= A+BCD+BCE\end{aligned}$$

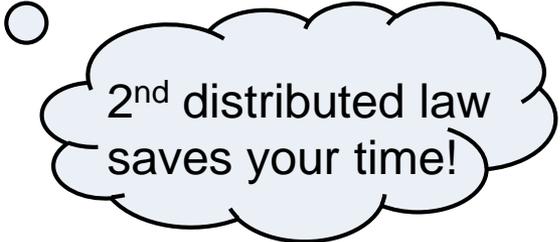2. **Or, apply 2nd distributive law first: $(X+Y)(X+Z)=X+YZ$**

$$\begin{aligned}(A+BC)(A+D+E) &= A+BC(D+E) \\ &= A+BCD+BCE\end{aligned}$$



2nd distributed law
saves your time!

Factoring

24

- Use the second distributive law

$$X + YZ = (X + Y)(X + Z)$$

to factor an expression to obtain a **product-of-sums** form


- e.g.,

$$(A + B')(C + D + E)(A + C' + E') \quad (V)$$

$$(A + B)(C + D + E)F \quad (V)$$

$$AB'C(D' + E) \quad (V)$$

$$(A + B)(C + D) + EF \quad (X)$$

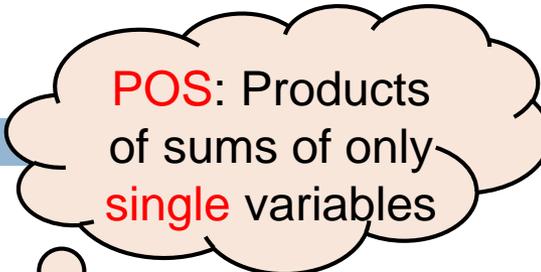

POS: Products of sums of only **single** variables

Example: Factoring

1. Factor $A + B'CD$

$$A + B'CD = (A + B')(A + CD) = (A + B')(A + C)(A + D)$$


2. Factor $AB' + C'D$

$$AB' + C'D = (AB' + C')(AB' + D) = (A + C')(B' + C')(A + D)(B' + D)$$


3. DIY: Factor $C'D + C'E' + G'H$

Iteratively apply
2nd distributed law


SOP vs. Logic Gates

Realize SOPs by **two-level** circuits (**AND-OR**)

▣ $AB' + CD'E + AC'E'$

AND


OR

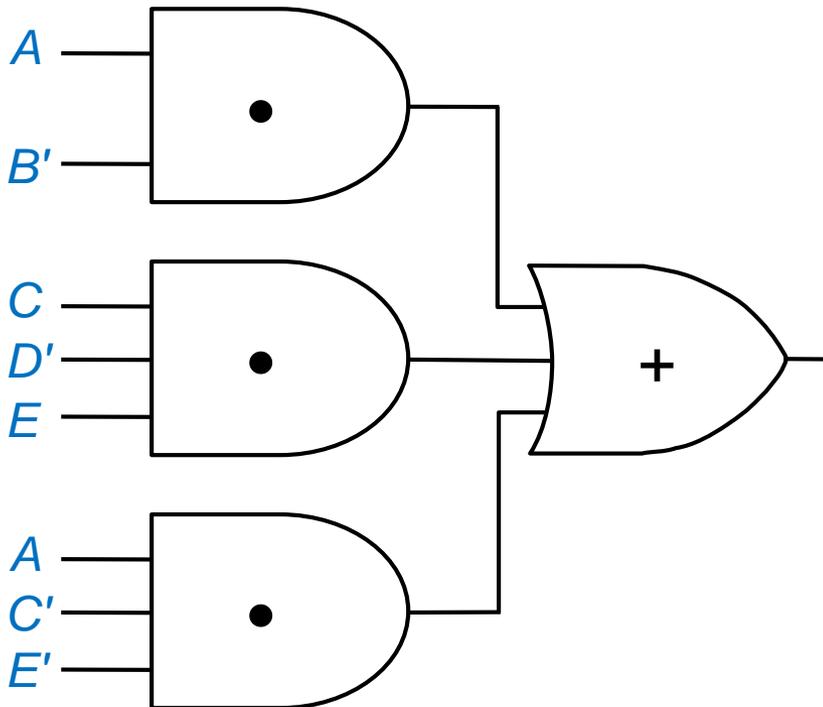

▣ $A + B' + C + D'E$

AND

OR

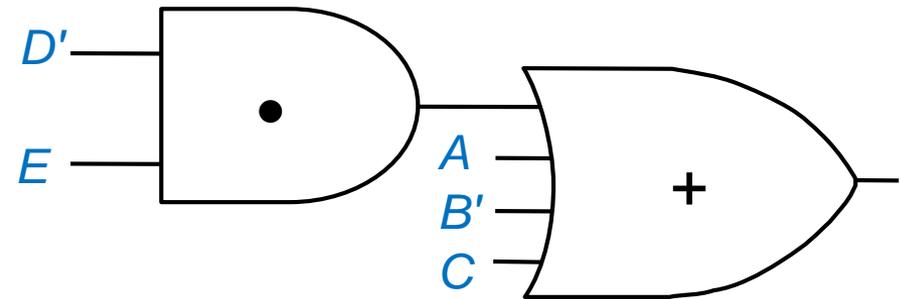


POS vs. Logic Gates

□ Realize POSs by **two-level** circuits (**OR-AND**)

□ $(A + B')(C + D + E)(A + C' + E')$

OR


AND

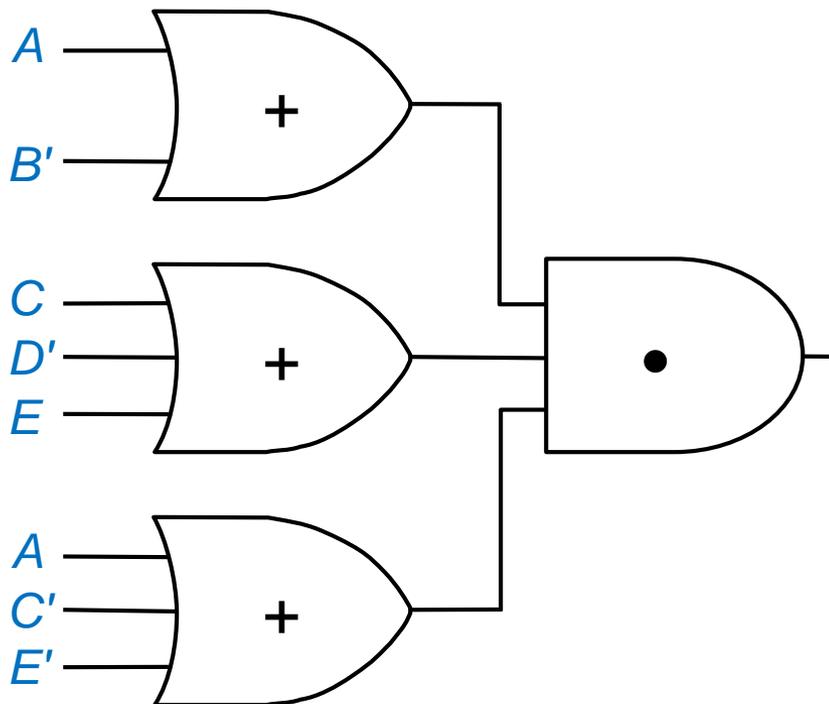

□ $AB'C(D' + E)$

OR

AND

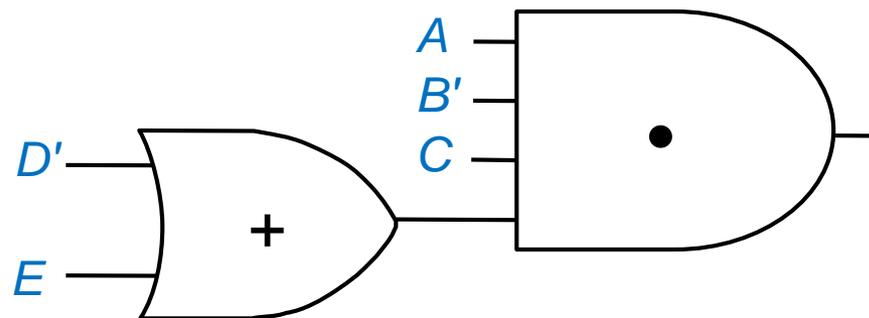

DeMorgan's Laws

□ Complement a Boolean expression by DeMorgan's laws

$$\square (X + Y)' = X'Y'$$

$$\square (XY)' = X' + Y'$$

□ Proof: By truth table

X	Y	X'	Y'	$X+Y$	$(X+Y)'$	$X'Y'$	XY	$(XY)'$	$X'+Y'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

□ Generalize to n variables:

$$\square (X_1 + X_2 + \dots + X_n)' = X_1'X_2' \dots X_n'$$

$$\square (X_1X_2 \dots X_n)' = X_1' + X_2' + \dots + X_n'$$

□ One-step rule:


$$\square [f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]' = f(x_1', x_2', \dots, x_n', 1, 0, \bullet, +)$$

$$\square x \leftrightarrow x'; + \leftrightarrow \bullet; 0 \leftrightarrow 1$$

Example: Complementing $(AB' + C)D' + E$

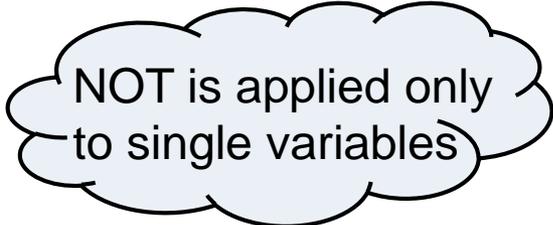1. Iteratively apply DeMorgan's laws:

$$\begin{aligned} [(AB' + C)D' + E]' &= [(AB' + C)D']'E' \\ &= [(AB' + C)' + D]E' \\ &= [(AB)'+C'+D]E' \\ &= [(A'+B)C'+D]E' \end{aligned}$$



NOT is applied only to single variables

2. Or, use one-step rule:

$$\begin{aligned} [(AB' + C)D' + E]' &= [(((A \bullet B') + C) \bullet D') + E]' \\ &= (((A'+B) \bullet C') + D) \bullet E' \end{aligned}$$

Duality

- **Dual:**
 - $[f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]^D = f(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)$
 - $+ \leftrightarrow \bullet; 0 \leftrightarrow 1$
- **Cf. DeMorgan's laws:**
 - $[f(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)]' = f(x_1', x_2', \dots, x_n', 1, 0, \bullet, +)$
 - $x \leftrightarrow x'; + \leftrightarrow \bullet; 0 \leftrightarrow 1$
- \Rightarrow **Find the dual of an expression:**
 - Complement the entire expression
 - Complement each individual variable
- e.g., $(XYZ\dots)^D = X + Y + Z + \dots$
- e.g., $(AB' + C)^D = ?$
 $(AB' + C)' = (A'+B)C' \Rightarrow (AB' + C)^D = (A+B)C$
- **Application: $F = G \Leftrightarrow F^D = G^D$**