

UNIT 9

MULTIPLEXERS, DECODERS & PROGRAMMABLE DEVICES



Fall 2021

Multiplexers, Decoders & PLDs

□ Contents

- Multiplexers
- Three-state buffers
- Decoders and encoders
- Read-only memories
- Programmable logic devices
- Complex programmable logic devices
- Field programmable gate arrays


□ Reading

- Unit 9

3

Multiplexers

MUX

 


Multiplexers (1/3)

4

© Iris H.-R. Jiang

□ A multiplexer (data selector, MUX)

 
- Uses the control inputs to select one of the data inputs and connects it to the output terminal
- One combination of control inputs corresponds to one data input
- Symbol



□ Truth table

A	B	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

□ Switch

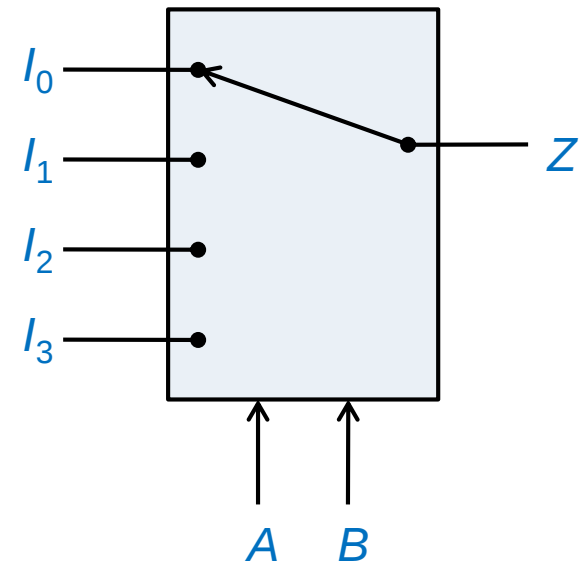

Multiplexers (2/3)


5

© Iris H.-R. Jiang

Logic equation of 4-to-1 MUX

$$\begin{aligned} Z &= A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3 \\ &= m_0I_0 + m_1I_1 + m_2I_2 + m_3I_3 \end{aligned}$$

A	B	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


Multiplexers (3/3)

6

© Iris H.-R. Jiang

□ The general equation for n control inputs

 □ $Z = m_0 I_0 + m_1 I_1 + \dots + m_i I_i + \dots + m_{2^n-1} I_{2^n-1} = \sum_{k=0..2^n-1} m_k I_k$




Application: Quad Multiplexer

7

© Iris H.-R. Jiang

- Select one of two 4-bit data words

 

Multiplexers, decoders & PLDs

Application: Realizing Combinational Logic

8


© Iris H.-R. Jiang

- e.g., realize a 3-variable function by a 4-to-1 MUX

$$F(A, B, C) = A'B' + AC$$


$$= A'B' + AC(B + B')$$
 
$$= 1 \bullet A'B' + 0 \bullet A'B + C \bullet AB' + C \bullet AB$$



A	B	F
0	0	1
0	1	0
1	0	C
1	1	C

Tri-state buffers

 



Buffers

10

© Iris H.-R. Jiang

- **Buffers:** increase the **driving capability** of a gate output

- Symbol

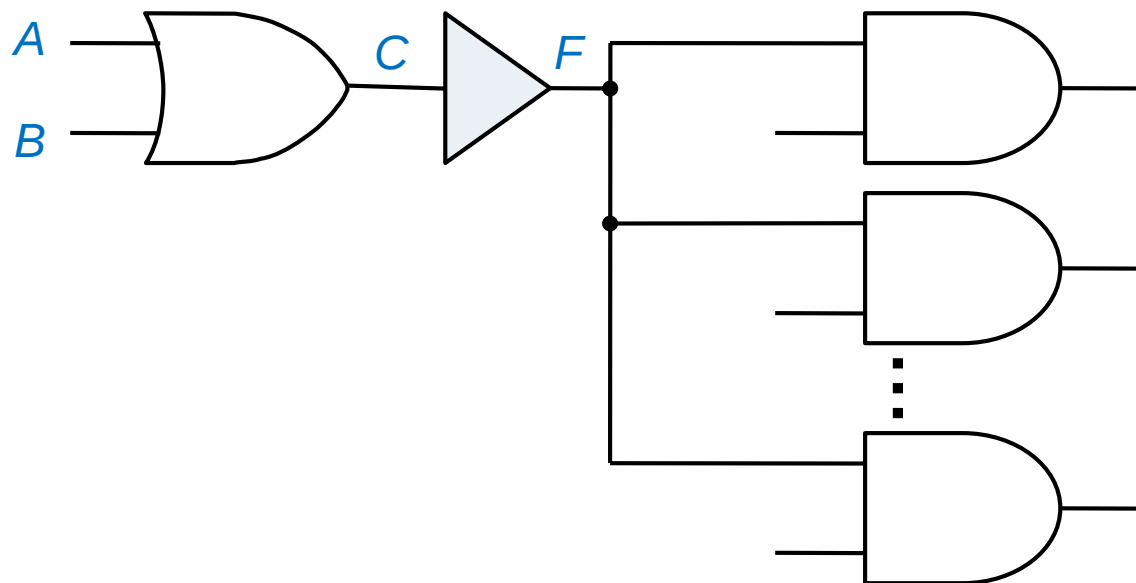 


Three-State Buffers

11


© Iris H.-R. Jiang

- Three-state (tri-state) buffers: permits gate outputs to be connected together

- Symbol

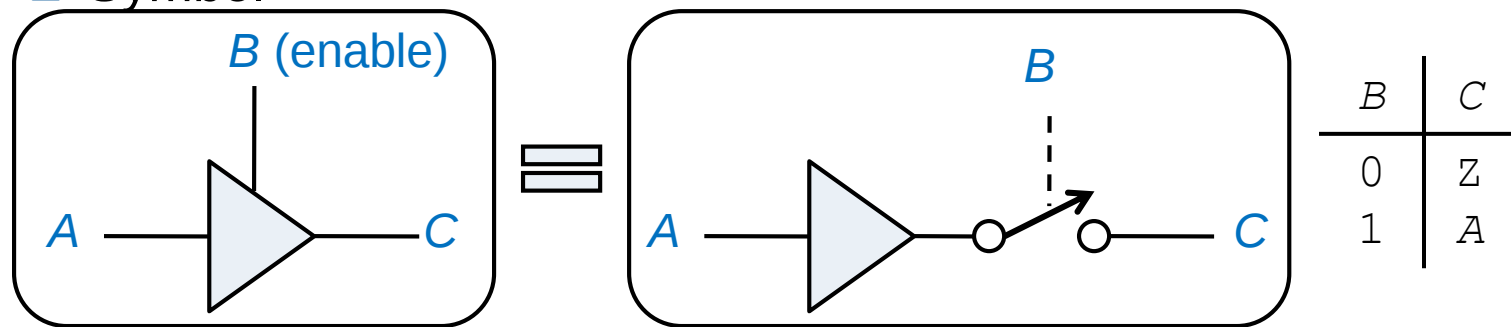

- 4 variants

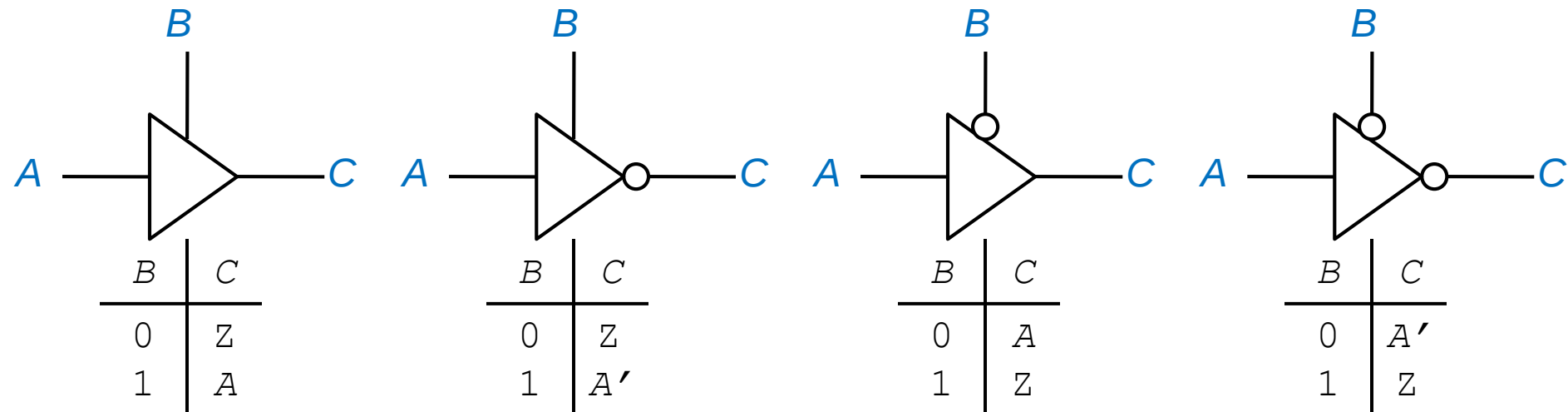


Application (1/2)


12

© Iris H.-R. Jiang

□ Data selection

 

□ Circuit with 2 tri-state buffers

 

outputs of buffers


		X	0	1	Z
X	X	X	X	X	X
0	X	0	X	0	
1	X	X	1	1	
Z	X	0	1	Z	

Application (2/2)


13

© Iris H.-R. Jiang

□ Tri-state bus

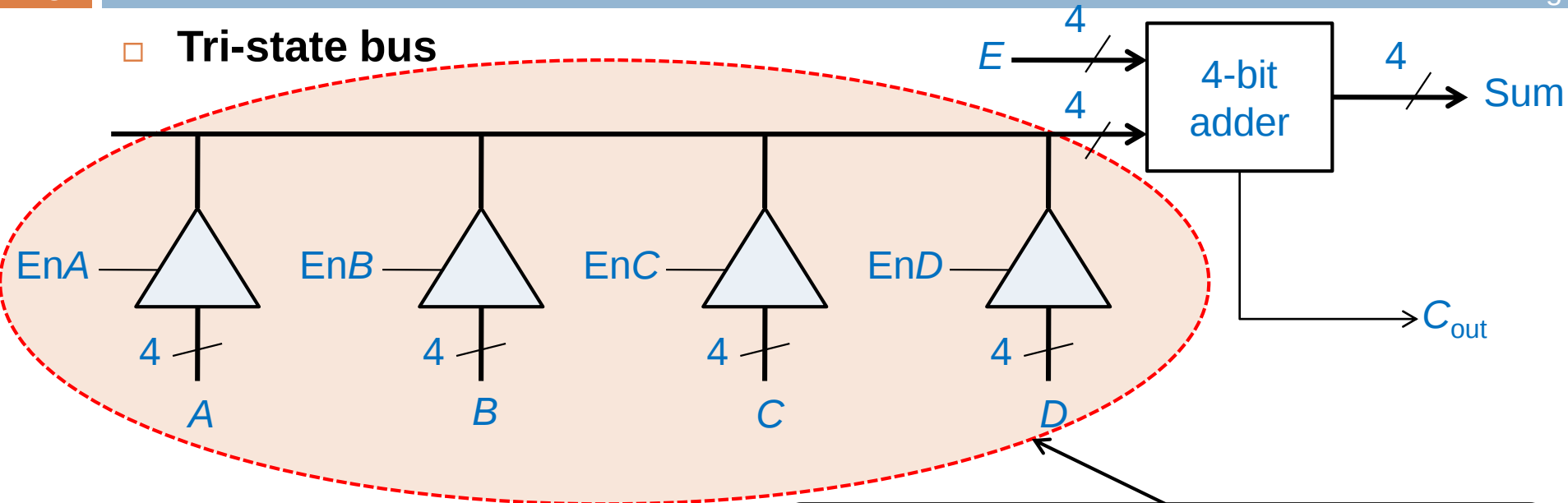

□ Bi-directional I/O pin

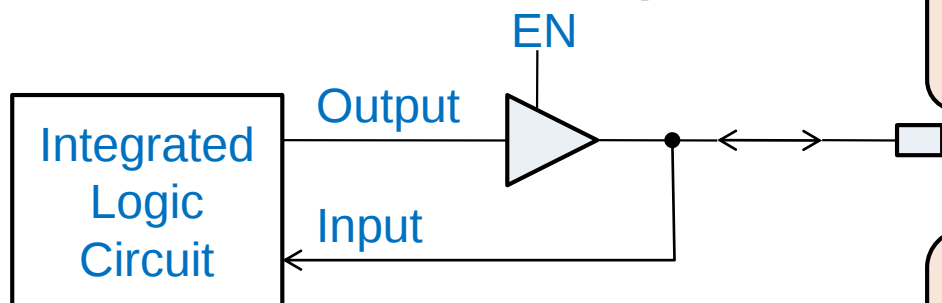

Key:
{EnA, EnB, EnC, EnD} must be **exclusive**
(Only 1 active at a time)

Bi-directional input-output pin:
The same pin can be used as an **input** pin and as an **output** pin, but not both at the same time

14

Decoders and Encoders

Decoders


15

© Iris H.-R. Jiang

□ **Decoder:** generates all of the minterms of input variables

▣ Exactly one output line corresponds to one input combination

▣ Symbol

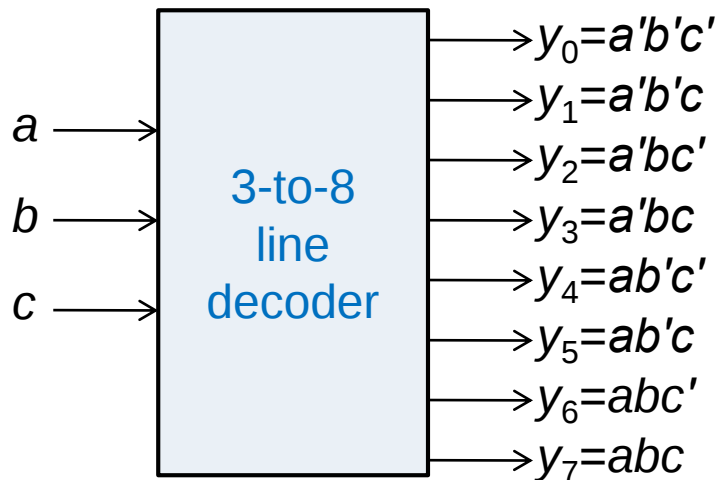

▣ Truth table

	a	b	c	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
m_0	0	0	0	1	0	0	0	0	0	0	0
m_1	0	0	1	0	1	0	0	0	0	0	0
m_2	0	1	0	0	0	1	0	0	0	0	0
m_3	0	1	1	0	0	0	1	0	0	0	0
m_4	1	0	0	0	0	0	0	1	0	0	0
m_5	1	0	1	0	0	0	0	0	1	0	0
m_6	1	1	0	0	0	0	0	0	0	1	0
m_7	1	1	1	0	0	0	0	0	0	0	1

▣ General n -to- 2^n decoder

■ Noninverted outputs: $y_i = m_i$, $i = 0$ to $2^n - 1$


■ Inverted outputs: $y_i = m_i' = M_i$, $i = 0$ to $2^n - 1$

Example: 4-to-10 Line Decoder

16

© Iris H.-R. Jiang


Block diagram

 

Truth table

BCD input	Decimal output									
<i>ABCD</i>	0	1	2	3	4	5	6	7	8	9
0000	0	1	1	1	1	1	1	1	1	1
0001	1	0	1	1	1	1	1	1	1	1
0010	1	1	0	1	1	1	1	1	1	1
0011	1	1	1	0	1	1	1	1	1	1
0100	1	1	1	1	0	1	1	1	1	1
0101	1	1	1	1	1	0	1	1	1	1
0110	1	1	1	1	1	1	0	1	1	1
0111	1	1	1	1	1	1	1	0	1	1
1000	1	1	1	1	1	1	1	1	0	1
1001	1	1	1	1	1	1	1	1	1	0
1010	1	1	1	1	1	1	1	1	1	1
1011	1	1	1	1	1	1	1	1	1	1
1100	1	1	1	1	1	1	1	1	1	1
1101	1	1	1	1	1	1	1	1	1	1
1110	1	1	1	1	1	1	1	1	1	1
1111	1	1	1	1	1	1	1	1	1	1

Logic diagram

 


Application: Realizing n -Variable Functions

17


© Iris H.-R. Jiang

 - **Exactly one output line corresponds to one minterm**
 - ▣ $\Rightarrow$ Realize n -variable functions by **OR**ing selected minterm outputs from a decoder
 - ▣ e.g., $f_1 = \Sigma m(1, 2, 4)$, $f_2 = \Sigma m(4, 7, 9)$



Encoders

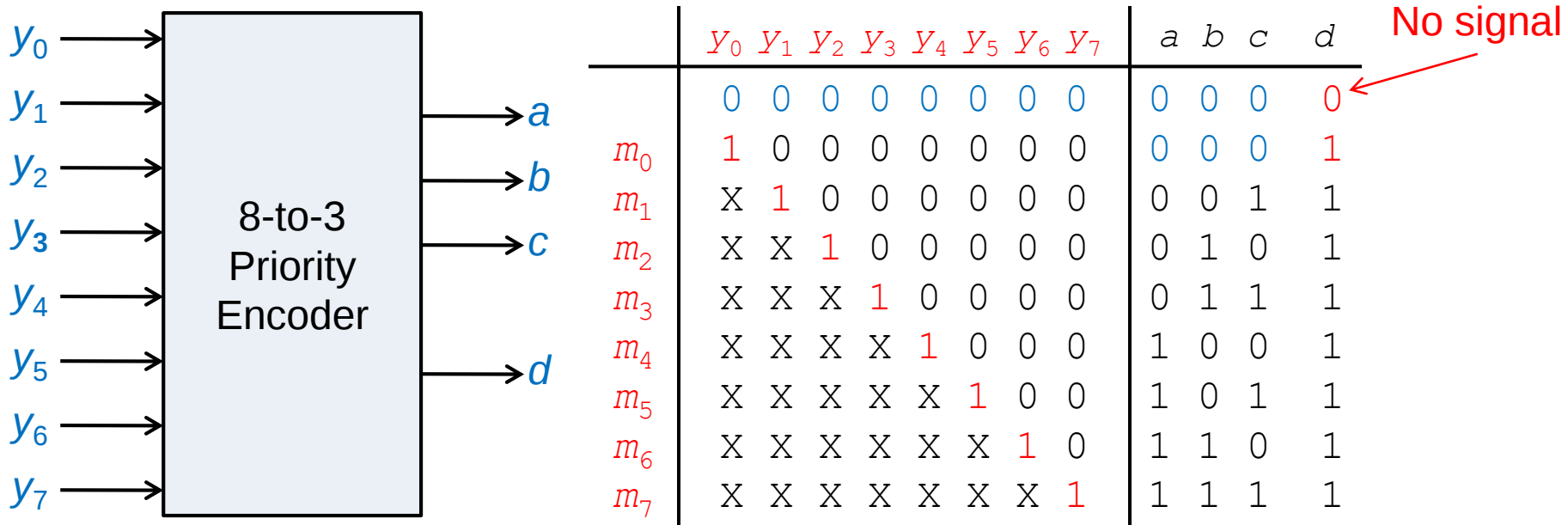- **Encoder:** performs the inverse function of a decoder
 - ▣ If $y_i = 1$, abc outputs represent a binary number equal to i
 - ▣ If **more than one** input can be 1 at a time, use a priority scheme



19

Read-Only Memories


ROM

Read-Only Memories (1/3)

20

© Iris H.-R. Jiang

 - A **read-only memory (ROM)**: stores an array of binary data
 - ▣ Stored data cannot be changed
 - ▣ e.g., 8-word $\times$ 4-bit ROM: each word is 4-bit, total 8 words
 - Input: ABC : 3-bit lines can index 2^3 values (0~7 address)
 - Output: $F_0F_1F_2F_3$: each output pattern is called a word




typical data stored in ROM
(2^3 words of 4 bits each)

ROM (2/3)

21

© Iris H.-R. Jiang

 
- Generalized form: 2^n Words $\times$ m Bits ROM (n -inputs m -outputs)



Size = $m \times 2^n$ bits m output lines

- Basic ROM structure

- A decoder + memory array

 

ROM (3/3)

22


© Iris H.-R. Jiang

The contents of a ROM are usually specified by a truth table


ABC	$F_0 F_1 F_2 F_3$
000	1 0 1 0
001	1 0 1 0
010	0 1 1 1
011	0 1 0 1
100	1 1 0 0
101	0 0 0 1
110	1 1 1 1
111	0 1 0 1

A
 B
 C

3-to-8
Decoder

 

Multiplexers, decoders & PLDs

 

Application: Multi-Output Combinational Ckts


23

© Iris H.-R. Jiang

□ e.g., hex to ASCII code converter

Hex	$A_6A_5A_4A_3A_2A_1A_0$
0	011 0000
1	011 0001
2	011 0010
3	011 0011
4	011 0100
5	011 0101
6	011 0110
7	011 0111
8	011 1000
9	011 1001
A	100 0001
B	100 0010
C	100 0011
D	100 0100
E	100 0101
F	100 0110

$A_5 = A_4$
 $A_6 = A'_4$

 

Multiplexers, decoders & PLDs

Three Common Types of ROMs

- **Mask-programmable ROMs**
 - ▣ Use mask to program
 - Include/omit switching elements
- **Programmable ROMs (PROMs)**
 - ▣ Program once
- **Electrically erasable programmable ROMs (EEPROMs)**
 - ▣ Can reprogram 100—1000 times

25

Programmable Logic Devices

PLD


PLA / PAL

Programmable Logic Arrays (1/3)

26

© Iris H.-R. Jiang

 - **Programmable logic arrays (PLAs): 2-level SOP implementation**
 - ▣ **AND plane** generates product terms
 - ▣ **OR plane** sums the product terms



PLA (2/3)




27

□ e.g.,

$$\begin{aligned} F_0 &= A'B' + AC' \\ F_1 &= AC' + B \\ F_2 &= A'B' + BC' \\ F_3 &= B + AC \end{aligned}$$



Product term	Inputs			Outputs			
	A	B	C	F_0	F_1	F_2	F_3
$A'B'$	0	0	–	1	0	1	0
AC'	1	–	0	1	1	0	0
B	–	1	–	0	1	0	1
BC'	–	1	0	0	0	1	0
AC	1	–	1	0	0	0	1

   

PLA (3/3)

28

© Iris H.-R. Jiang

□ e.g.,

□ $f_1(a, b, c, d) = \Sigma m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

□ $f_2(a, b, c, d) = \Sigma m(2, 3, 5, 6, 7, 10, 11, 14, 15)$

□ $f_3(a, b, c, d) = \Sigma m(6, 7, 8, 9, 13, 14, 15)$


□ Minimize using K-map

□ $f_1 = abd + a'bd + b'c + ab'c'$

□ $f_2 = c + a'bd$

□ $f_3 = bc + ab'c' + abd$

a	b	c	d	f_1	f_2	f_3
0	1	-	1	1	1	0
1	1	-	1	1	0	1
1	0	0	-	1	0	1
-	0	1	-	1	0	0
-	-	1	-	0	1	0
-	1	1	-	0	0	1

 


Programmable Array Logic (1/2)

29

© Iris H.-R. Jiang


 
- **Programmable array logic (PAL):** A special case of PLA
 - AND array: programmable
 - OR array: **fixed**
 - Symbol



PAL (2/2)

30


Fixed OR array

  

Application: Full Adder

31

H.-R. Jiang

 

X	Y	C_{in}	C_{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_{out} = XY + XC_{in} + YC_{in}$$


$$Sum = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$$

32 Complex Programmable Logic Devices

CPLD

33

 - ▣ Tools will program for you
- ▣ e.g., Xilinx XCR3064XL



CPLD (2/2)


34

© Iris H.-R. Jiang

□ CPLD function block and macrocell

- ▣ A simplified version of XCR3064XL

36 Inputs from IA

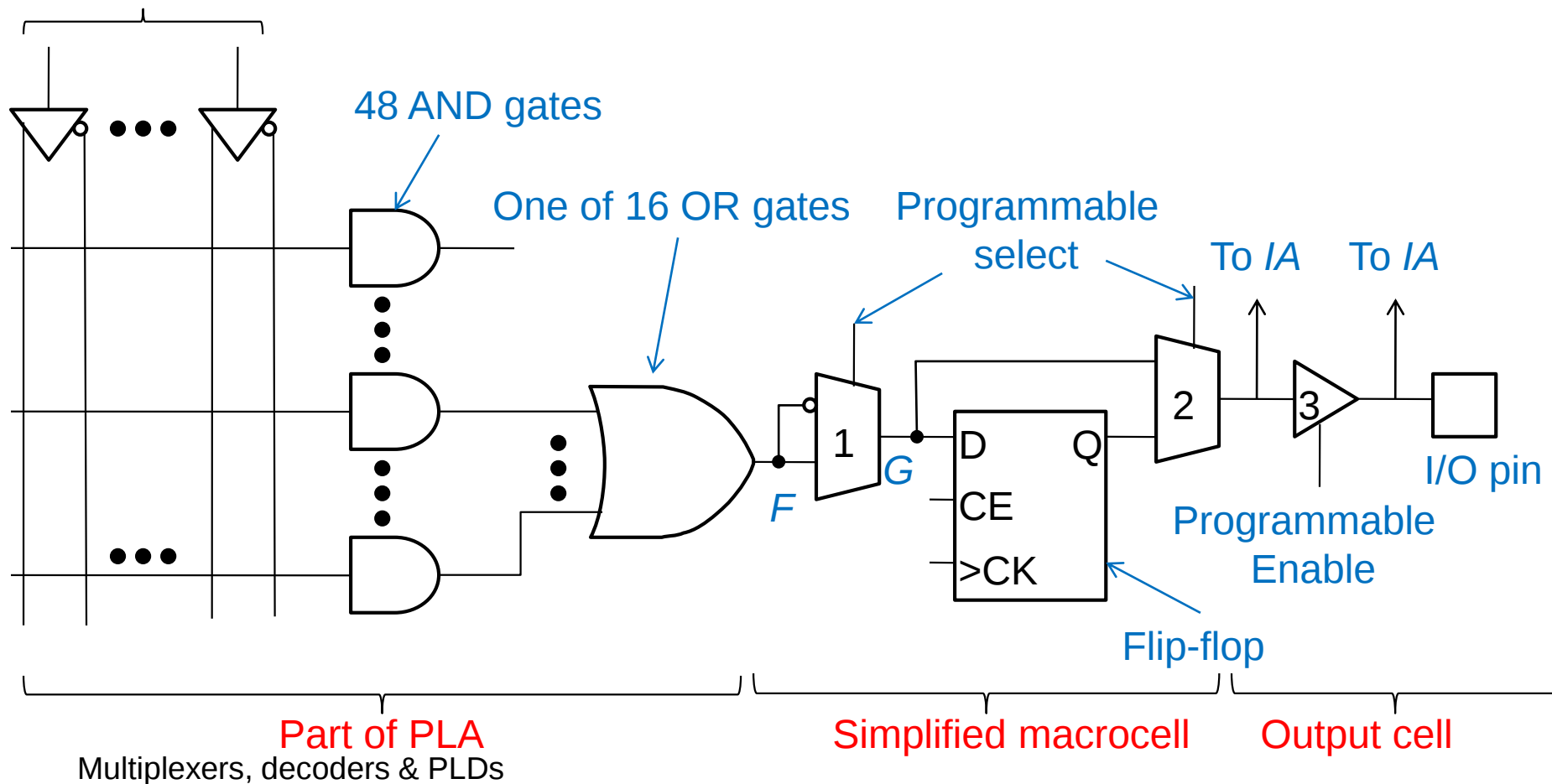

35

Field Programmable Gate Arrays


FPGA

Field Programmable Gate Arrays

36

© Iris H.-R. Jiang

 
- Field programmable gate arrays (**FPGA**): an array of identical logic cells + programmable interconnections



Simplified Configurable Logic Block (CLB)

37


© Iris H.-R. Jiang

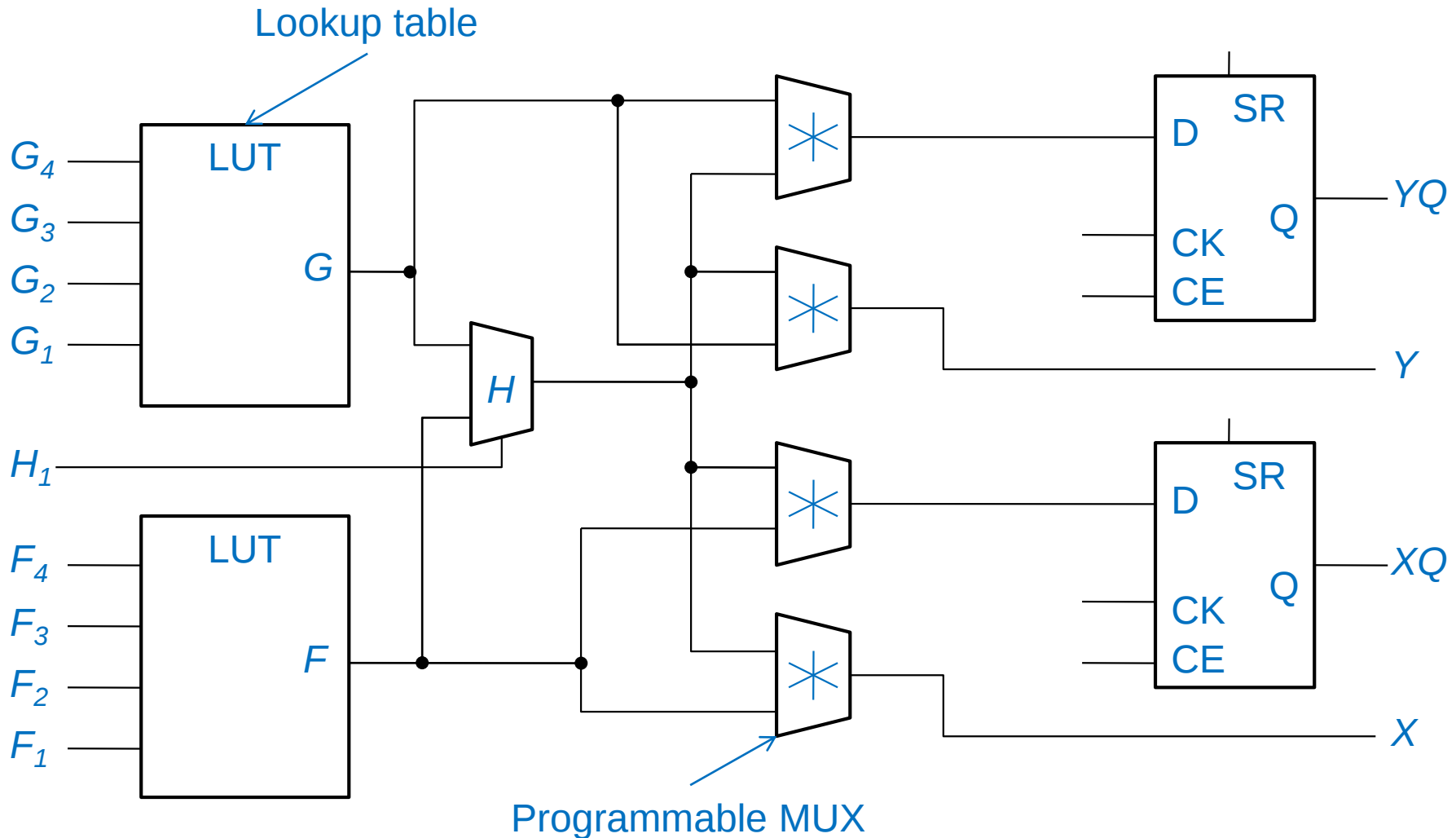

Implementation of a Lookup Table (LUT)

38

© Iris H.-R. Jiang

 

Realization with Function Generators

39


© Iris H.-R. Jiang

Realize a 5-variable function with 4-variable FGs:


■ $F(a, b, c, d, e) = a'F(0, b, c, d, e) + aF(1, b, c, d, e) = a'F_0 + aF_1$

■ 2 4-variable FGs + 2-to-1 MUX (controlled by a)

Q: 6-variable function?

 

Multiplexers, decoders & PLDs

 


Decomposition of Switching Functions

40



© Iris H.-R. Jiang

□ **Shannon's expansion theorem:** reduces input variables
 
$$\begin{aligned} \square \quad & f(x_1, x_2, \dots, x_{i-1}, x_i, x_{i+1}, \dots, x_n) = x'_i f_0 + x_i f_1 \\ & = x'_i f(x_1, x_2, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n) + x_i f(x_1, x_2, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n) \end{aligned}$$



F

 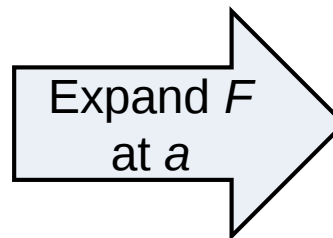

F_0

F_1