
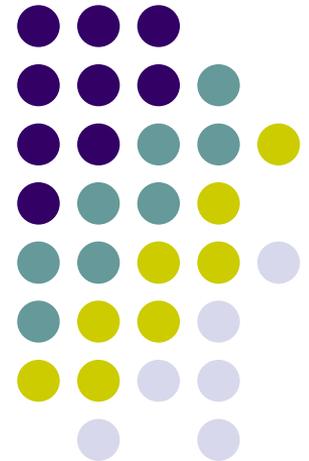


Chapter 4 Fault Simulation

錯誤模擬

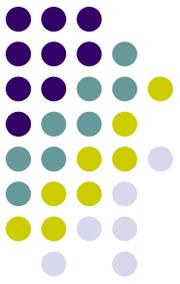


Outline



- Introduction to Fault Simulation
- Fault Simulation for Combinational Circuits
- Techniques for Sequential Circuits
- Fault Grading

What is Fault Simulation?

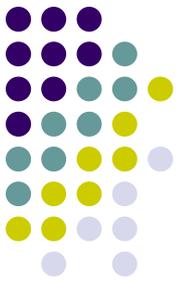


Given :

- **A circuit**
- **A test (sequence of test vectors)**
- **A fault model**

Determine:



- **Fault coverage (the fraction of modeled faults detected)**
- **Undetected faults**

Applications of Fault Simulation

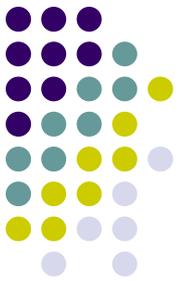

- Determine fault coverage of a given test sequence
 - Measure test quality by fault coverage
- Determine undetected faults for test generation
- Construct fault dictionary for diagnosis
 - Use a fault simulator to compute & store the response for every fault
 - If the output response of the circuit under test matches any of the response in the fault dictionary, the fault location is identified

Conceptual Fault Simulation

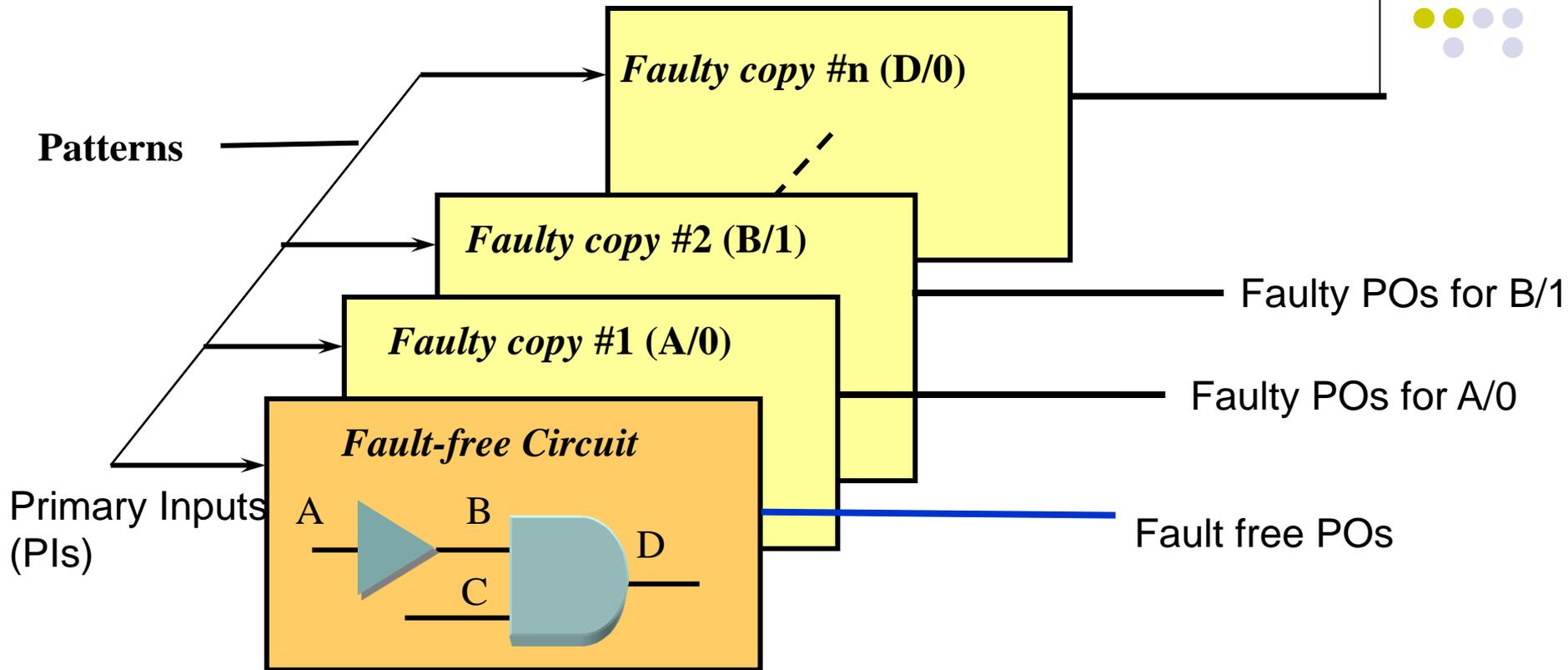 

- One logic simulation for every fault-free and faulty circuits
- Complexity $\sim O(F \times P \times G)$
 - F : # of faults; P : # of patterns; G : # of gates
- A simple technique: fault dropping.

Fault Simulation Techniques




- Parallel-Fault (Single-Pattern) Simulation
- Deductive Fault Simulation
- Concurrent Fault Simulation
- Parallel-Pattern Single-Fault Simulation
- Critical Path Tracing

Parallel Fault Simulation




- Simulate multiple circuits at a time
 - The inherent parallel operation of computer words to simulate faulty circuits in parallel with fault-free circuit
 - The number of faulty circuits (one for each fault) to be simultaneously processed is limited by the word length, e.g., 32 circuits for a 32-bit computer
- The fault-free logic simulation is repeated for each pass
 - This can be avoided by storing fault-free values in another word.

Speedup of Parallel Fault Simulation

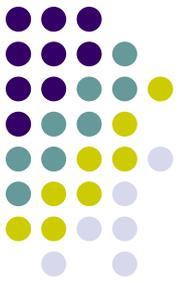

- There are extra costs associated with parallel fault simulation, so the speed up is only sub-linear.
 - An event, a value-change of a single fault or fault-free circuit leads to the computation of the entire word
 - A proper **fault grouping** is needed.
 - Group *similar* faults in the same simulation


Example: Parallel Fault Simulation

 


- Assume 4-bit computer words
- Consider three faults: J s-a-0, B s-a-1, and F s-a-0
- Bit allocation:

A/0	B/1	F/0	FF
------------	------------	------------	-----------


 ← Fault free bit

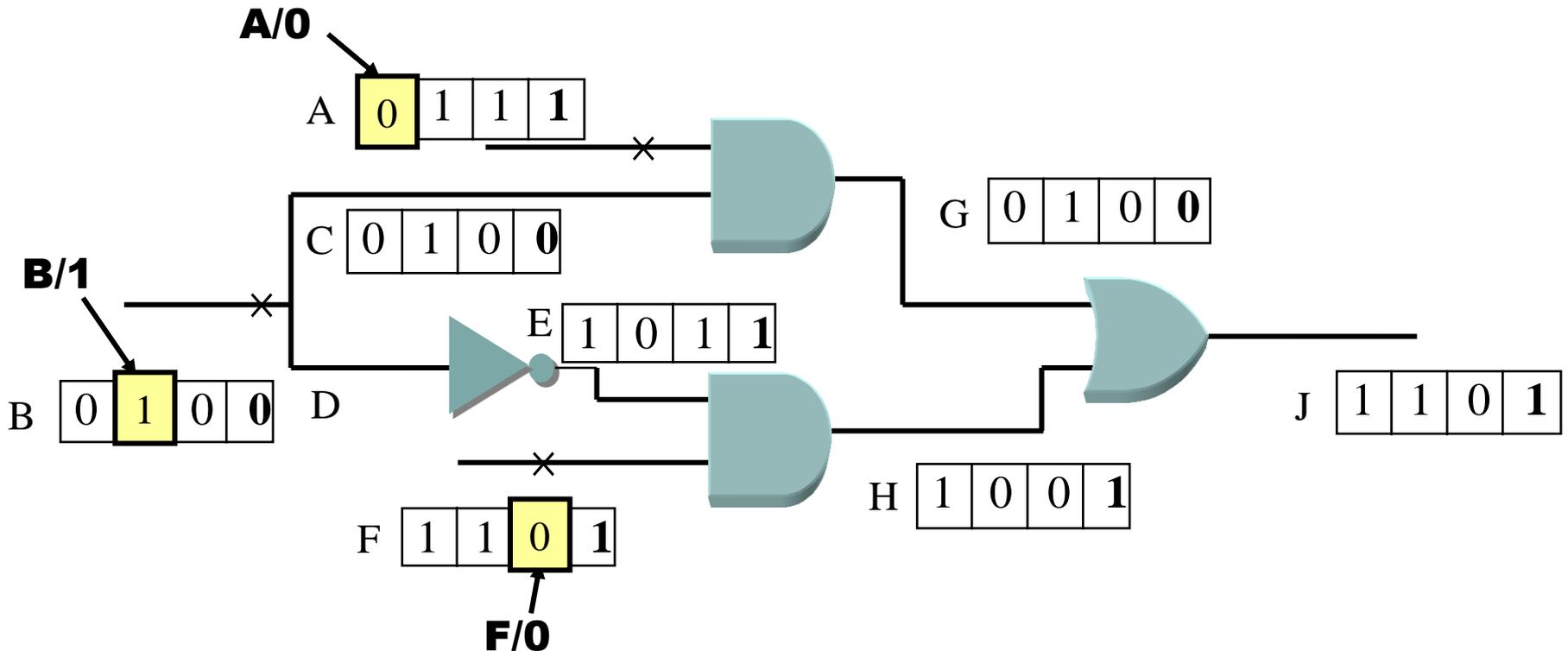


Fault Injection by Circuit Modeling

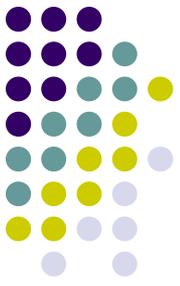

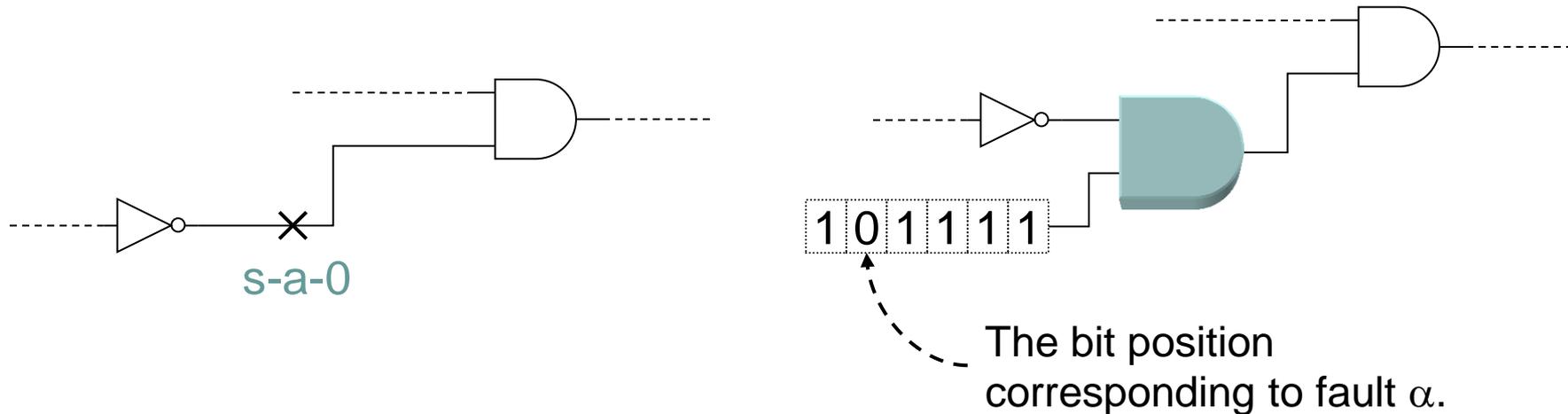- By changing only the circuits, we can use a parallel logic simulator to implement a parallel fault simulation.




Parallel Fault Simulation – Summary

 


- Most effective for
 - Interconnected logic gate netlist
 - Stuck-at faults
 - Two-valued logic
- Little resource required
 - Easy to implement
 - Fixed and low memory requirement
- Some extra cost
 - Faults injected in the same word may not generate the same events.
 - The fault-free circuit is simulated in each pass.


Fault List in Deductive Fault Simulation

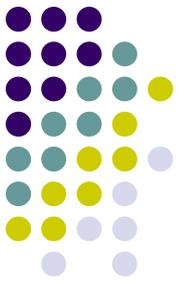

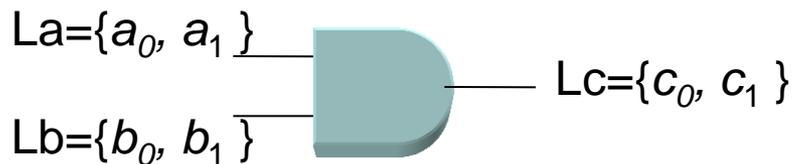- Maintain a fault list of every signals in a logic set.
- A fault is in a fault list of each signal if
 - The fault changes the fault-free value of the signal, or
 - The fault is propagated to the signal




Fault list before simulation

 



Fault list after logic simulation

Propagation of Fault List

 

- Create an initial fault list at every signal (inject collapsed faults)
- Propagate fault list starting from PIs.
- Propagate through gates level by level (logic deduction)
 - Propagation rules are set operations and depends only on gate type and its input values.
- A fault is detected if it appears in the fault list of a primary output.

An Example of Fault List Propagation

  


- Input $a = 0, b = 1$
- $a = 0 \rightarrow L_a = \{a_1\}$
 - a_1 : a stuck-at-1
- b_0 in L_b is not propagated to L_c because $a = 0$ is the controlling value.

Rule of Fault List Propagation



	<i>a</i>	<i>b</i>	<i>z</i>	Output fault list
AND	0	0	0	$\{L_a \cap L_b\} \cup z_1$
	0	1	0	$\{L_a - L_b\} \cup z_1$
	1	0	0	$\{L_b - L_a\} \cup z_1$
	1	1	1	$\{L_a \cup L_b\} \cup z_0$
OR	0	0	0	$\{L_a \cup L_b\} \cup z_1$
	0	1	1	$\{L_b - L_a\} \cup z_0$
	1	0	1	$\{L_a - L_b\} \cup z_0$
	1	1	0	$\{L_a \cap L_b\} \cup z_0$
NOT	0		1	$L_a \cup z_0$
	1		0	$L_a \cup z_1$

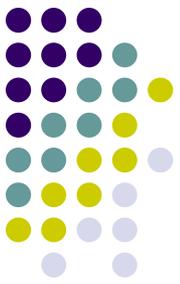

Fault List Propagation Rule

- Notations:
 - Let I be the set of inputs of a gate Z with a controlling value c and inversion i (i.e., i is 0 for AND, OR and 1 for NAND, NOR)
 - Let C be the set of inputs with value c

Non-controlling case:

$$\text{if } C = \phi \text{ then } L_z = \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s-a} - (c \oplus i)\}$$


union (with arrow pointing to the union symbol)

Controlling cases:

$$\text{else } L_z = \left\{ \bigcap_{j \in C} L_j \right\} - \left\{ \bigcup_{j \in I-C} L_j \right\} \cup \{Z \text{ s-a} - (\bar{c} \oplus i)\}$$


intersection (with arrow pointing to the intersection symbol)

A Generalized Propagation Rule – Cont'd

 

- If no input has value c , any fault effect on any input propagates to the output.
- If some inputs have value c , only a fault effect that affects all the inputs at c without affecting any of the inputs at c' propagates to the output.

An Example of Deductive Fault Simulation

 

$$L_a = \{a_0\}$$

$$L_b = \{b_0\}$$

$$L_c = \{b_0, c_0\}$$


$$L_d = \{b_0, d_0\}$$

$$L_e = L_a \cup L_c \cup \{e_0\} = \{a_0, b_0, c_0, e_0\}$$

$$L_f = \{b_0, d_0, f_1\}$$


$$L_g = \{L_e - L_f\} \cup \{g_0\} = \{a_0, c_0, e_0, g_0\}$$

The Deductive Fault Simulation Algorithm

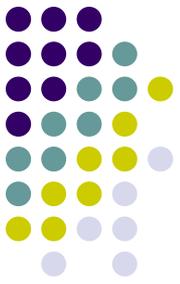


- **Levelize the circuit from PIs to POs.**
- **Step 1: Read a test vector.**
- **Step 2: Perform logic simulation.**
- **Step 3: Perform fault list propagation.**
- **Step 4: Determine detected faults.**
- **Goto step 1**

Fault Collapsing

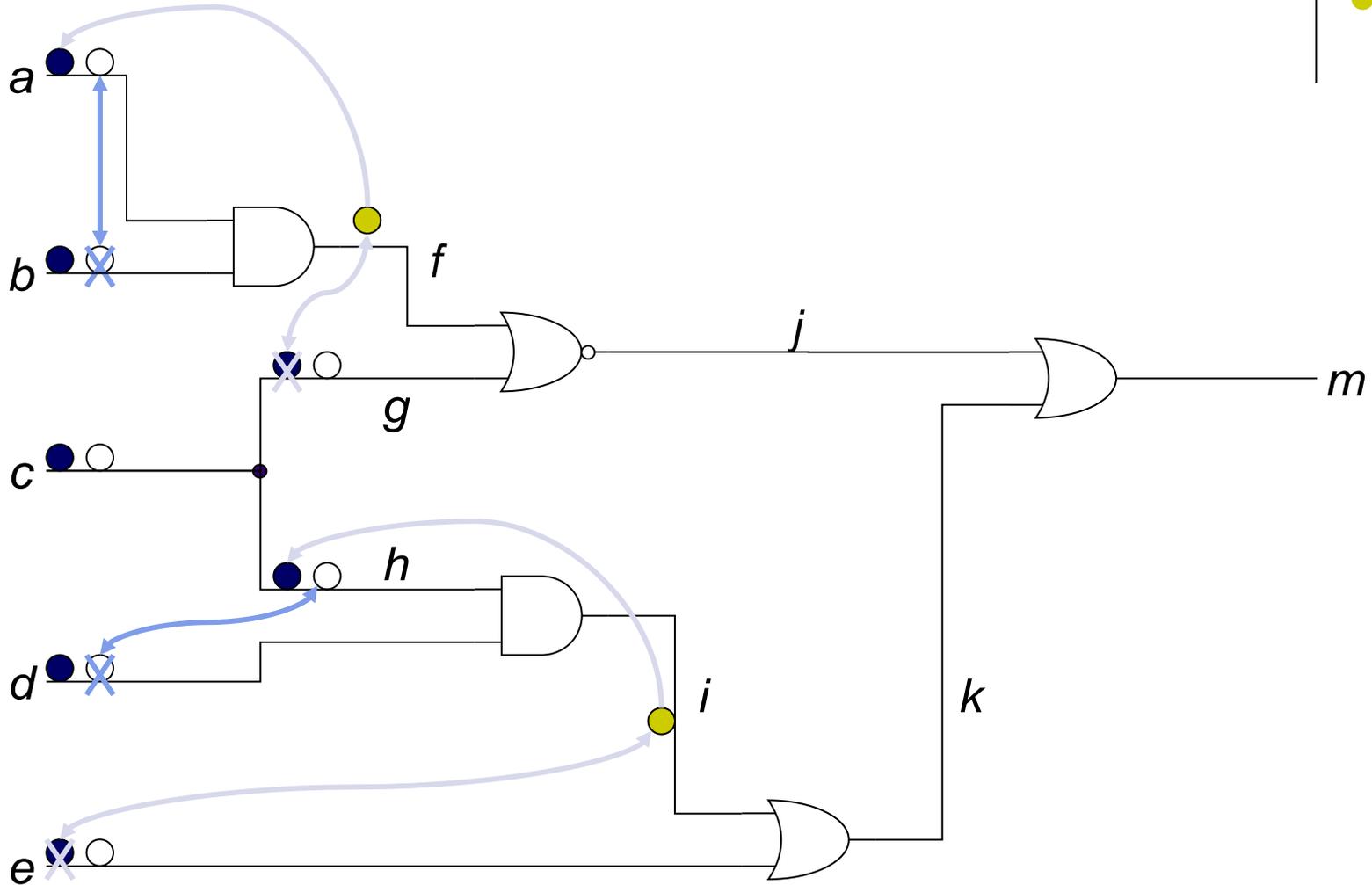


Collapsed fault list: $\{a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1\}$


Logic Simulation

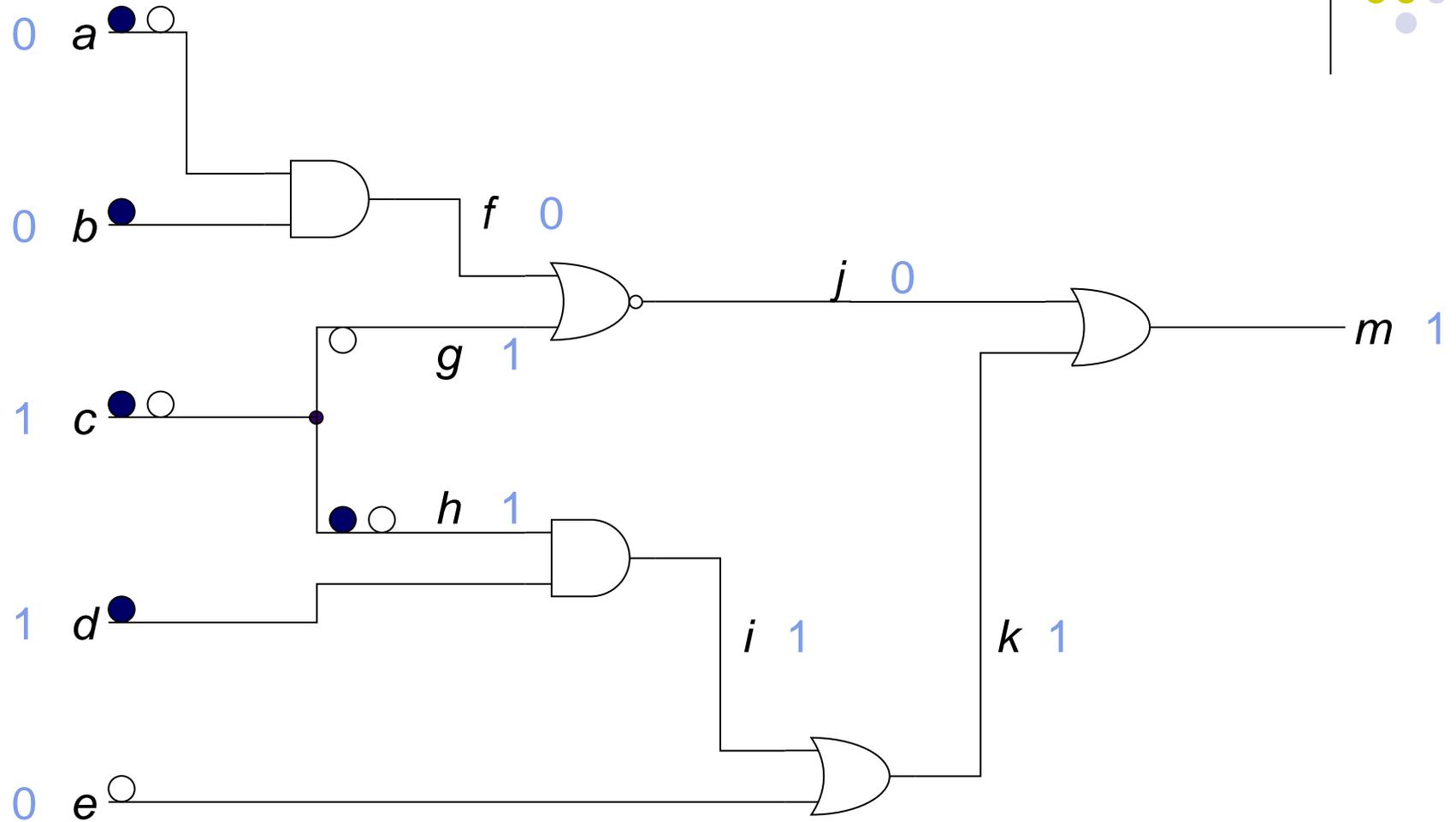



Fault List Propagation

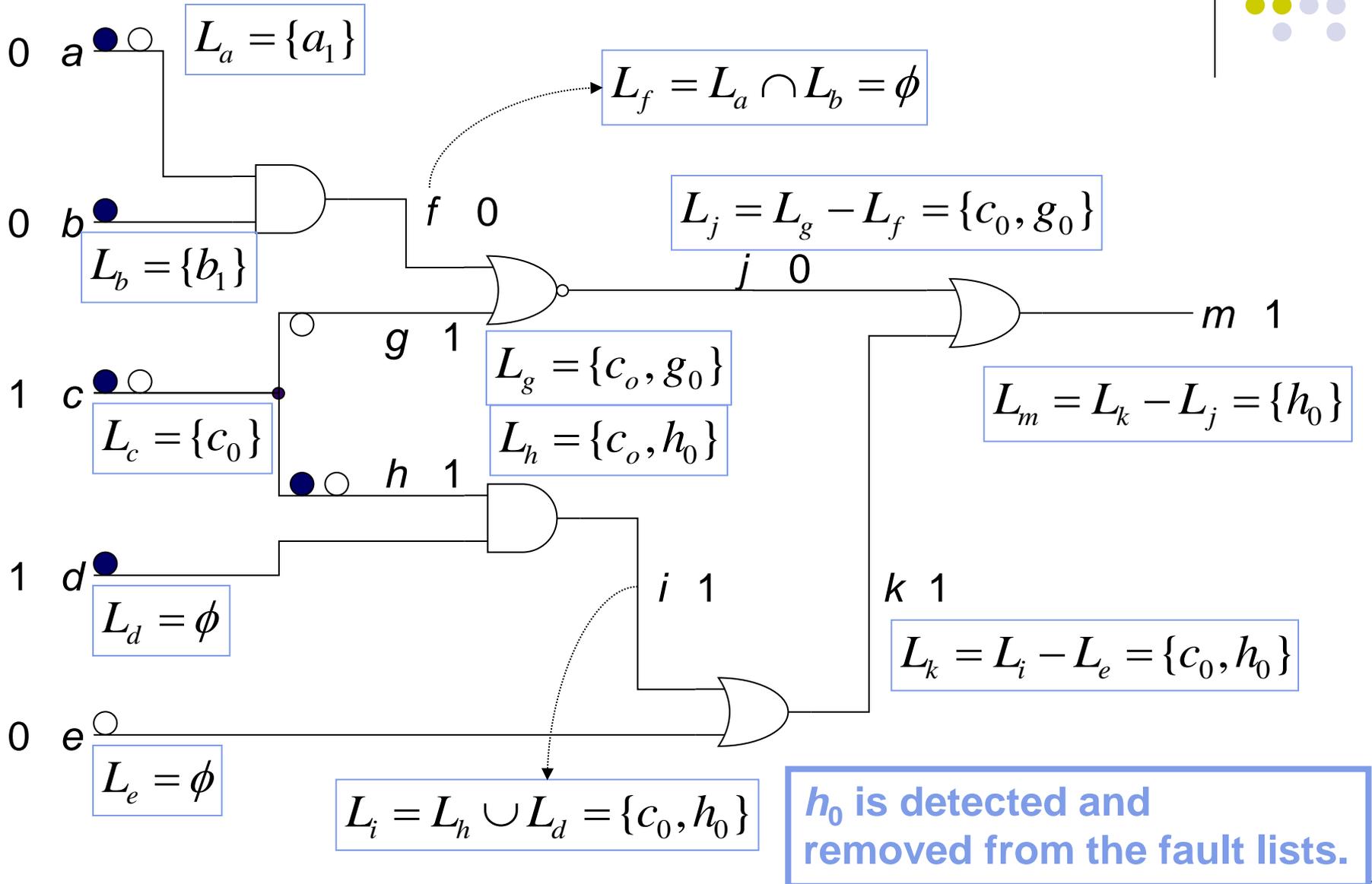

Apply the Next Vector

 

Fault List Propagation

  


Faults in Concurrent Fault Simulation




- Maintain a fault list for every signal in a list of faulty gates.
 - Each faulty gate stores the status of a fault
 1. If a fault is activated (i.e., the signal is the fault site) or
 2. Propagated to this gate.

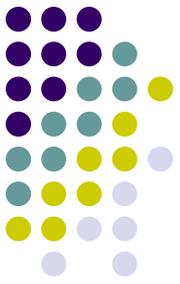Faulty Gate Structure in Concurrent Fault Simulation




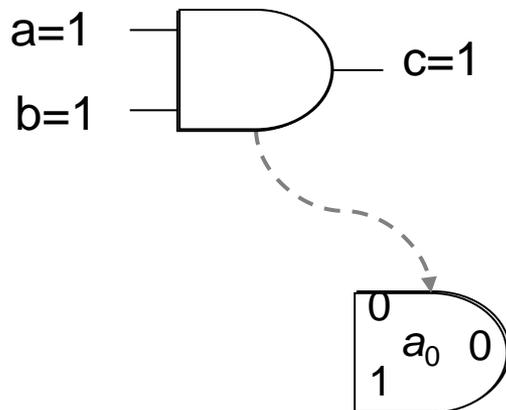- Each element in the fault list contains
 - Fault index
 - For example, a0 in the following
 - Fault states: input and output values of an element




This faulty gate (for a stuck-at 0) changes a faulty input to 0 and output to 0.

Concurrent Fault Simulation

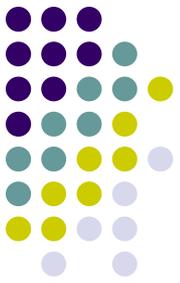

- An extension of event-driven simulation
 - Event-driven simulation for both fault free events and faulty events.
- Events in concurrent fault simulation
 - **Fault-free event:** (signal, value)
 - Generated by PI changes
 - Applied to both fault free and faulty circuits.
 - **Faulty event:** (fault index, signal, value)
 - Generated by faults
 - Applied only to the faulty circuit.

Maintain the Faulty List

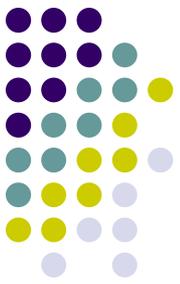



- After fault-free and faulty event propagation, an element is in the list iff the I/O values of the faulty circuit are different from the fault-free values.
- Faulty gates with the same output values as true circuits are kept,
 - Fault can propagate through multiple paths: we might need to evaluate a faulty gate several times before we know no faulty effects pass
- A local fault (at inputs or outputs of a gate) will remain in the list even there is no difference of I/O values with faulty free circuits.
 - Note that dropped faults will be deleted.

Fault Dropping




- We can hash every dropped faults, and process every faulty list to remove dropped faults.
- We can also remove dropped faults at fault site, and remove faulty gates if no fanin faulty list contains the fault.


Concurrent Fault Simulation – Example

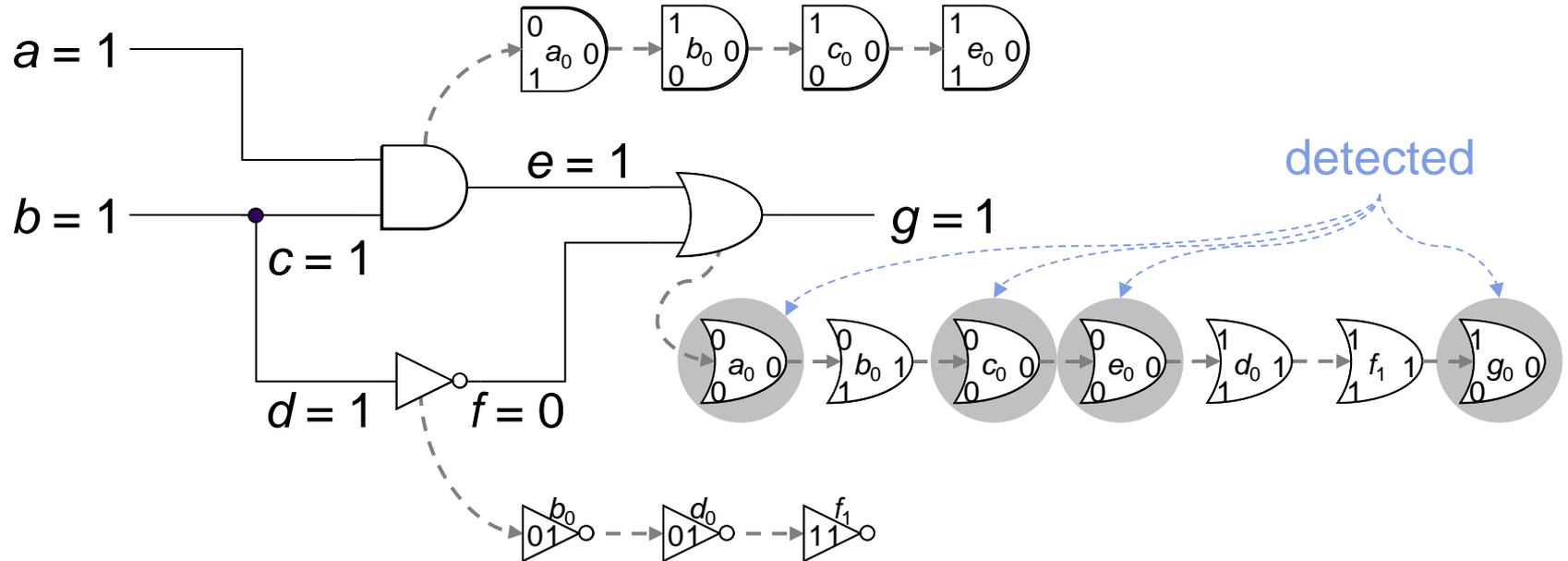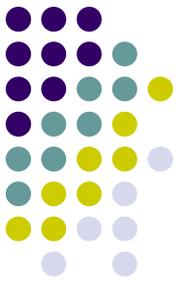


Concurrent Simulation - Convergence

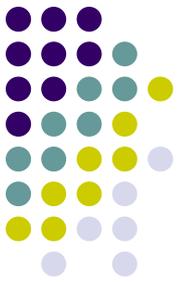

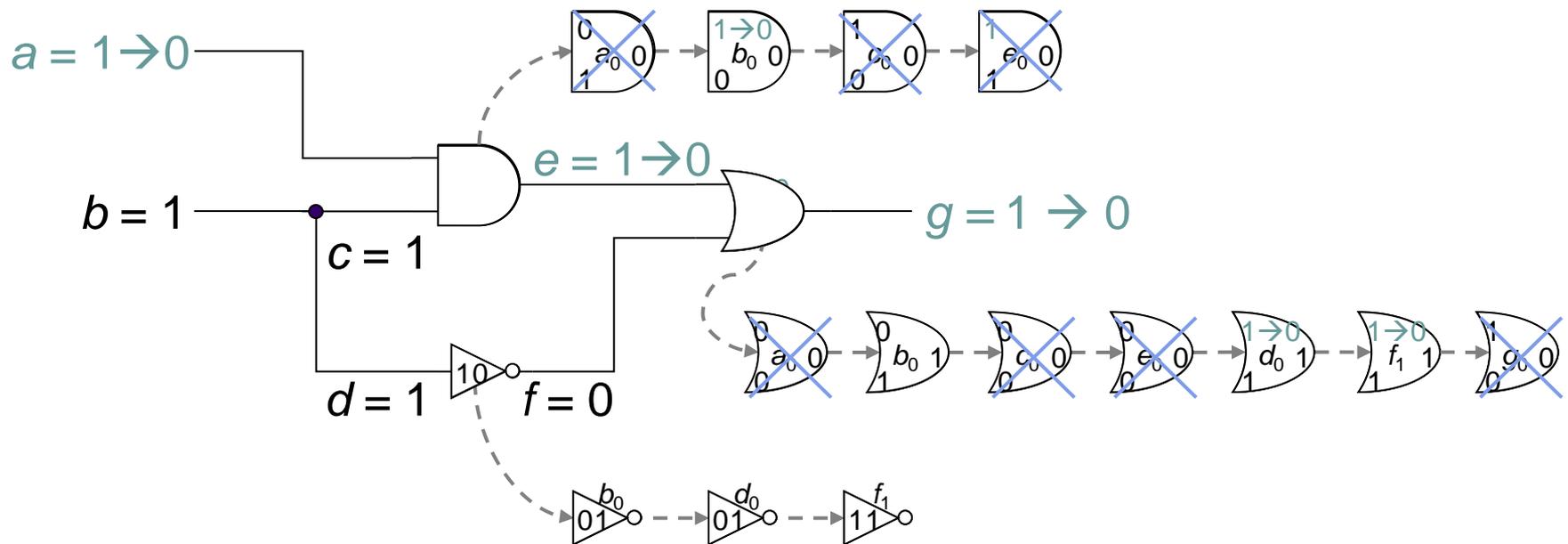
a_0 , c_0 and e_0 converge
into good gates.




Concurrent Simulation - Convergence

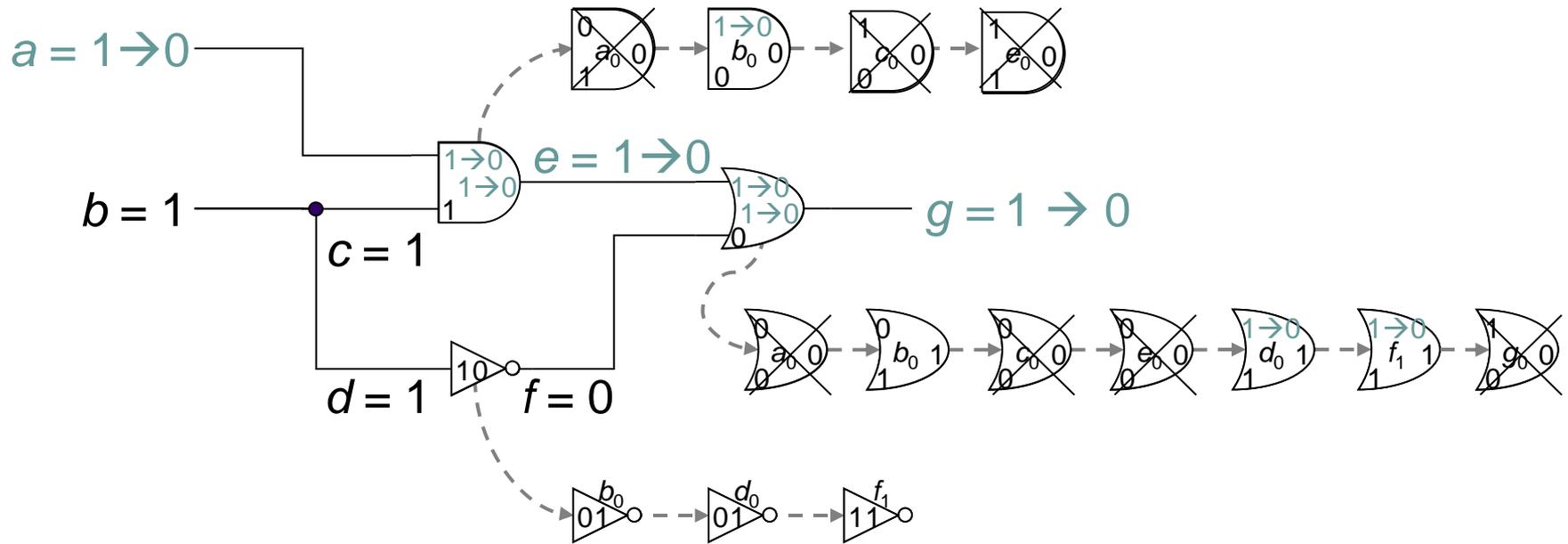

Concurrent Simulation - Divergence

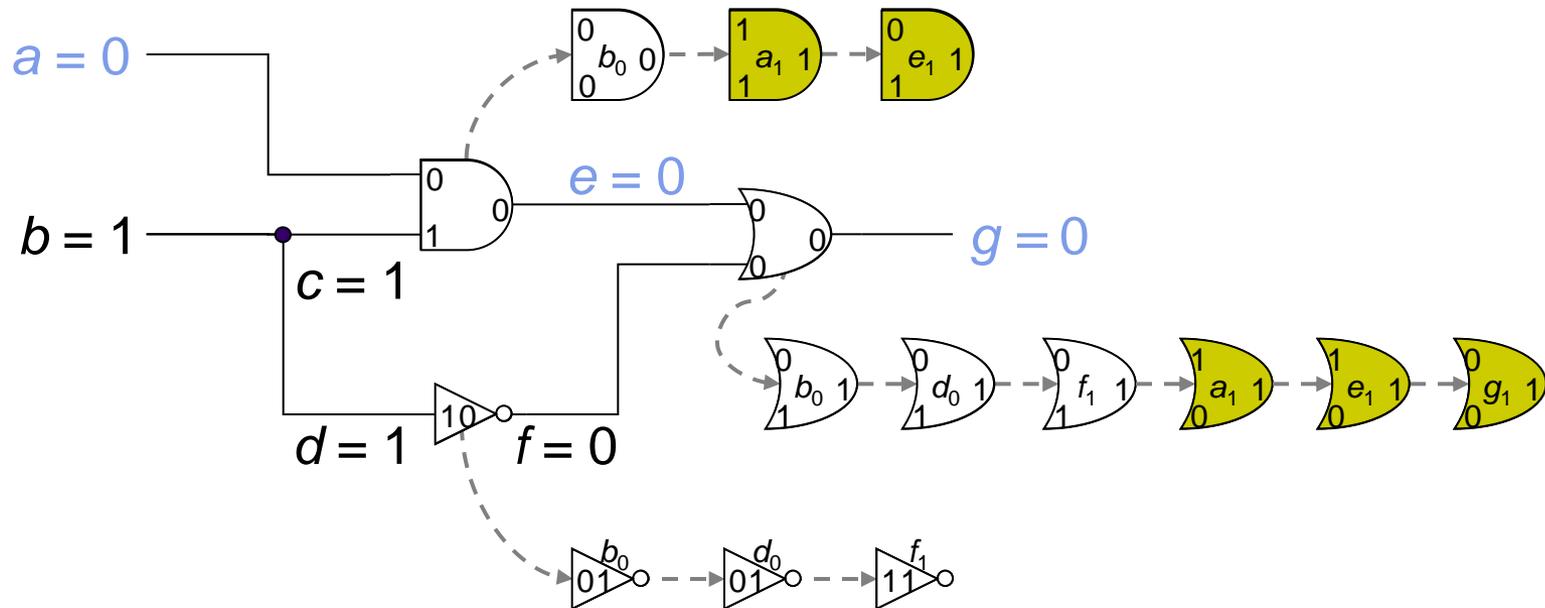

Concurrent Simulation - Divergence

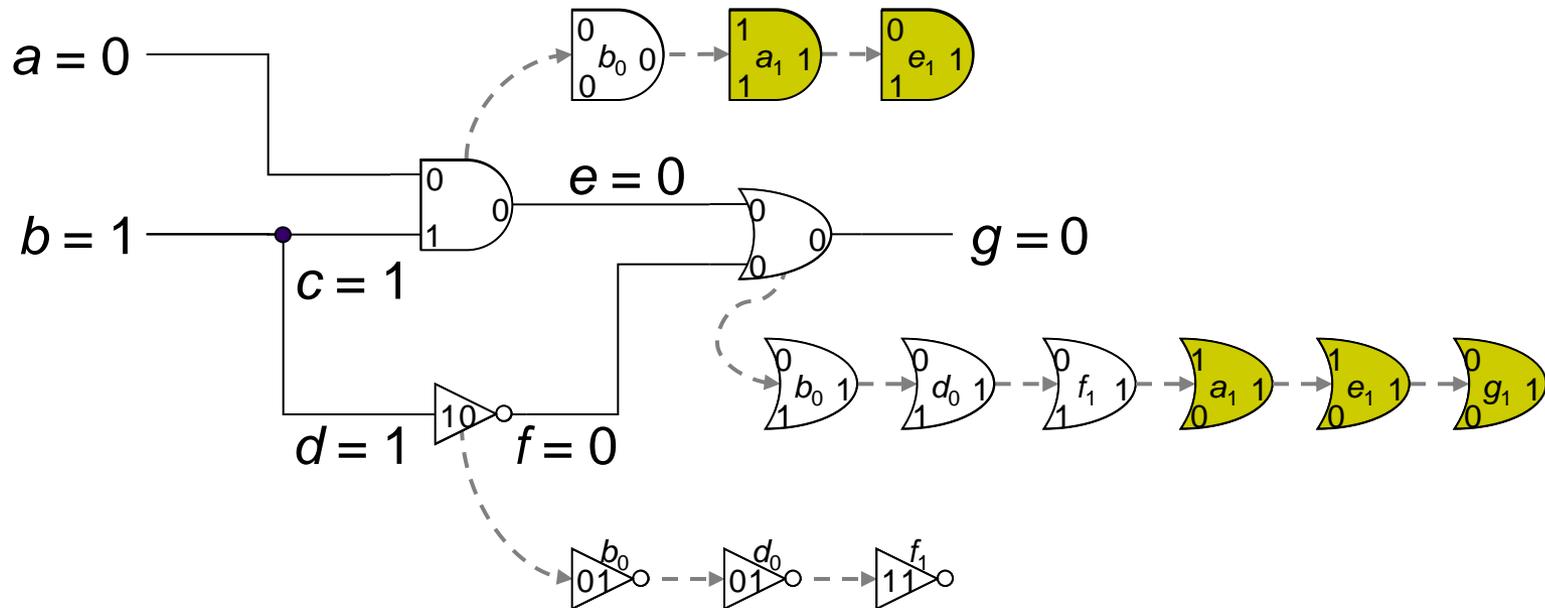

Disadvantages of Deductive & Concurrent Fault Simulation



- Large memory to record the status of all circuits (fault-free & faulty).
 - Dynamic memory (linked lists)
- Evaluation overhead on the linked lists
 - Comparing fault lists
 - Removing faults
 - Adding faults
- Performance overhead in memory management
- However, concurrent fault simulation is very popular because it is flexible.
 - Different fault types, timing, etc.

Parallel-Pattern Single-Fault Propagation (PPSFP)




- Use multiple computer words to simulate multiple input patterns.
- It can be based on an event-driven simulation.
- Simple and Extremely Efficient
 - Basis of most modern combinational fault simulators
 - Note that this is mostly the case we use a fault simulator, since ATPG is also limited to combinational circuits.
- It is also applicable to sequential circuits.

Parallel-Pattern v.s. Parallel-Fault




Parallel-pattern

(P1, P2, P3 are events by patterns)

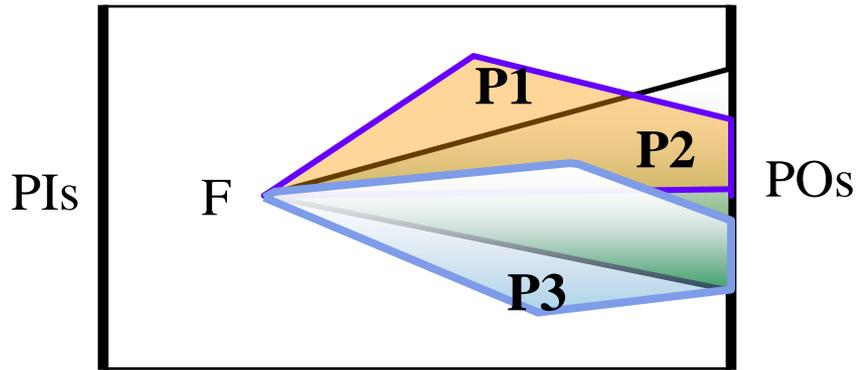


Parallel-fault

(F1, F2, F3 are events by faults)

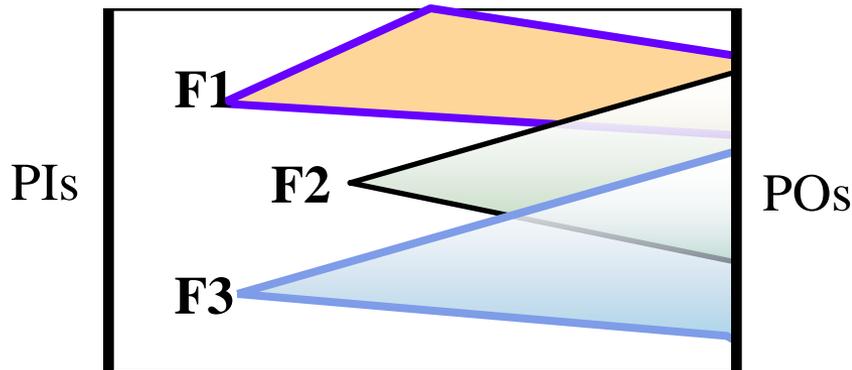

- Parallel fault simulation will be more efficient if
 - Faulty events are generated and propagated to POs.
 - Otherwise, events are useless.
- In general, parallel faults generate different events, and they are usually not detected simultaneously by a single PI pattern.
- Parallel pattern simulation is more efficient.


Re-visit Parallel Fault Simulation

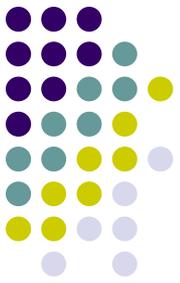


- Bit allocation:

A/0	B/1	F/0	FF
------------	------------	------------	-----------

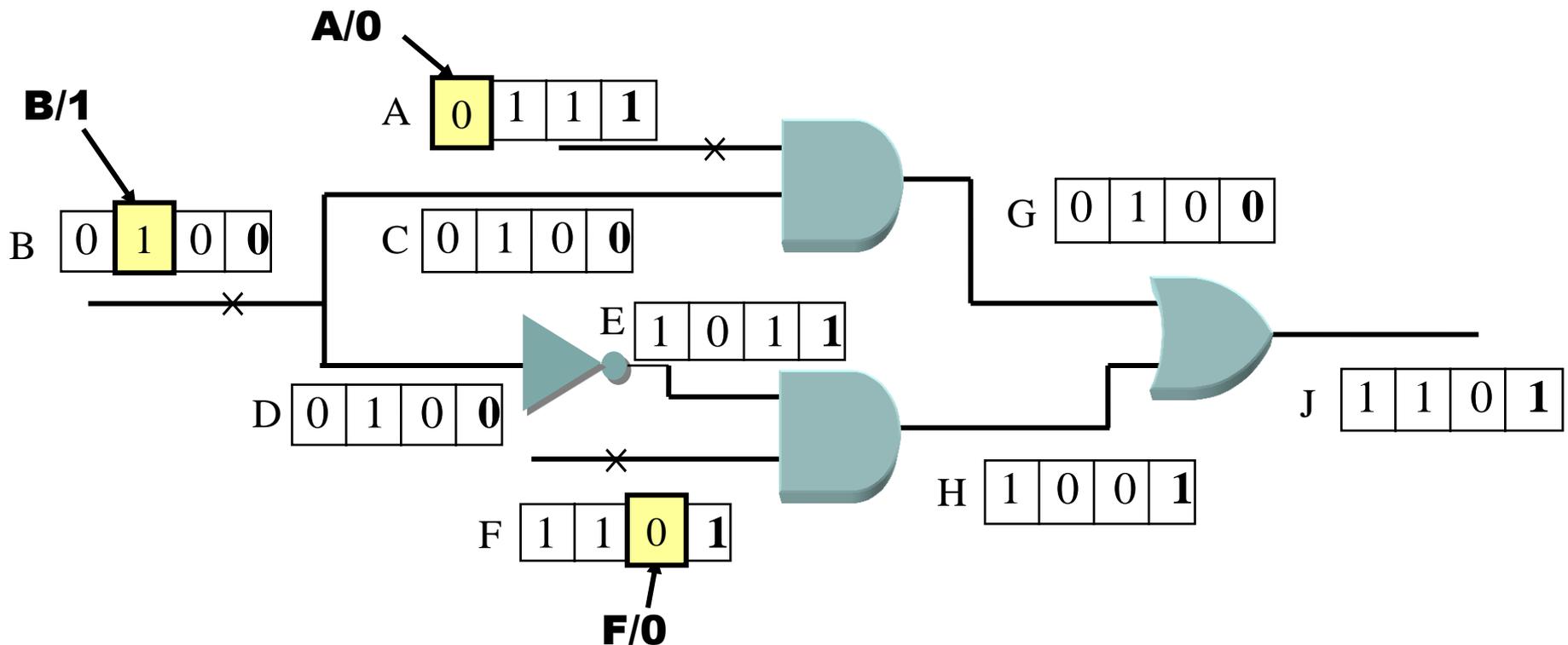 ← Fault free bit
- There are 9 events, but only one fault is detected!





Example: Parallel Pattern Simulation

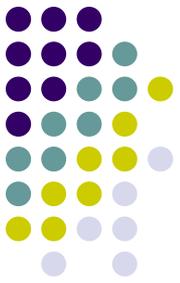

- Consider one fault F/0 and four patterns: P3,P2,P1,P0
- Bit allocation:


P3	P2	P1	P0
-----------	-----------	-----------	-----------
- There are only three faulty events!

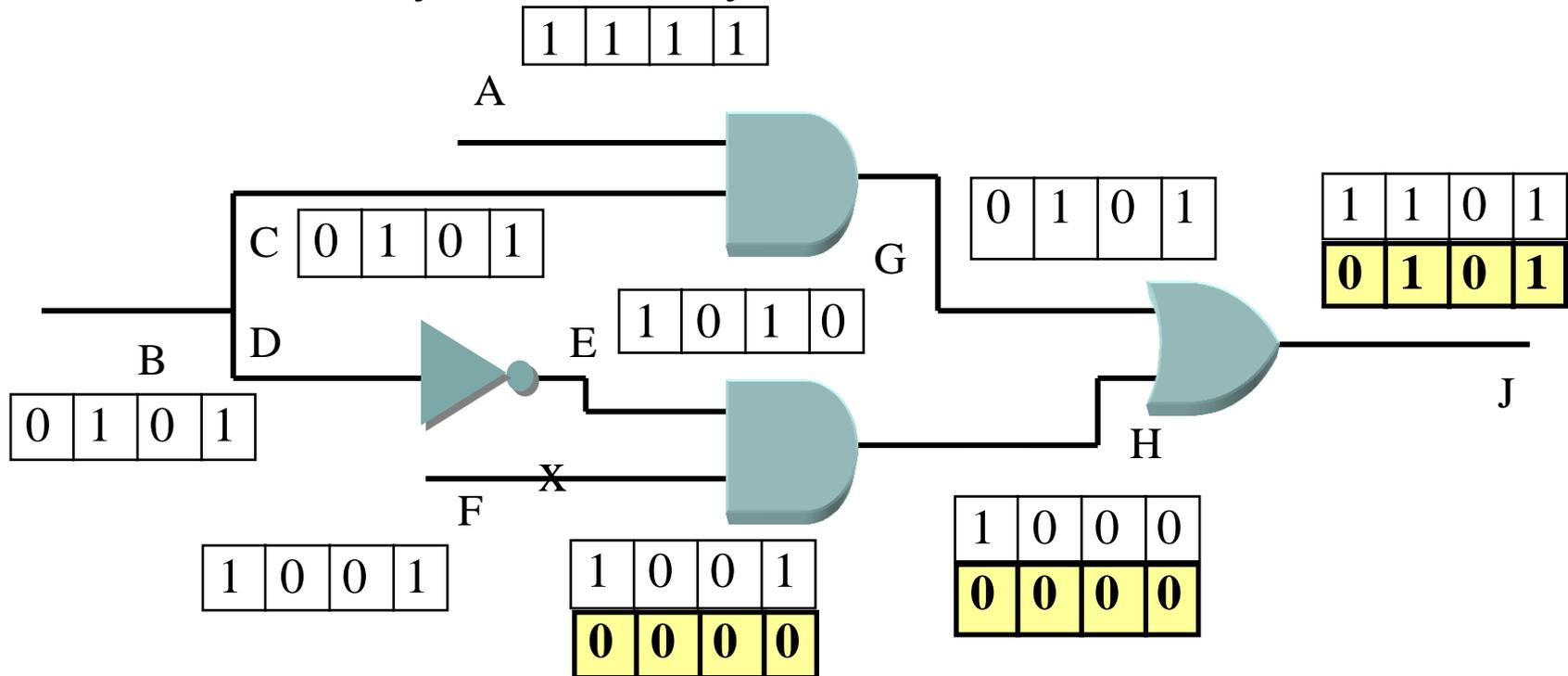

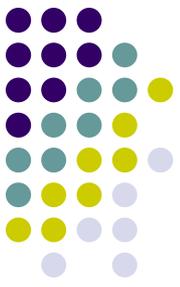


Critical Path Tracing

- Find faults detected by a test without simulating all faults.
- The key is to find critical lines in the circuits by tracing from POs.
 - line w is **critical** for a pattern t iff t detects w stuck-at v
 - fault-free value of w is v' (under t)
- Any PO is critical.
- Find whether any inputs of gates to PO are critical recursively
 - If a line of a gate output is critical, the critical property can be transferred to its sensitive inputs.
 - A gate input i is **sensitive** if complementing the value of i changes the value of the gate output

 

Algorithm of Critical Path Tracing

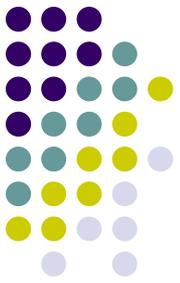


- For a fanout-free circuit,
 - Critical lines can be determined by backward traversing the sensitive gate inputs from PO's, in linear time
 - In general, special processing has to be done for stems
- General Critical path tracing:
 1. Fault-free simulation
 2. Extract single-PO logic cones and process each cone
 1. Process stems with highest levels
 2. If **the stem is critical**, mark critical lines in the fanout free region according to the sensitivity properties.


Critical Property of a Stem



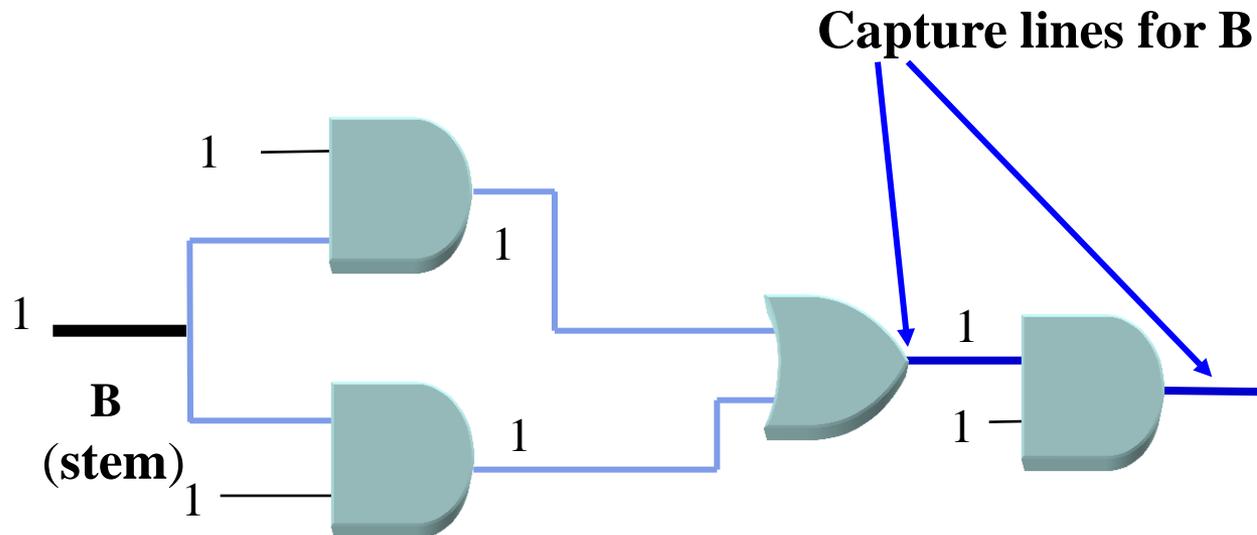- A stem is critical
 - If all the capture lines are critical.
 - All sensitized paths to POs for the stem pass through the capture lines (dominator).
- Note that this is only an approximation!



Problems of Critical Path Tracing

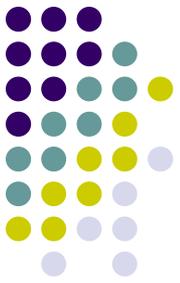


- The fault coverage by complete critical path tracing is approximate.
 - Self-masking paths lead to over-estimation
 - Multiple-path sensitization leads to under-estimation.
- Not very useful as a standalone simulator.
- Applied to individual fanout-free regions
 - Note that stem faults are only simulated to its dominators and then faults at dominators become representatives.



Self-masking Paths



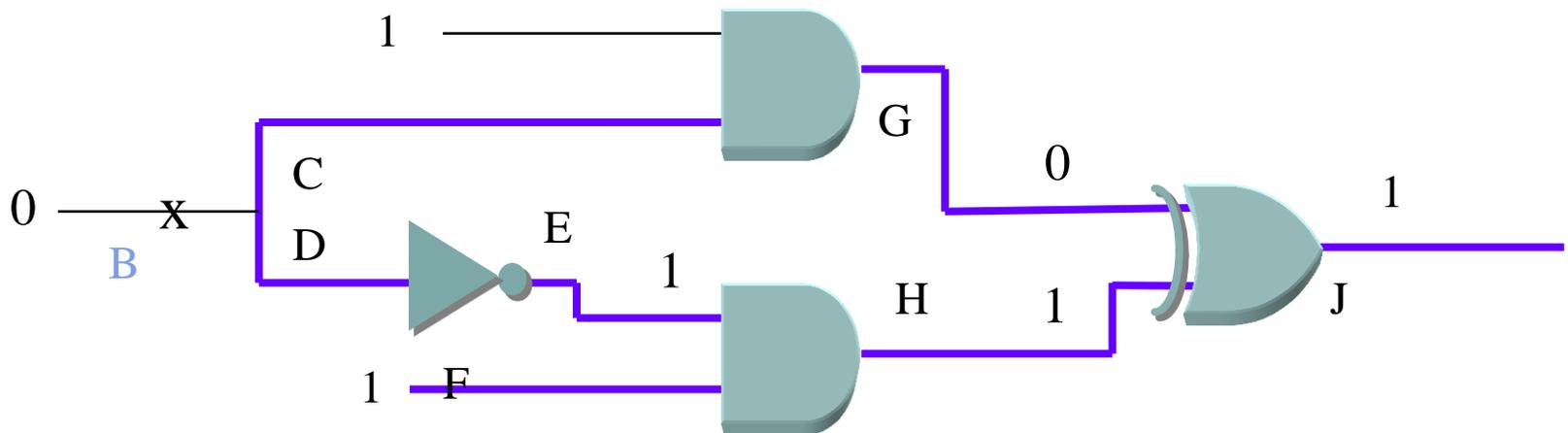- Detected faults in the fanout-free region: {J/0, H/0, G/1, F/0, E/0, D/1, C/1}
- **Stem criticality** is hard to infer from branches.
 - For example, is B/1 detectable by the given pattern?
- **B/1 is not detectable** even though both C and D are critical, because their effects cancel out each other at gate J
 - **Self masking when** paths go through different inversions



Multiple Path Sensitization

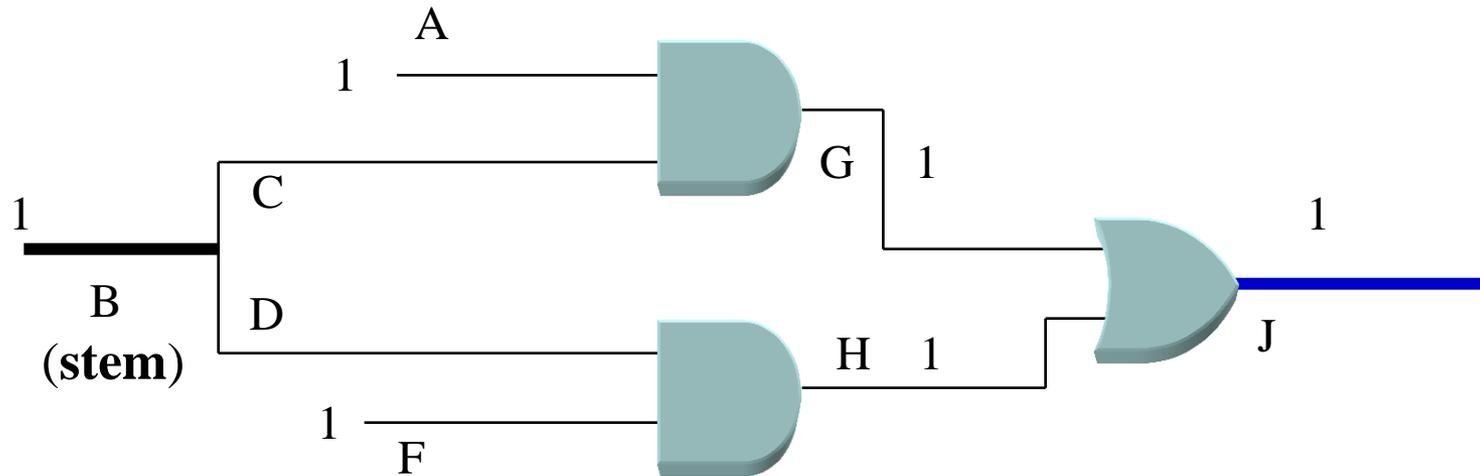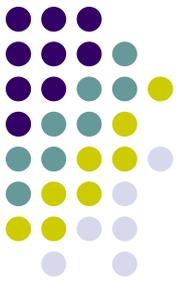


Both C and D are not critical, yet B is critical and B/0 can be detected at J by multiple path sensitization.

Techniques for Sequential Fault Simulation




- Fault simulation without restoration
- Fault grouping for parallel fault simulation
- Single Event Faults
- Management of hypertrophic faults
- Parallel pattern simulation for sequential circuits

Sequential Circuit Model

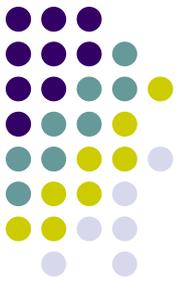


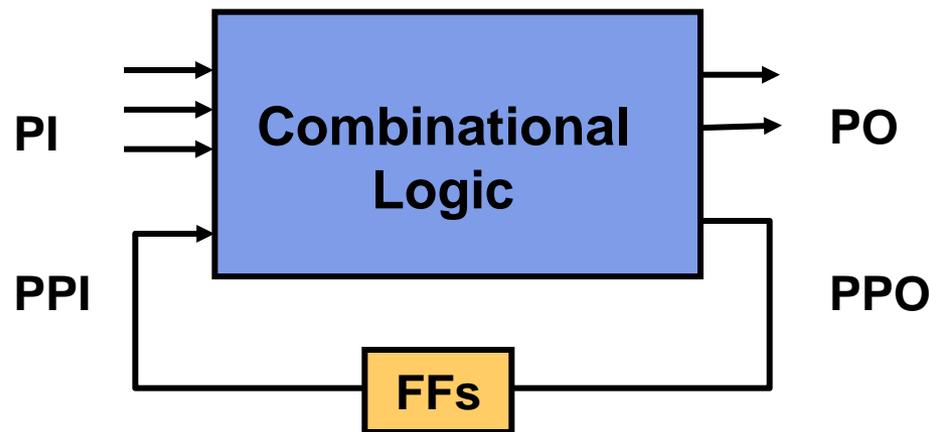- For sequential circuits, a Huffman model will be used for the following discussion.




PPI: pseudo primary inputs (i.e., outputs of flip-flops)
PPO: pseudo primary outputs (i.e., inputs of flip-flops)

Faulty State in Sequential Simulation

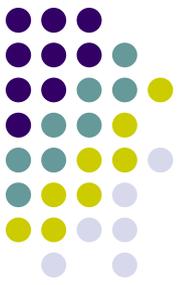

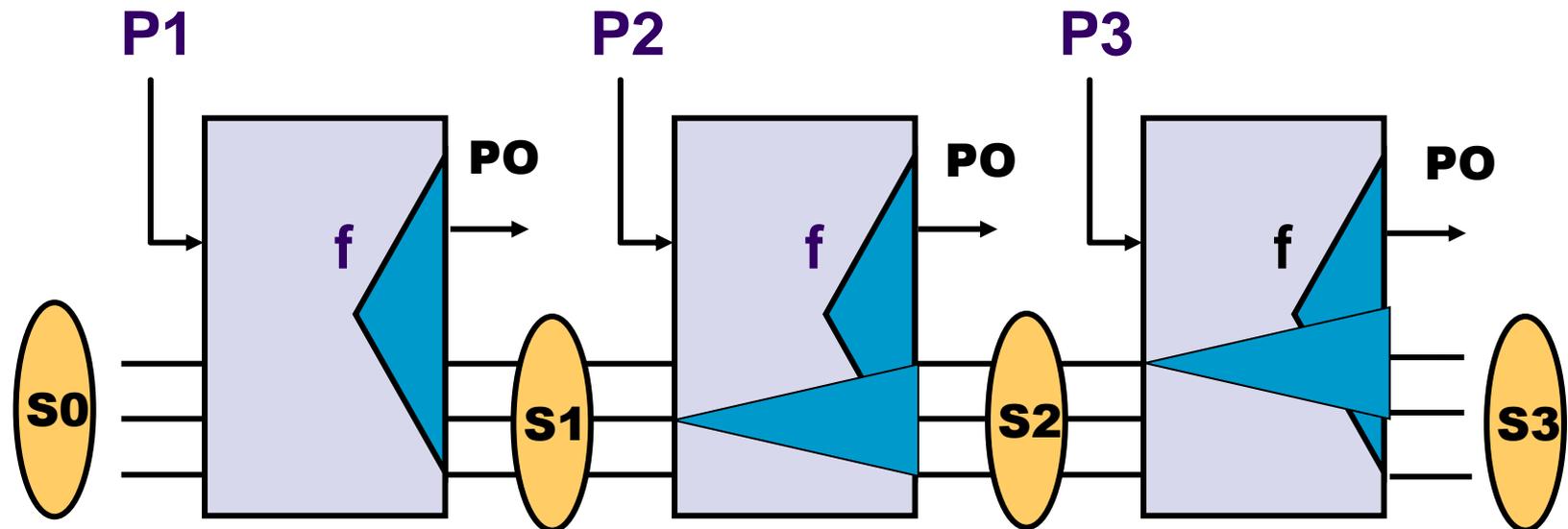
- Faults will propagate to FF's
 - Need to record faulty states
 - Like multiple faults



Ex: Input Sequence (P1, P2, P3)



State Sequence (S0 → S1 → S2 → S3)

Fault Simulation without Restoration

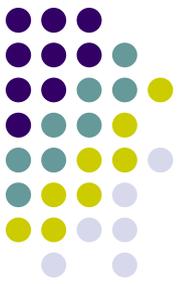


- A new fault can be simulated without restoring status of previous fault status to fault-free value.
 - To store and restore fault-free values is inefficient
- Techniques for simulation without restoration
 - Only two sets of values are retained at each gate: one for fault-free and one for faulty ones.
 - Each active fault at any given time is given a unique identifier (ID).
 - Only faulty values with the same ID are used.
 - Otherwise, true values are used.
- Efficient in both time and memory space[ROOFS89].

Simulation without Restoration

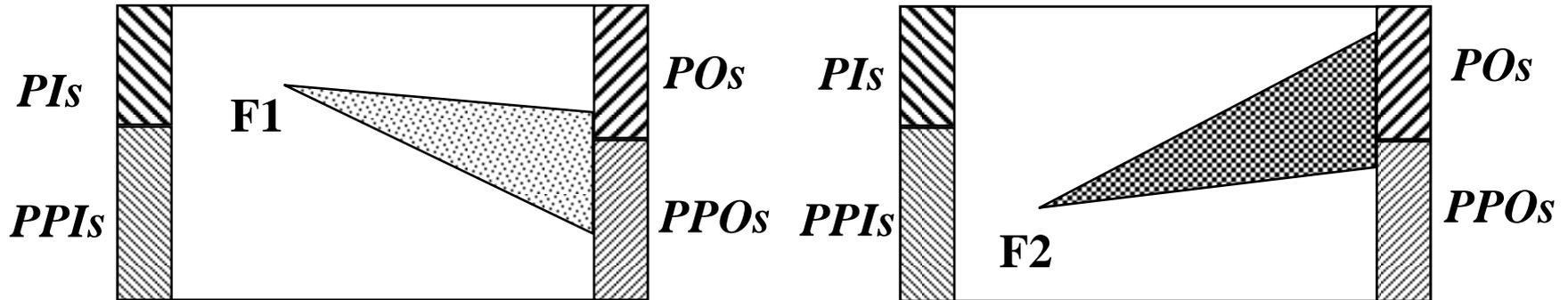 


 With Restoration: Effect of F1 is cleared before simulating F2




Without Restoration: F2 is simulated right over effect of F1

Fault Grouping

 


- Faults with coincident events can be grouped together for parallel simulation.
 - **Static fault grouping**
 - Based on circuit structure such as fan-in cone, depth-first path from POs.
 - **Dynamic fault grouping**
 - Fault grouped according to the similarity of faulty states
 - At the beginning of each time frame, faults are dynamically re-grouped for effective usage of all bits in a word

 Fault Grouping in Parallel Fault Simulation



- The lower grouping case is evidently more desirable than the upper case because similar faulty events are simulated in parallel.
- Similar events have higher probability to be
 - dropped together
 - detected together
- Distinct faulty events will cause unnecessary simulation of inactive faults


Single Event Faults

 

- For circuit in a time frame, faults are classified into **single event faults**, e.g. , F1, and **multiple event faults**, e.g., F2.

- Single event faults are those whose effects originate only from the fault sites of the current time frame.
- Sophisticated combinational techniques, such as **simulate-to-dominators**, can then be applied with significant performance improvement.
- Only single-event stem faults or multiple-event faults are parallel-simulated.
- [HOPE DAC92]

Hypertrophic Faults

 



- A hypertrophic fault is a fault that diverges from the fault-free circuit with a large number of X's
 - Usually a stuck-at fault occurring at a control line and thus prevents the circuit initialization
 - A small number of hypertrophic faults can account for a large percentage of fault events and CPU time
- These faults are sometimes dropped
 - as **potentially detected faults** to reduce simulation time. (Fault coverage is approximate)
- In parallel fault simulator
 - such as PROOFS, these faults can be simulated in parallel with fault-free circuit with little additional memory while achieving performance close to approximate simulator [HyHOPE IEE Circuits, Devices and Systems 94].

Parallel Pattern Simulation for Sequential Circuits



- Sequential circuits are state dependent by nature
 - However, many of them have a short memory, which can be exploited by parallelism of sequences or patterns.
- The basic mechanism of both parallel sequence and pattern
 - To initialize unknown FFs as Xs
 - Simulate the circuit and update the FFs by multiple passes.
 - States will converge to the true values eventually.
- The convergence rate (# of passes)
 - Determines the speed of simulation.
 - Usually small compared with the word length
 - Dependent on the circuit as well as the given sequence.

Sequential Simulation Example

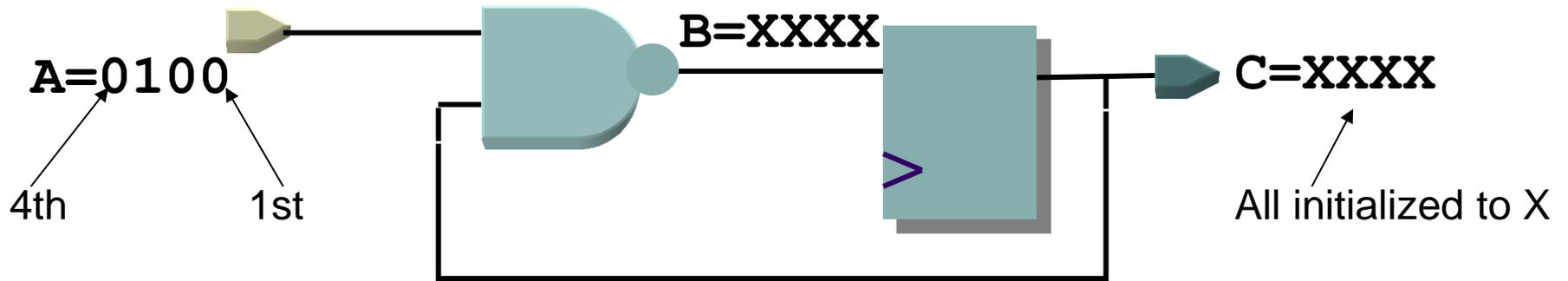 


1st **A=0**
A=0
A=1
 4th **A=0**

B=XXX1
B=XX11
B=X011
B=1011

C= XX1X
C= X11X
C= 011X
C=1011X

To be used for 5th

Parallel Sequential Simulation Example

 

A=0100

B=1X11

C=1X11X

A=0100

B=1011

C=1011X



A=0100

B=1011

C=1011X


Converge for three passes

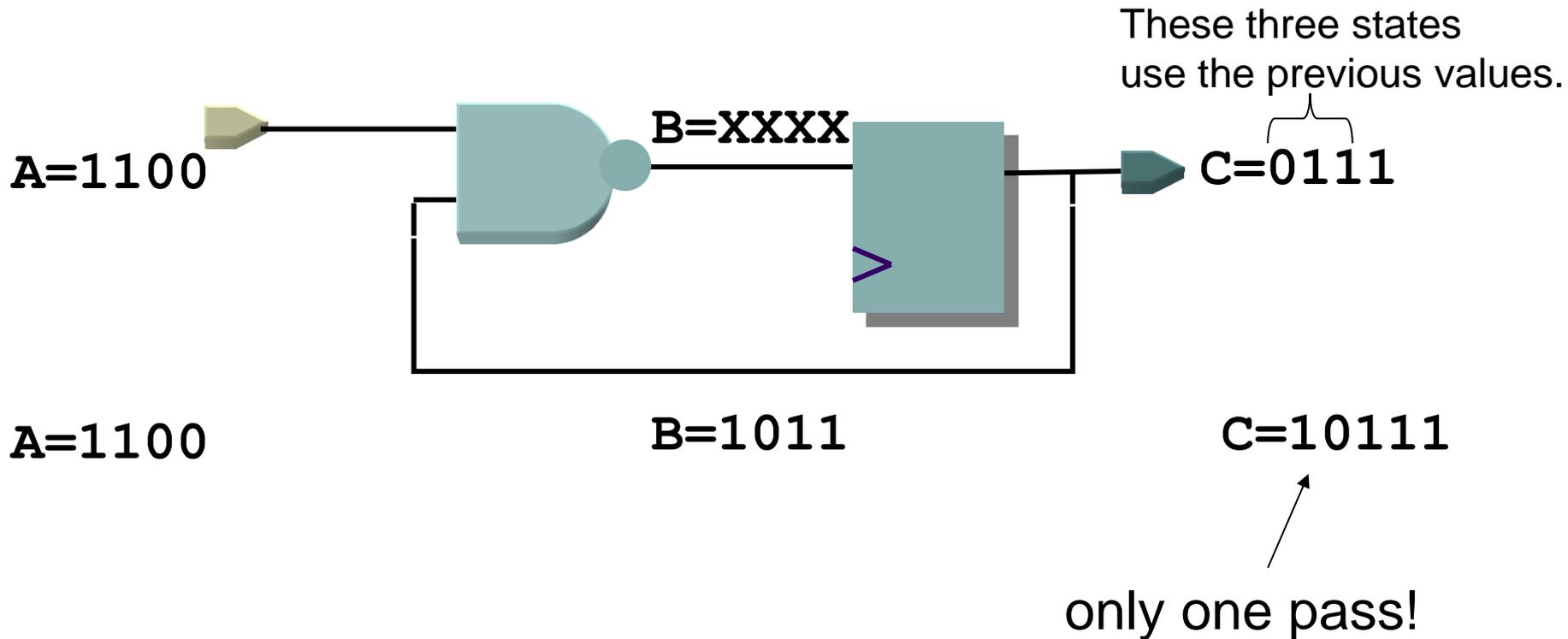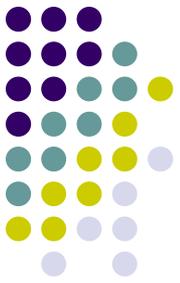Parallel Sequential Simulation with Look-ahead Heuristic



Usually most state variables stay the same, so they are good guess for next simulation.

 Parallel Sequential Simulation Example (If Look-ahead not used)




A=1100
A=1100
A=1100

B=XX11
B=X011
B=1011

C=XX111
C=X0111
C=10111

Also need three passes

 
An Extreme Example of Short-Memory Circuit



A pipelined data-path

Because there is no feedback, every patterns can be simulated independently.

Fault Grading

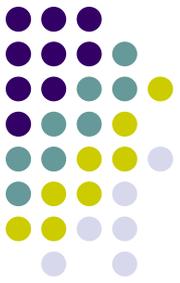


- Approximate fault coverage
 - Can be obtained in much shorter computational time than regular fault simulation.
 - Not suitable for high fault coverage.
 - It often occurs that the accuracy requirement exceeds error ranges of fault grading.
- Typical fault grading methods:
 - Toggle test, e.g. DATAS
 - Detection probability computation, e.g. STAFAN
 - Fault sampling
 - Estimate from a selected subset of total faults

Toggle Test



- Circuit node transition
 - is computed during logic simulation and the number of node transition or toggle rate is used as the basis of fault coverage estimation.
 - e.g. **zero toggle rate** implies either s-a-0 or s-a-1 is not detected.
- Only logic simulation is performed.
 - very low computational cost
- Controllability-based estimation
 - Single stuck-at faults are only activated but not necessary propagated to POs.

STAFAN

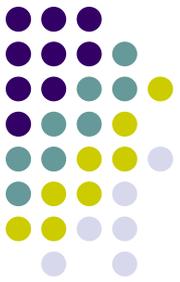


- Compute fault detection probability from logic simulation.
 - d_l = detection probability of s-a-0 on l = $C1(l)O(l)$
 - d_l = detection probability of s-a-1 on l = $C0(l)O(l)$

$$C0(l) = \frac{0\text{-count}}{n}, \quad C1(l) = \frac{1\text{-count}}{n}$$


$$S(l) = \frac{\text{sensitization-count}}{n}$$

$$O(l) = S(l)O(m)$$

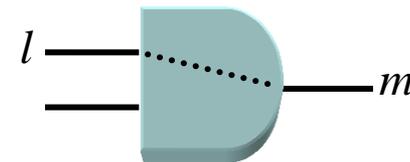

- m is the immediate successor of l
- **observability** can be computed backwards from POs

STAFAN(cont.)

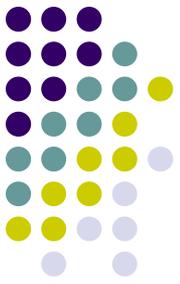

- The probability of detecting a fault with n test vectors

$$d_f^n = 1 - (1 - d_f)^n$$

- n is the # of vectors
- $(1 - d_f)^n$ is prob. of not being detected **after n test vectors**


- The fault coverage is
$$\frac{\sum_{f \in \Phi} d_f^n}{|\Phi|}$$

- Φ is the number of total faults of interests
- More sophisticated than toggle test with same computation complexity

Fault Sampling



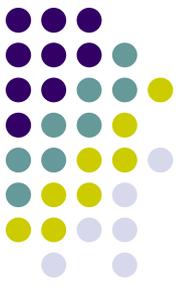- M : total number of collapsed faults
 m : number of faults randomly selected
 K : number of faults detected by the test set T
 k : number of selected faults detected by T
- Actual fault coverage $F = K/M$
- $P_k(M, m, K)$: the probability that T will detect k faults from a random sample size of m , given that it detects K faults from the entire set of M faults.



- $$P_k(m, M, K) = \frac{C_k^K C_{m-k}^{M-K}}{C_m^M}$$

- **P_k is hypergeometric distribution with**
mean $\mu_k = m K / M = m F$
variance $\sigma_k^2 = m K / M [1 - k / M] (M - m) / (M - 1)$
 $\cong m F (1 - F) (1 - m / M)$
- For large M , this distribution can be approximated by a normal distribution with mean μ_k and standard deviation σ_k



- **The estimated fault coverage f is a random variable with normal distribution:**

$$\mu_f = \mu_k / m = F$$

$$\sigma_f^2 = \sigma_k^2 / m^2 = (1/m)F(1-F)(1-m/M)$$

- **With a confidence level of 99.7%, the estimated fault coverage $f \in [F-3\sigma_f, F+3\sigma_f]$.**

$$e_{\max} = 3\sqrt{F(1-F)(1-m/M)1/m}$$
$$\cong 3\sqrt{F(1-F)/m} \quad \text{if } m \ll M$$

Independent of M !!

Maximum Errors of the Estimated Fault Coverage

